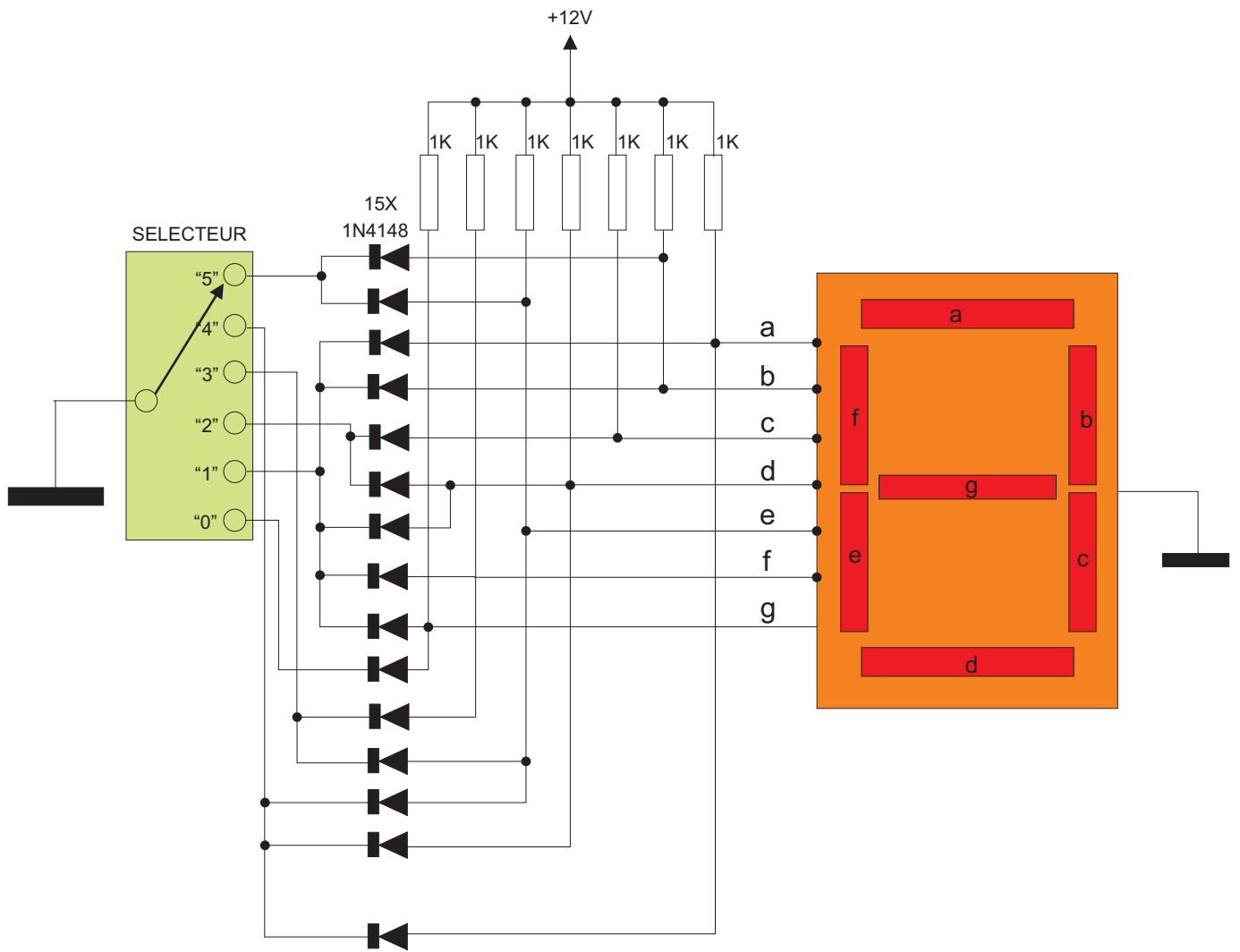


SELECTEUR DE VITESSE



LOGIQUE NEGATIVE= 15 DIODES 1N4148

AFFICHAGE ->	Nb diodes		Diagrammes des segments allumés							
	5	15	1	2	3	4	5	6	7	
"0"	5	1	a,b,c,d,e,f							
"1"	2			b,c						
		5	a,d,e,f,g							
"2"	5				a,b,d,e,g					
		2	c,f							
"3"	5					a,b,c,d,g				
		2	e,f							
"4"	4						b,c,f,g			
		3	a,d,e							
"5"	5								a,c,d,f,g	
		2	b,e							

LOGIQUE "POSITIVE" 26
 LOGIQUE "NEGATIVE" 15