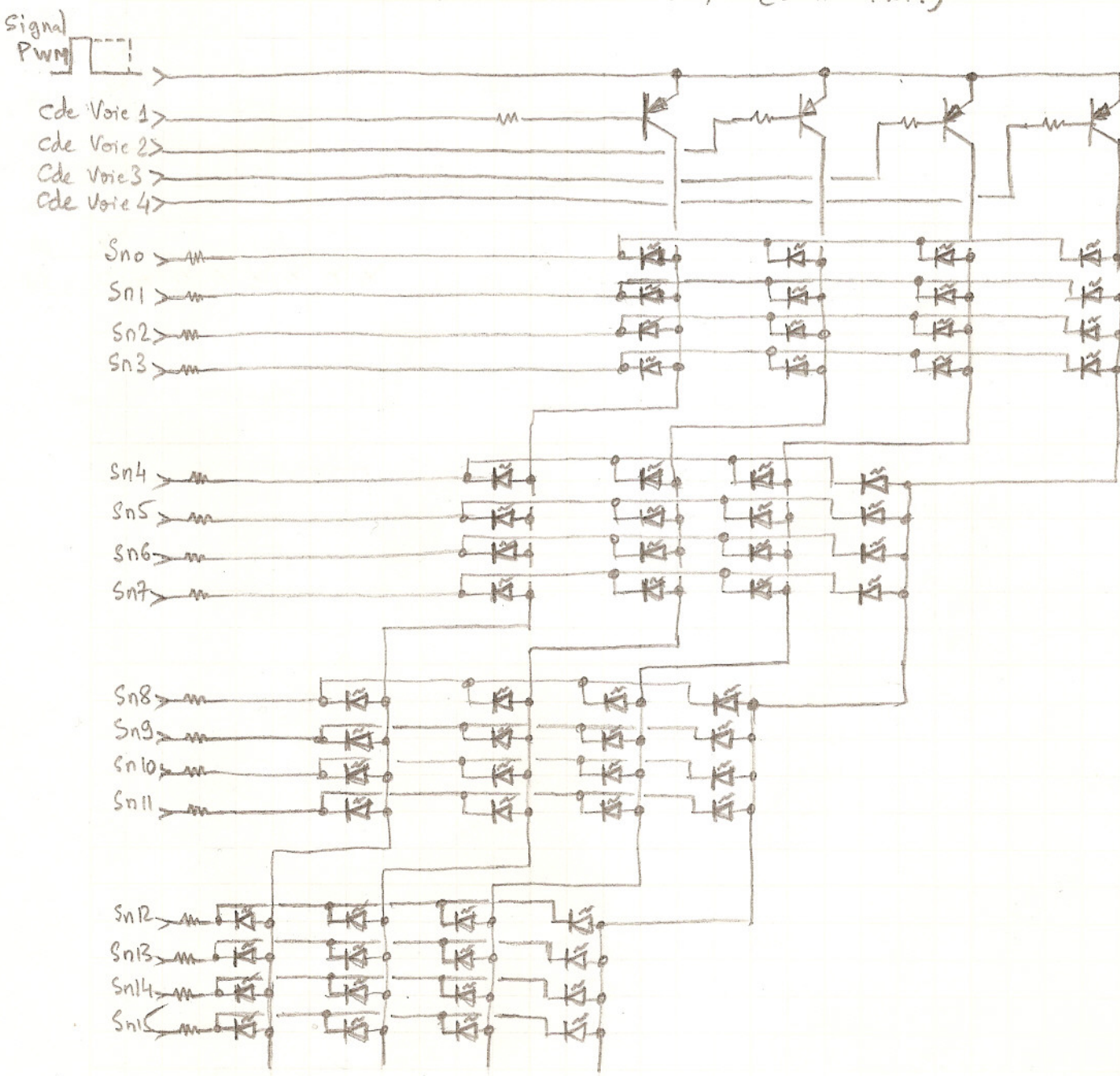


SOLUTION AVEC 21 I/O (dont 1 PWM)



Extrapolable en =

cube 5x5x5	→	26 I/O	pour 125 LEDS	} Pic 16F876/16F877
cube 6x6x6	→	31 I/O	pour 216 LEDS	
cube 7x7x7	→	36 I/O	pour 343 LEDS	} Pic 18F6622
cube 8x8x8	→	41 I/O	pour 512 LEDS	

