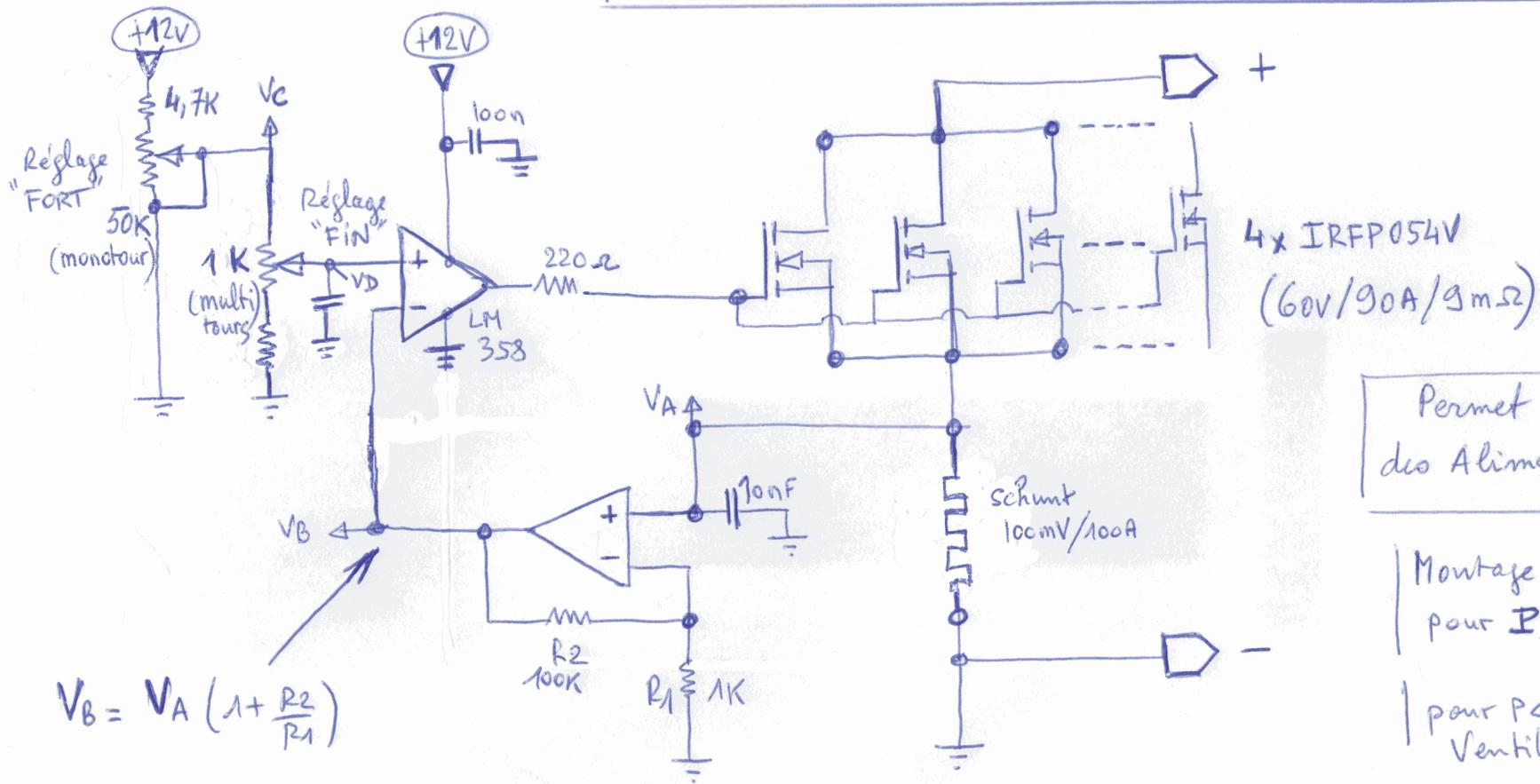


$$\begin{cases} 0V < V_C < 10V \\ 0 < V_D < V_C \end{cases}$$

# BANC DE CHARGE POUR TESTER LES ALIM DE FORTES PUISSANCES



4x IRFP054V  
(60V/90A/9mΩ)

Permet de tester  
des Alims 40V/100A

Montage en bain d'huile  
pour P > 300W

pour P < 300W  
Ventilation forcée

$$V_B = V_A \left(1 + \frac{R_2}{R_1}\right)$$

$$2 < V_B < 10V$$

$$0 < V_A < 100mV$$

$$\Rightarrow 1 + \frac{R_2}{R_1} = \frac{V_B}{V_A} = \frac{10}{0,1} = 100$$

$$\Rightarrow \frac{R_2}{R_1} = 99 \Rightarrow R_1 = \frac{R_2}{99}$$

$$R_1 + R_2 = \frac{V_B}{100\mu A} = \frac{10}{100 \cdot 10^{-6}} = 100K\Omega$$

Si	$V_A = 1mV (\Rightarrow 1A)$	$\Rightarrow V_B = 100mV$
	$V_A = 10mV (\Rightarrow 10A)$	$\Rightarrow V_B = 1V$
	$V_A = 50mV (\Rightarrow 50A)$	$\Rightarrow V_B = 5V$
	$V_A = 100mV (\Rightarrow 100A)$	$\Rightarrow V_B = 10V$

$$\begin{aligned} R_1 &= 100K - 99R_1 \\ \Rightarrow R_1(1+99) &= 100K \Rightarrow R_1 = \frac{100K}{100} = 1K / R_2 = 99R_1 \neq 100K \end{aligned}$$