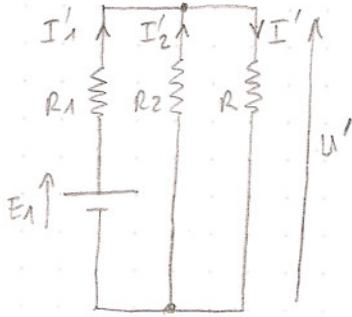


$$\begin{cases} R_1 = 10 \Omega \\ Y_1 = 0,1 \text{ S} \end{cases} \quad \begin{cases} R_2 = 20 \Omega \\ Y_2 = 0,05 \text{ S} \end{cases} \quad \begin{cases} R = 30 \Omega \\ Y = 0,033 \text{ S} \end{cases}$$

$$E_1 = 10 \text{ V}; E_2 = 20 \text{ V}.$$

Q1



a/ Equations du nœud A:

$$I'_1 + I'_2 = I' \quad Y = \frac{1}{R}; Y_1 = \frac{1}{R_1}; Y_2 = \frac{1}{R_2}$$

$$\begin{cases} V_A = E_1 - R_1 I'_1 \\ V_A = -R_2 I'_2 \\ V_A = U' = +R I' \end{cases} \Rightarrow \begin{cases} V_A = E_1 - \frac{I'_1}{Y_1} \\ V_A = -\frac{I'_2}{Y_2} \\ V_A = U' = \frac{I'}{Y} \end{cases}$$

$$\Rightarrow \begin{cases} I'_1 = (E_1 - V_A) Y_1 \\ I'_2 = -V_A Y_2 \\ I' = V_A Y \end{cases}$$

$$b/ U' = V_A = \frac{I'}{Y} = \frac{I'_1 + I'_2}{Y} = \frac{(E_1 - V_A) Y_1 - V_A Y_2}{Y}$$

$$\Rightarrow U' = \frac{(E_1 - U') Y_1 - U' Y_2}{Y}$$

$$\Rightarrow U' (Y + Y_1 + Y_2) = E_1 Y_1$$

$$\Rightarrow \boxed{U' = \frac{E_1 Y_1}{Y + Y_1 + Y_2}} \quad \text{AN: } \boxed{U' = 5,45 \text{ V}}$$

$$\text{Soit } I' = V_A Y = U' Y = 5,45 \times 0,033 = \boxed{0,182 \text{ A}}$$

$$I'_1 = (E_1 - U') Y_1 = \boxed{0,454 \text{ A}}$$

$$I'_2 = -U' Y_2 = \boxed{-0,272 \text{ A}}$$

$$\text{Vérification } \Rightarrow I' = I'_1 + I'_2 \Rightarrow I' = 0,454 - 0,272 = 0,182 \text{ A}$$