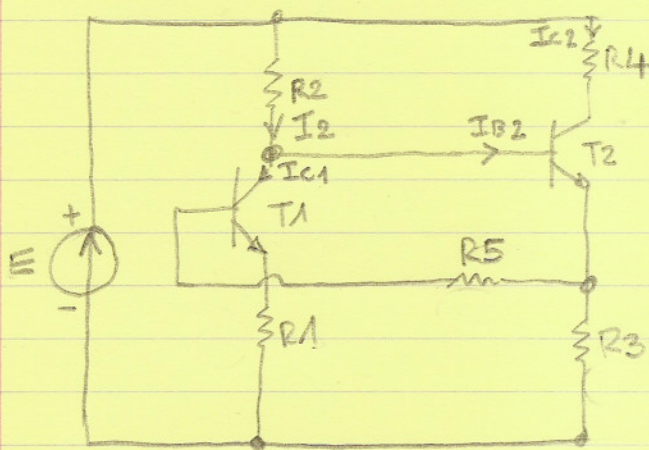


# Polarisation de transistors



- $E = 12V$
- $\beta = 100$
- $V_{BE} = 0,6V$
- $R_1 = 1K\Omega$
- $R_2 = 8,2K\Omega$
- $R_3 = 3,3K\Omega$
- $R_4 = 4,7K\Omega$
- $R_5 = 180K\Omega$


→ Calculer les coordonnées du point de repos de T1 et T2

$$\begin{cases} I_{C2} = \beta I_{B2} \\ I_{B2} = I_2 - I_{C1} \\ I_{C1} = \beta I_{B1} \end{cases} \Rightarrow I_{C2} = \beta(I_2 - \beta I_{B1})$$

Calcul de  $I_2$  et  $I_{B1}$


$$V_{BE1} + (\beta+1)R_1 I_{B1} = -R_5 I_{B1} + R_3 [( \beta+1) I_{C2} - I_{B1}]$$
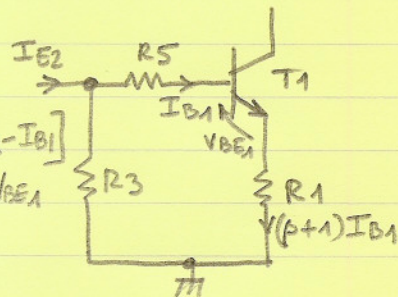
$$I_{B1} [(\beta+1)R_1 + R_5 + R_3] = R_3 \frac{\beta+1}{\beta} I_{C2} - V_{BE1}$$



on pose:  $R = (\beta+1)R_1 + R_5 + R_3$
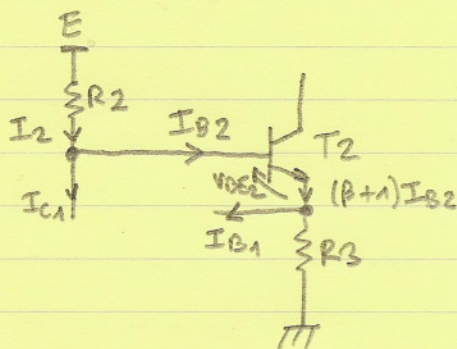
$$\Rightarrow I_{B1} = \frac{\beta+1}{\beta} \cdot \frac{R_3}{R} \cdot I_{C2} - \frac{V_{BE1}}{R}$$



$$E = R_2 I_2 + V_{BE2} + R_3 \left( \frac{\beta+1}{\beta} I_{C2} - I_{B1} \right)$$

$$\Rightarrow R_2 I_2 = E - V_{BE2} - \frac{\beta+1}{\beta} R_3 I_{C2} + \frac{R_3 (\beta+1)}{R \cdot \beta} I_{C2} - \frac{R_3 V_{BE1}}{R}$$

$$\text{Si on } I_2 = \frac{E - V_{BE2}}{R_2} - \frac{R_3 V_{BE1}}{R R_2} + \frac{\beta+1}{\beta} \cdot \frac{R_3}{R_2} \left( \frac{R_3}{R} - 1 \right) I_{C2}$$

$$\text{donc } I_{C2} = \beta \frac{\frac{E - V_{BE2}}{R_2} + \frac{V_{BE1}}{R} \left( \beta - \frac{R_3}{R_2} \right)}{1 + (\beta+1) \frac{R_3}{R_2} \left( 1 - \frac{R_3}{R} + \beta \frac{R_2}{R} \right)}$$

avec  $R = (\beta+1)R_1 + R_5 + R_3$

Application numérique :

on prend  $\beta \gg 1$   $\frac{R_3}{R} = 0,402 \ll \beta \Rightarrow R \approx \beta R_1 + R_5 + R_3 = 283,3K\Omega$

$$I_{C2} \approx \beta \frac{\frac{E - V_{BE2}}{R_2} + \frac{V_{BE1}}{R} \cdot \beta}{1 + \beta \frac{R_3}{R_2} \left( 1 + \beta \frac{R_2}{R} \right)} = \boxed{1,02 \text{ mA}} \text{ et } I_{B1} \approx \frac{R_3}{R} I_{C2} - \frac{V_{BE1}}{R} = \boxed{9,76 \mu\text{A}}$$

et  $I_{B2} = \boxed{10,2 \mu\text{A}}$

$I_{C1} = \boxed{976 \mu\text{A}}$