

The World Leader in High Performance Signal Processing Solutions



A Practical Guide to High-Speed Printed Circuit Board Layout

John Ardizzoni
Analog Devices

Dennis Falls
Avnet Electronics Marketing






Agenda

- ◆ **Overview**
- ◆ **Schematic**
- ◆ **Location, location, location**
- ◆ **Trust no one**
- ◆ **Power supply bypassing**
- ◆ **Parasitics**
- ◆ **Ground and power planes**
- ◆ **Packaging**
- ◆ **RF Signal routing and shielding**
- ◆ **Checking the layout**
- ◆ **Summary**



Overview

- ◆ **PCB layout is one of the last steps in the design process and often one of the most critical**
- ◆ **High-speed circuit performance is heavily dependant on layout**
- ◆ **A high-performance design can be rendered useless due to a poor or sloppy layout**
- ◆ **Today's presentation will help:**
 - **Improve the layout process**
 - **Ensure expected circuit performance is achieved**
 - **Reduce design time**
 - **Lower cost**
 - **Lower stress for you and the PCB designer**

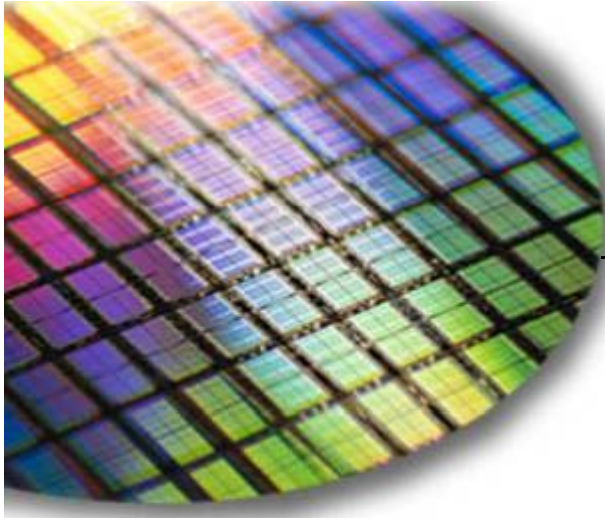

The World Leader in High Performance Signal Processing Solutions



Schematic

Schematic


- ◆ **The strength of any structure (including PCB's) is only as good as the foundation on which it built upon!**
- ◆ **A good layout starts with a good Schematic!**
- ◆ **Schematic flow and content**
- ◆ **Include as much information as you can**
- ◆ **What should you include?**




Items to Include on a Schematic

- ◆ **Notes**
- ◆ **Component tolerances and case sizes**
- ◆ **Part numbers (internal/external/alternative)**
- ◆ **Board stack up**
- ◆ **Tests or alignment procedures**
- ◆ **Power dissipation**
- ◆ **Controlled impedance and line matching**
- ◆ **Component de-rating**
- ◆ **Thermal requirements**
- ◆ **Keep outs**
- ◆ **Mechanical considerations**
- ◆ **Critical component placement**
- ◆ **Warning flags**
- ◆ **What ever else you can think of!**

Schematic

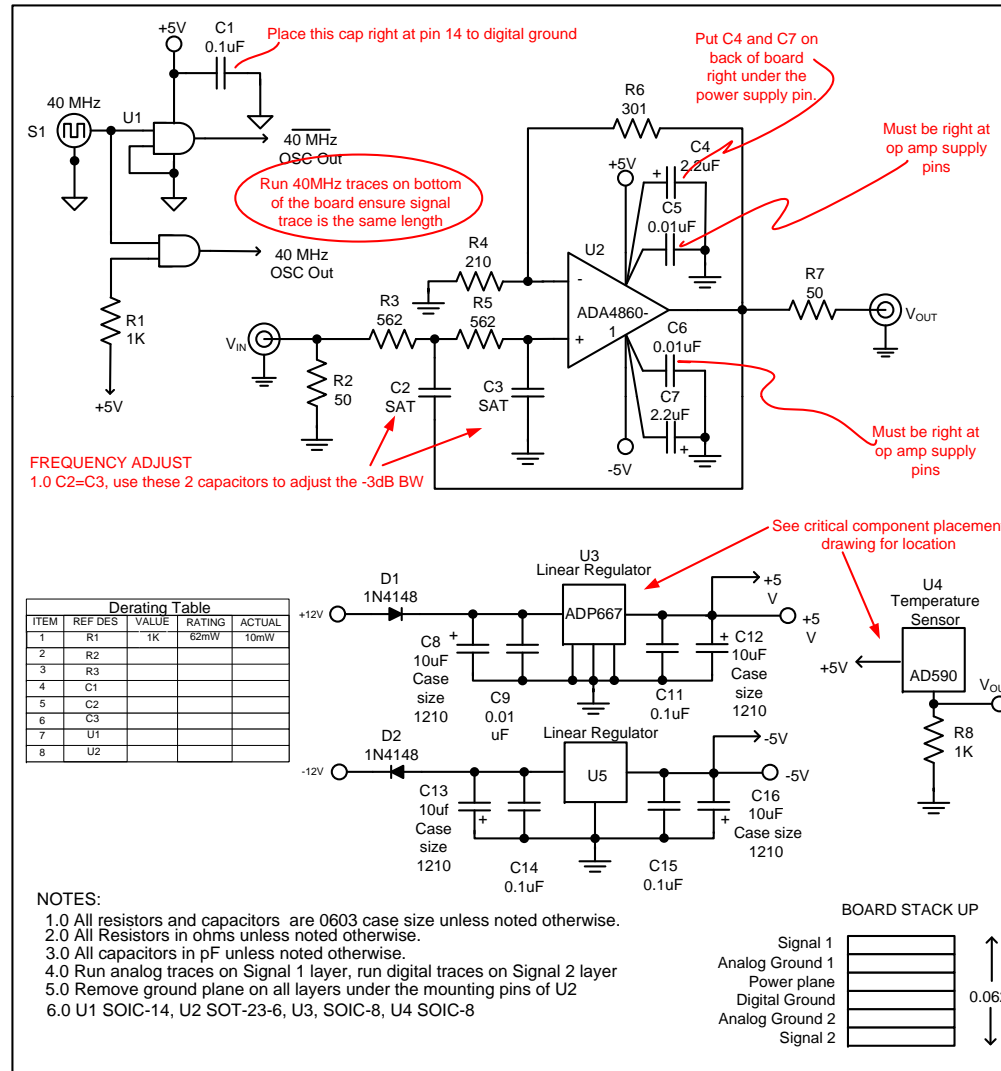

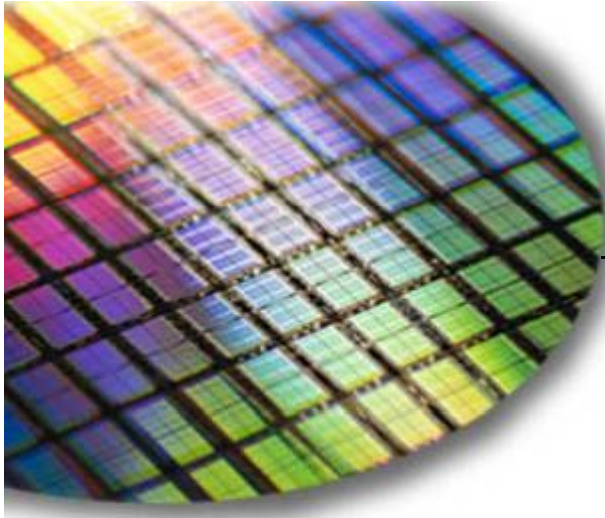


The World Leader in High Performance Signal Processing Solutions



Location, location, location!

Location, Location, Location

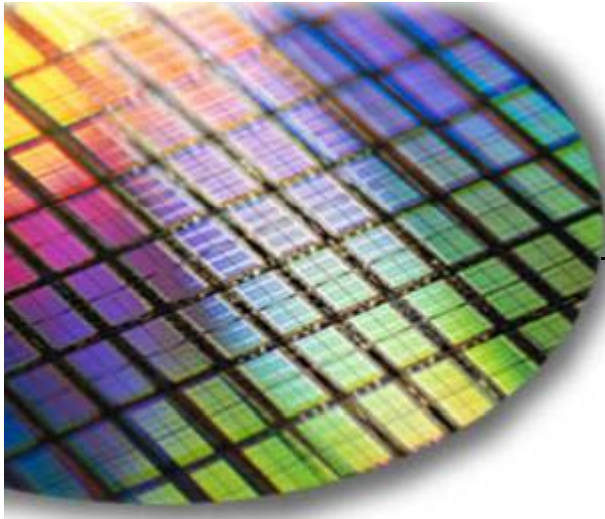- ◆ ***Just as in real estate location is everything!***
- ◆ ***Input/output and power connections are typically defined...Everything else is undefined***
 - ***Critical component placement***
 - ***Signal routing***
 - ***Circuit and component proximity***



The World Leader in High Performance Signal Processing Solutions




Trust No One




Trust No One

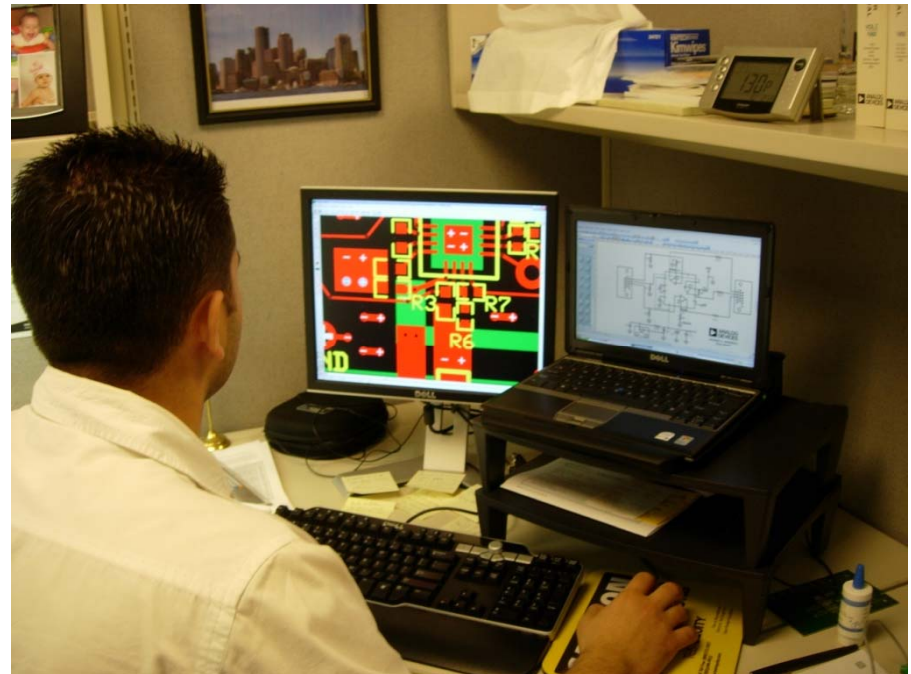- ◆ If you're doing your own layout, that's one thing.
- ◆ If you're not




Trust No One

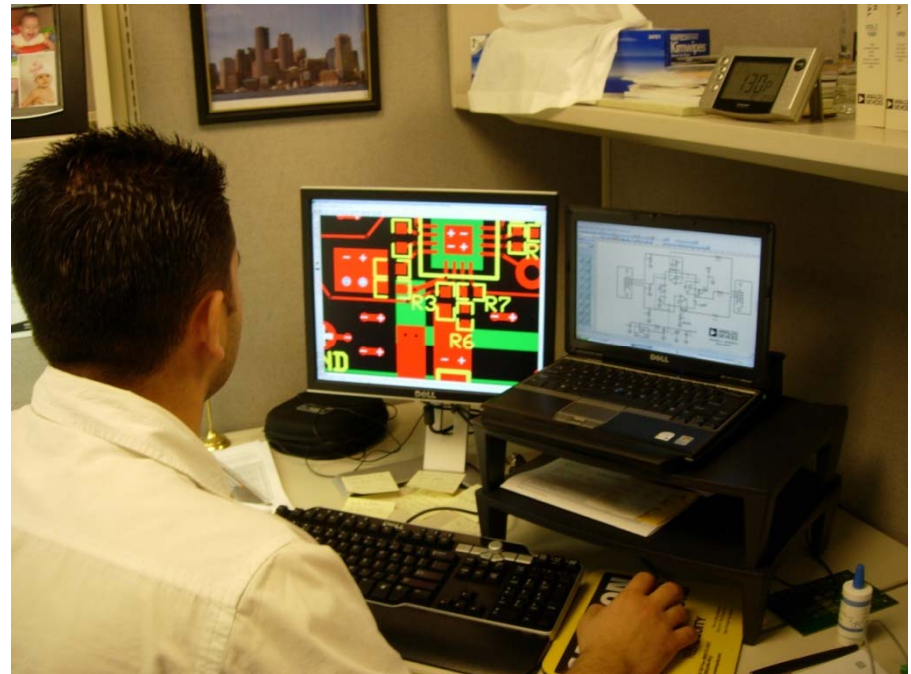- ◆ If you're doing your own layout, that's one thing.
- ◆ If you're not
 - Don't assume the CAD group is going to read your mind and get it right!




Trust No One

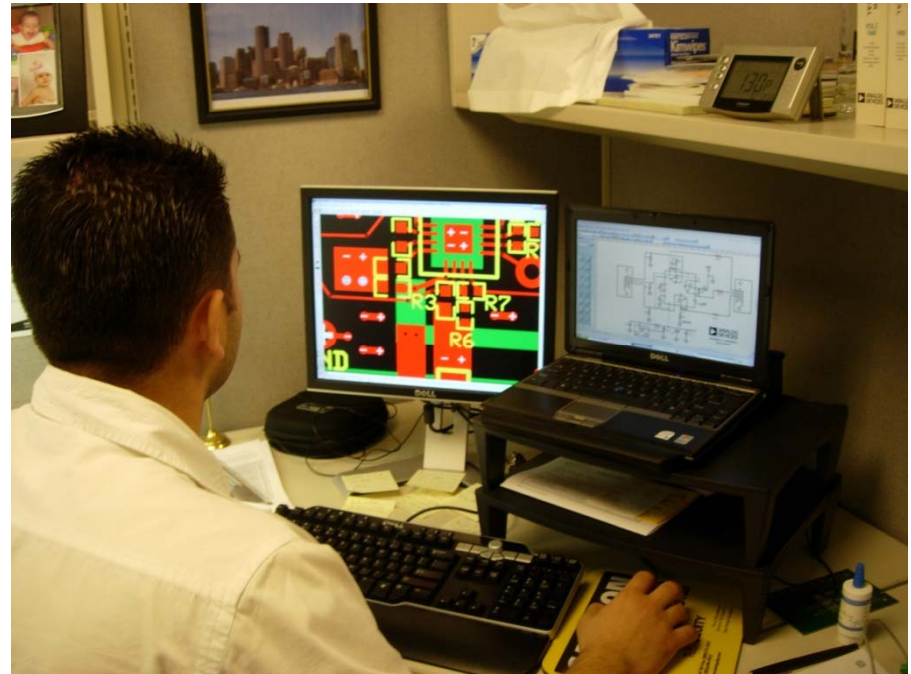- ◆ If you're doing your own layout, that's one thing.
- ◆ If you're not
 - Don't assume the CAD group is going to read your mind and get it right!
 - In the end you're responsible for making it work!




Trust No One

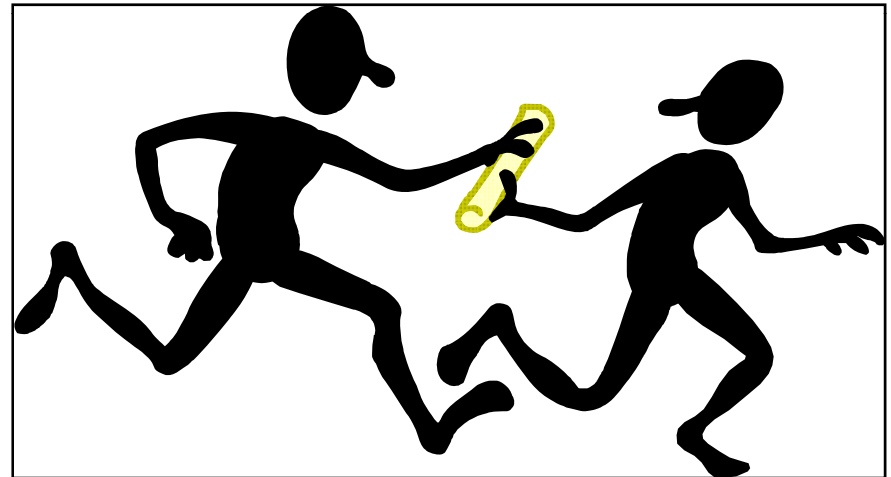- ◆ If you're doing your own layout, that's one thing.
- ◆ If you're not
 - Don't assume the CAD group is going to read your mind and get it right!
 - You're responsible for making it work!
- ◆ When working with the CAD Group



Trust No One

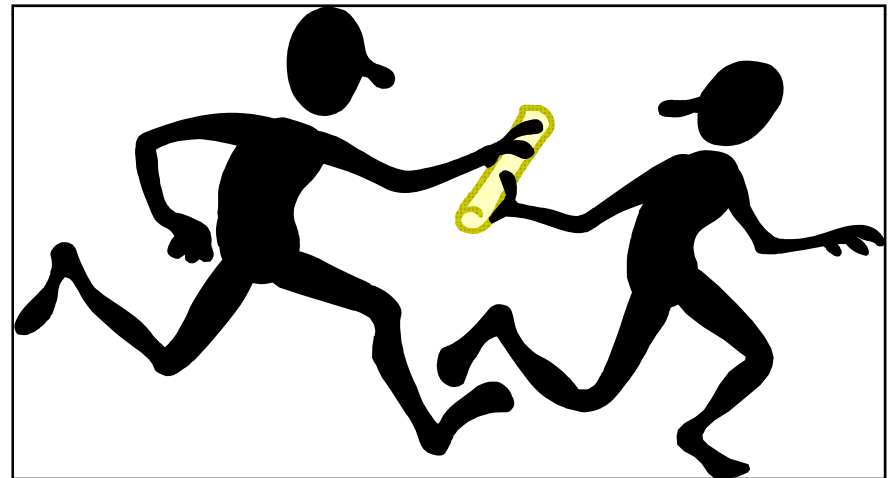- ◆ If you're doing your own layout, that's one thing.
- ◆ If you're not
 - Don't assume the CAD group is going to read your mind and get it right!
 - You're responsible for making it work!
- ◆ When working with the CAD Group
 - Make sure you and the designer are on the same page



Trust No One

- ◆ **If you're doing your own layout, that's one thing.**
- ◆ **If you're not**
 - **Don't assume the CAD group is going to read your mind and get it right!**
 - **You're responsible for making it work!**
- ◆ **When working with the CAD Group**
 - **Make sure you and the designer are on the same page**
 - **Brief circuit explanation**



Trust No One

- ◆ **If you're doing your own layout, that's one thing.**
- ◆ **If you're not**
 - Don't assume the CAD group is going to read your mind and get it right!
 - You're responsible for making it work!
- ◆ **When working with the CAD Group**
 - Make sure you and the designer are on the same page
 - Brief circuit explanation
 - Critical component placement




Trust No One

- ◆ **If you're doing your own layout, that's one thing.**
- ◆ **If you're not**
 - Don't assume the CAD group is going to read your mind and get it right!
 - You're responsible for making it work!
- ◆ **When working with the CAD Group**
 - Make sure you and the designer are on the same page
 - Brief circuit explanation
 - Critical component placement
 - Input/Output connections




Trust No One


- ◆ **If you're doing your own layout, that's one thing.**
- ◆ **If you're not**
 - Don't assume the CAD group is going to read your mind and get it right!
 - You're responsible for making it work!
- ◆ **When working with the CAD Group**
 - Make sure you and the designer are on the same page
 - Brief circuit explanation
 - Critical component placement
 - Input/Output connections
 - Board outline drawing and stack up

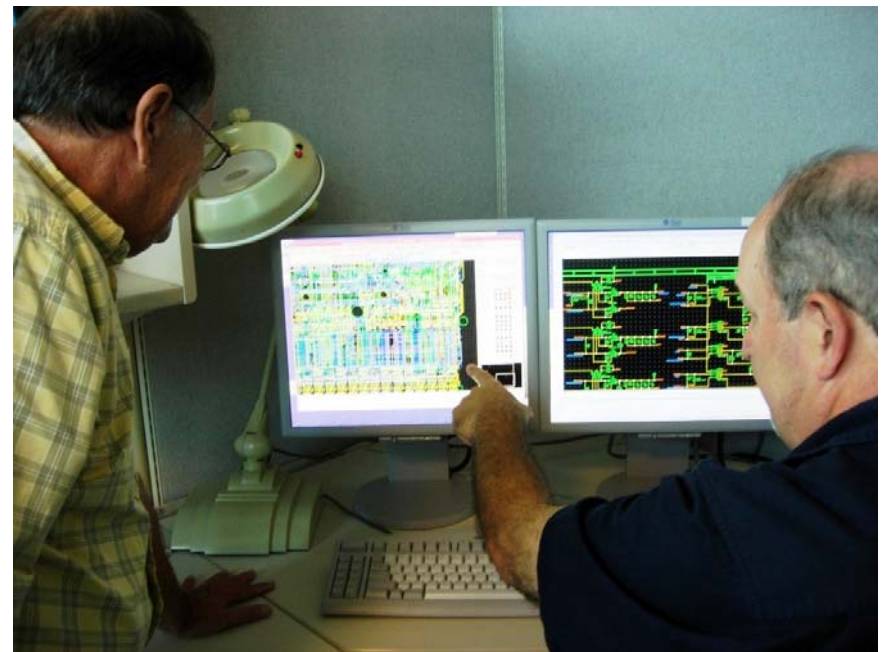

Trust No One

- ◆ **If you're doing your own layout, that's one thing.**
- ◆ **If you're not**
 - **Don't assume the CAD group is going to read your mind and get it right!**
 - **You're responsible for making it work!**
- ◆ **When working with the CAD Group**
 - **Make sure you and the designer are on the same page**
 - **Brief circuit explanation**
 - **Critical component placement**
 - **Input/Output connections**
 - **Board outline, stack up**
 - **Tell them to call you if they have a question!**

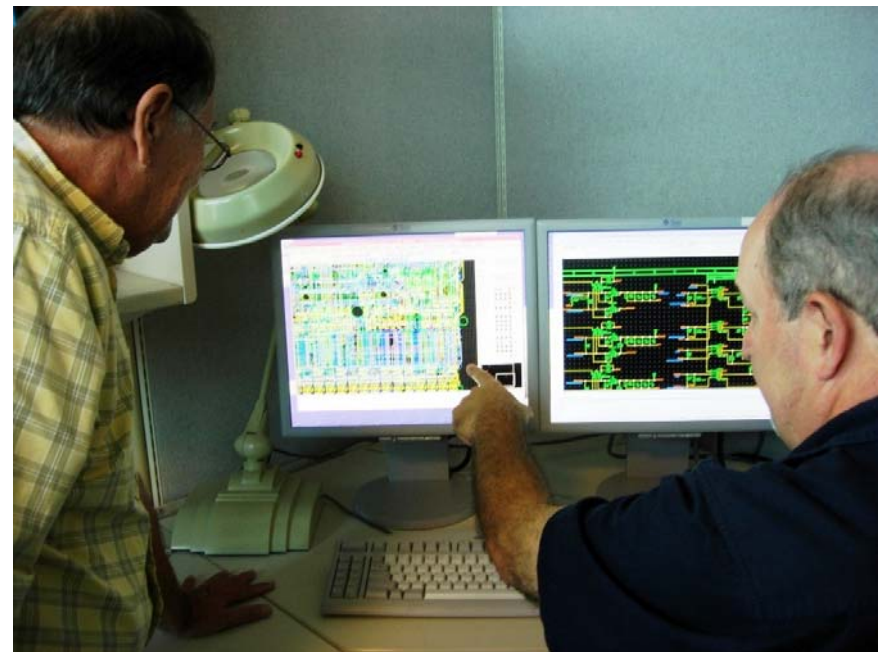

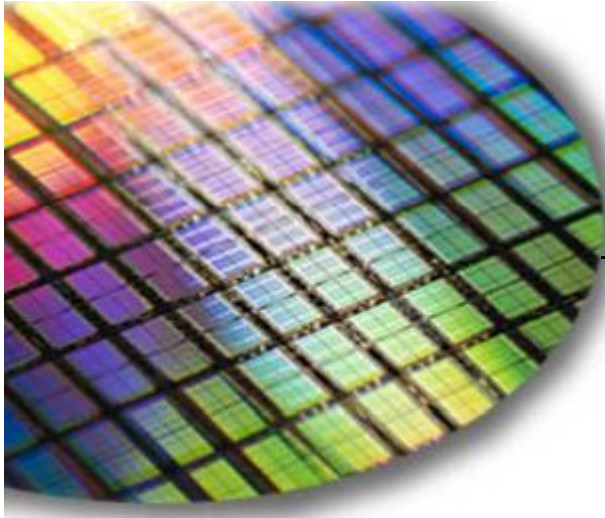


The World Leader in High Performance Signal Processing Solutions



Power Supply Bypassing


Power Supply Bypassing

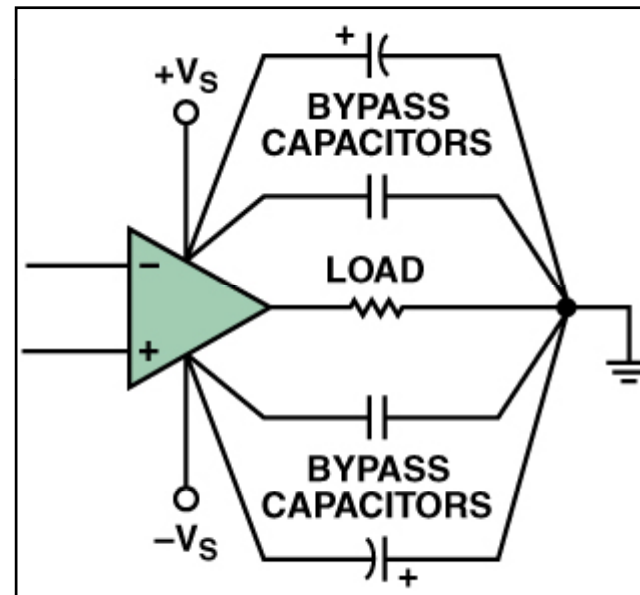- ◆ **Bypassing is essential to high speed circuit performance**




Power Supply Bypassing

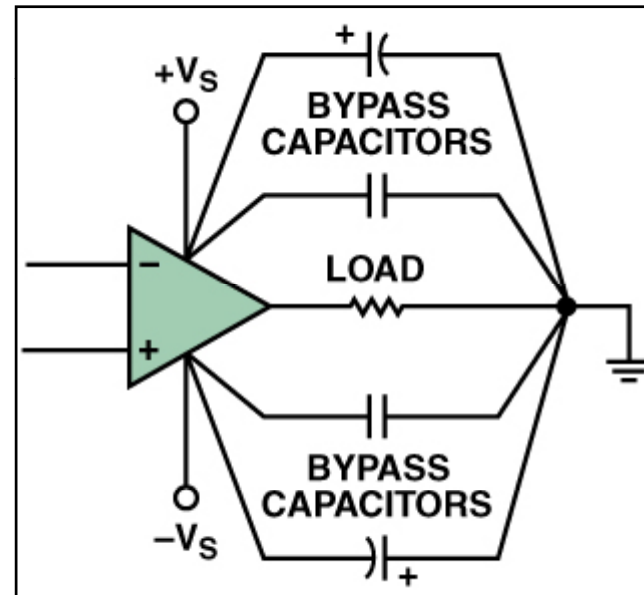- ◆ Bypassing is essential to high speed circuit performance
- ◆ Capacitors right at power supply pins




Power Supply Bypassing

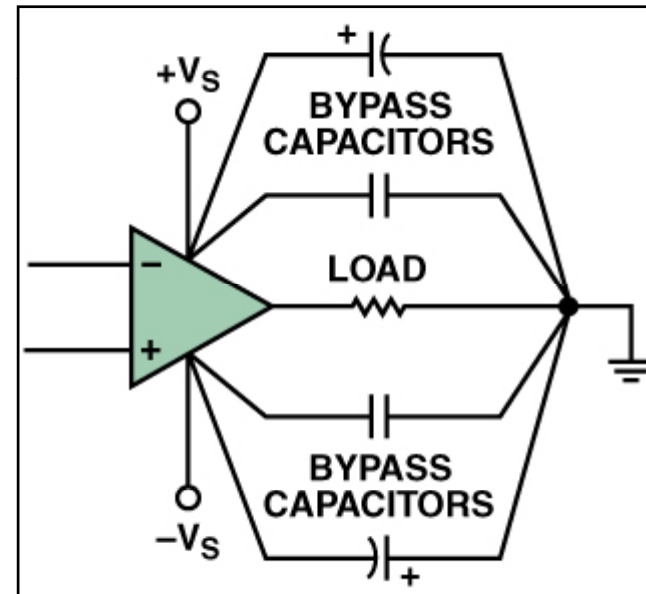- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - **Capacitors provide low AC impedance to ground**
 - **Provide local charge storage for fast rising/falling edges**



Power Supply Bypassing

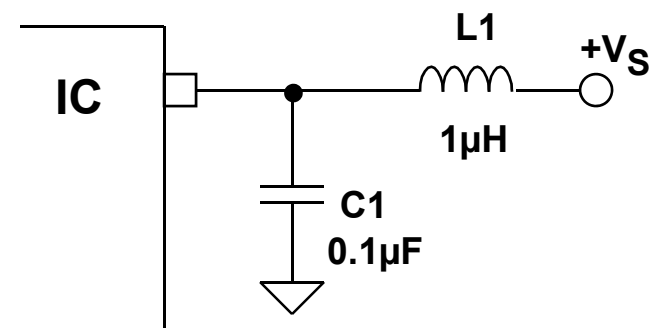- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - **Capacitors provide low AC impedance to ground**
 - **Provide local charge storage for fast rising/falling edges**
- ◆ **Keep trace lengths short**




EQUIVALENT DECOUPLED POWER LINE CIRCUIT RESONATES AT:

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$f = 500\text{kHz}$$

Power Supply Bypassing

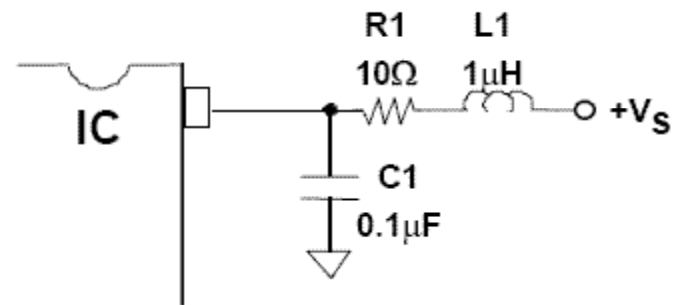
- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - **Capacitors provide low AC impedance to ground**
 - **Provide local charge storage for fast rising/falling edges**
- ◆ **Keep trace lengths short**



**SMALL SERIES RESISTANCE
CLOSE TO IC REDUCES Q**


Power Supply Bypassing

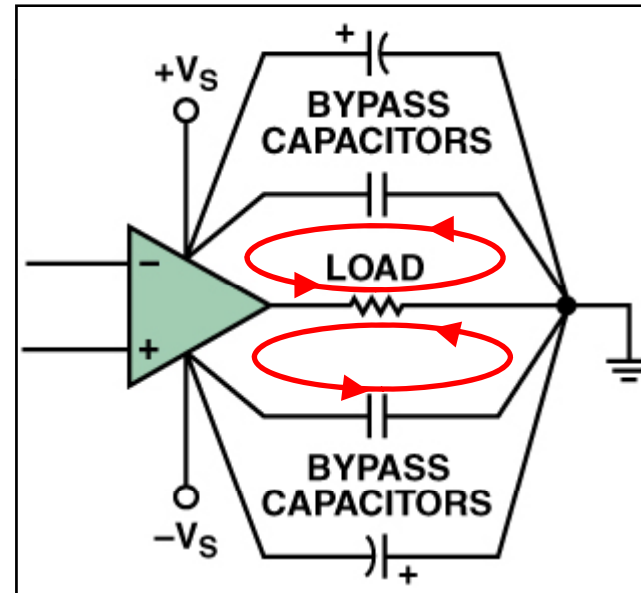- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - Capacitors provide low AC impedance to ground
 - Provide local charge storage for fast rising/falling edges
- ◆ **Keep trace lengths short**
- ◆ **Close to load return**
 - Helps minimize transient currents in the ground plane




Power Supply Bypassing

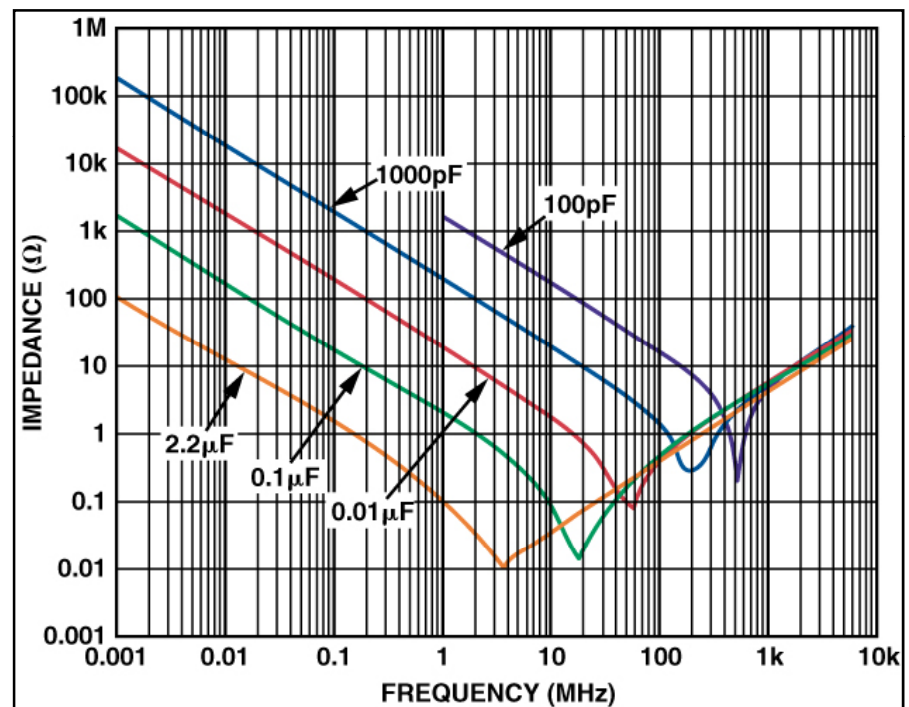- ◆ Bypassing is essential to high speed circuit performance
- ◆ Capacitors right at power supply pins
 - Capacitors provide low AC impedance to ground
 - Provide local charge storage for fast rising/falling edges
- ◆ Keep trace lengths short
- ◆ Close to load return
 - Helps minimize transient currents in the ground plane
- ◆ Values
 - Individual circuit performance




Power Supply Bypassing

- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - Capacitors provide low AC impedance to ground
 - Provide local charge storage for fast rising/falling edges
- ◆ **Keep trace lengths short**
- ◆ **Close to load return**
 - Helps minimize transient currents in the ground plane
- ◆ **Values**
 - Individual circuit performance
 - Maintains low AC impedance

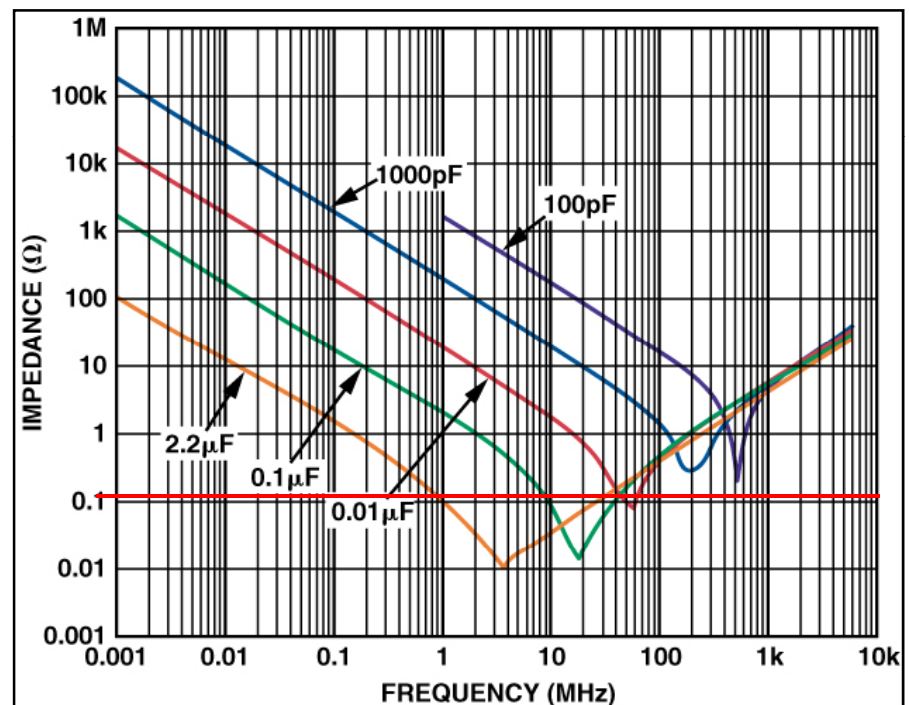


Power Supply Bypassing


- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - Capacitors provide low AC impedance to ground
 - Provide local charge storage for fast rising/falling edges
- ◆ **Keep trace lengths short**
- ◆ **Close to load return**
 - Helps minimize transient currents in the ground plane
- ◆ **Values**
 - Individual circuit performance
 - Maintains low AC impedance
 - Multiple resonances

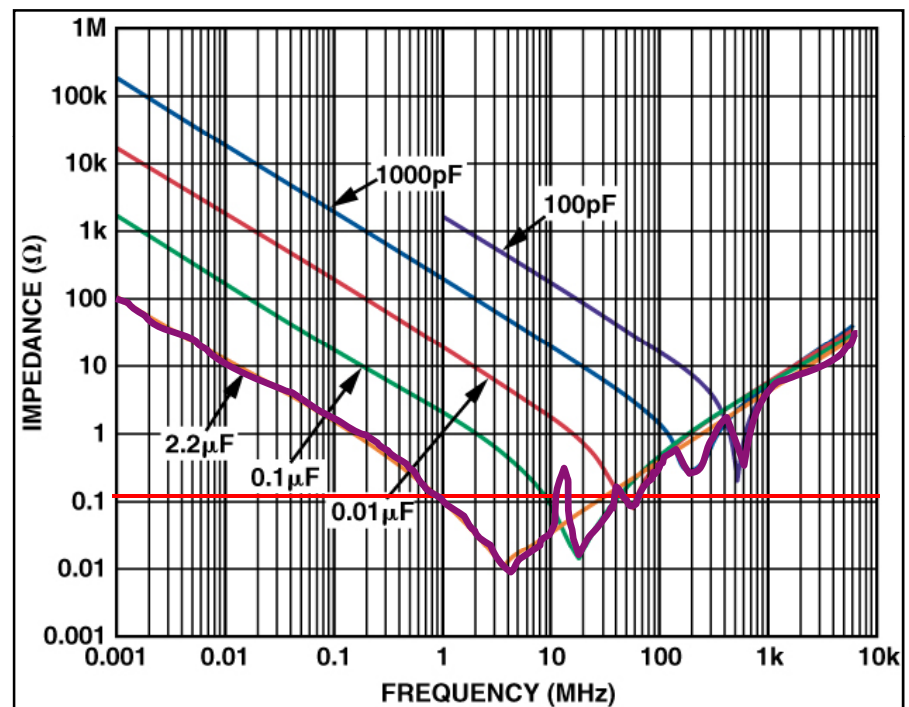

Power Supply Bypassing

- ◆ **Bypassing is essential to high speed circuit performance**
- ◆ **Capacitors right at power supply pins**
 - Capacitors provide low impedance AC return
 - Provide local charge storage for fast rising/falling edges
- ◆ **Keep trace lengths short**
- ◆ **Close to load return**
 - Helps minimize transient currents in the ground plane
- ◆ **Values**
 - Individual circuit performance
 - Maintains low AC impedance
 - Multiple resonances
- ◆ **Ferrite beads**

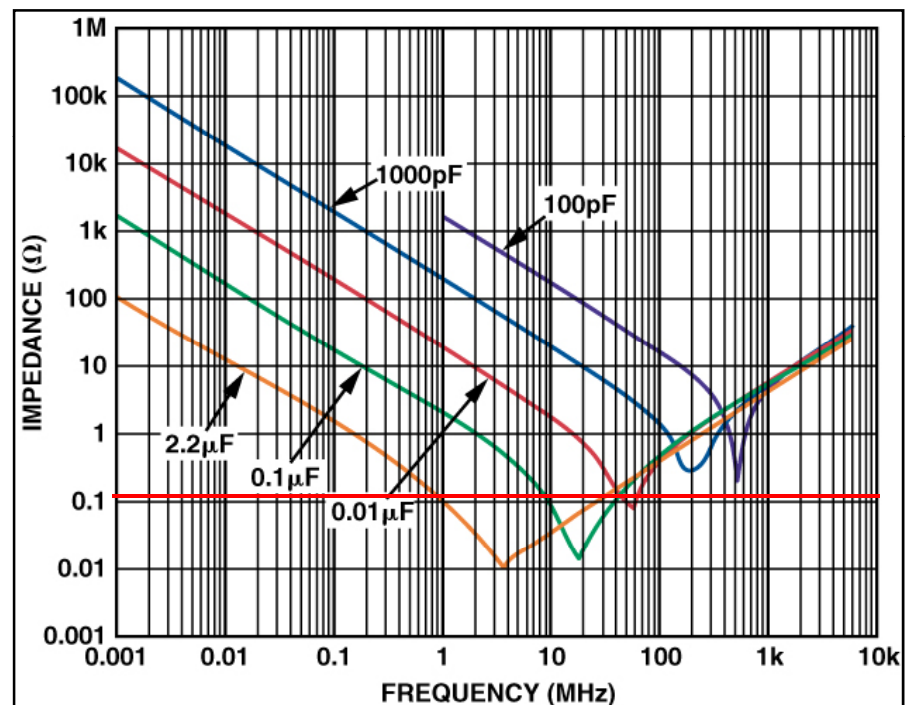

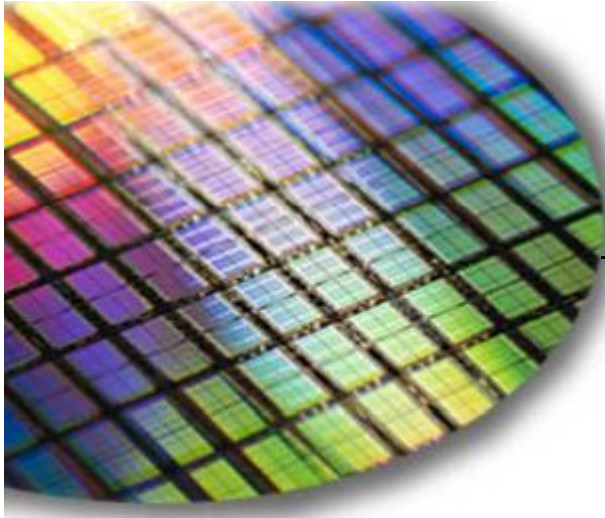

The World Leader in High Performance Signal Processing Solutions




Parasitics

Parasitics


- ◆ **Parasite – An organism that grows, feeds, and is sheltered on or in a different organism while contributing nothing to the survival of its host.**
- ◆ **Parasitics in high-speed PCB's, can destroy circuit performance!**

Parasitics

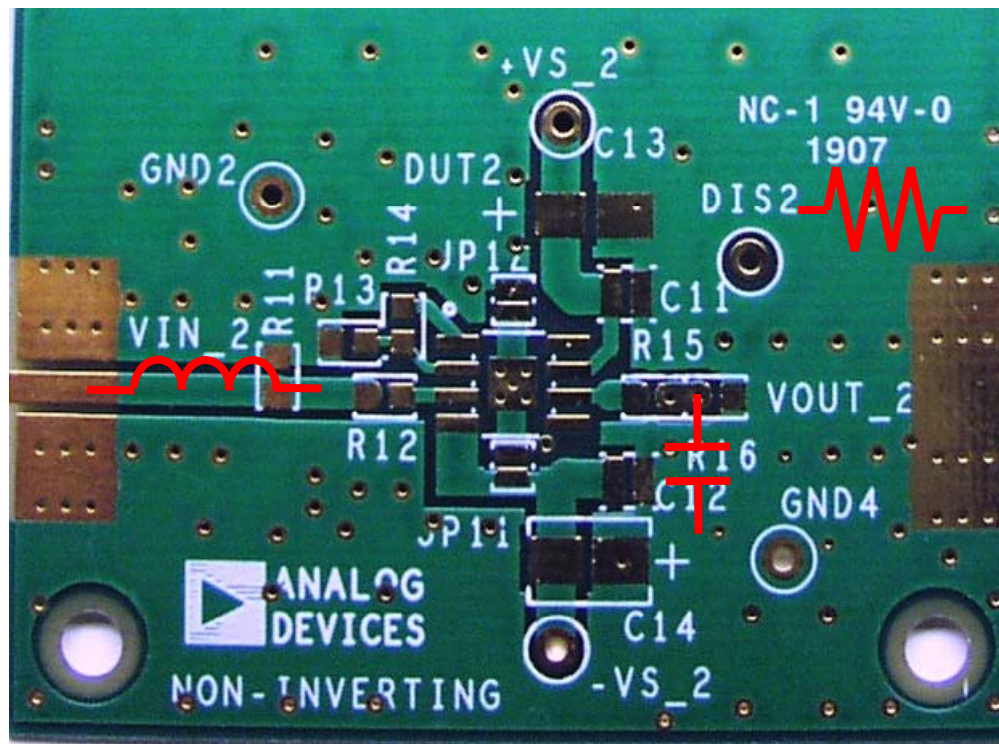
- ◆ PCB parasites take the form of undesired capacitors, inductors and resistors embedded within the PCB
- ◆ Parasitics are extremely difficult to remove from a PCB
- ◆ Prevention is the best method to minimize parasitics



Trace/Pad Capacitance

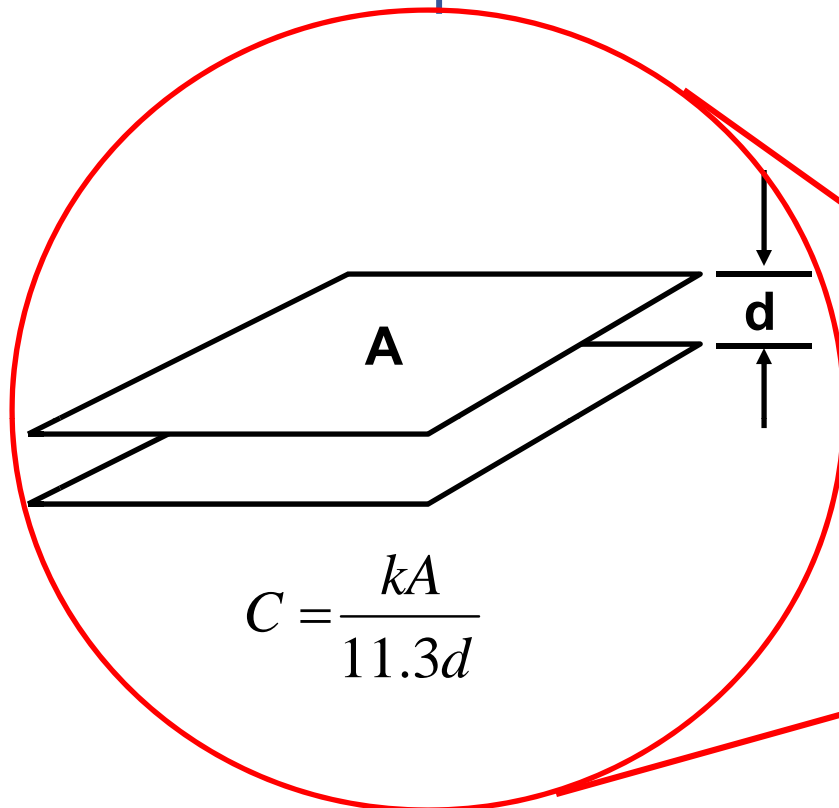

$$C = \frac{kA}{11.3d}$$

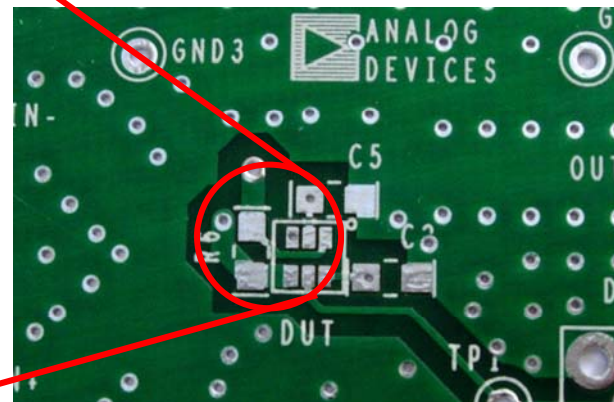


K = relative dielectric constant

A = area in cm²

d = spacing between plates in cm

Trace/Pad Capacitance

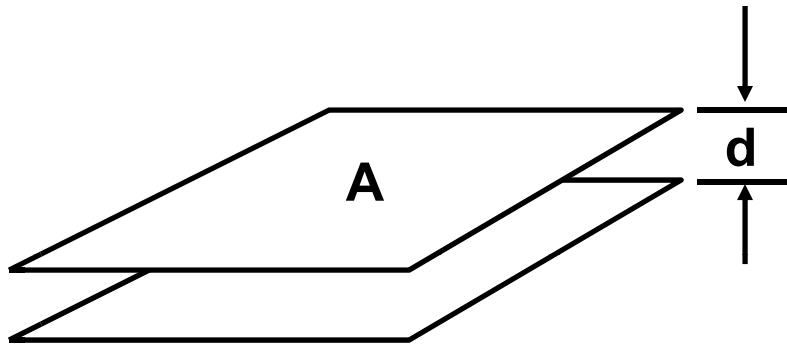

$$C = \frac{kA}{11.3d}$$

K = relative dielectric constant

A = area in cm²

d = spacing between plates in cm

Example: Pad of SOIC

L = 0.2cm W = 0.063cm


K = 4.7

A = 0.0126cm²

d = 0.073cm

C = 0.072pF

Trace/Pad Capacitance

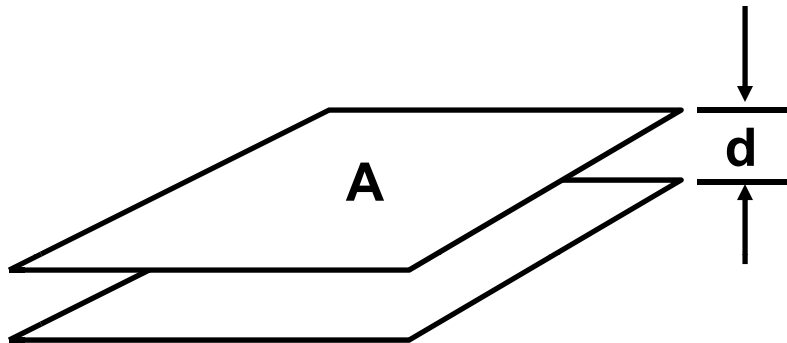

$$C = \frac{kA}{11.3d}$$

K = relative dielectric constant

A = area in cm²

d = spacing between plates in cm

Example: Pad of SOIC

L = 0.2cm W = 0.063cm

K = 4.7

A = 0.0126cm²


d = 0.073cm

C = 0.072pF


Reduce Capacitance

- 1) Increase board thickness or layers
- 2) Reduce trace/pad area
- 3) Remove ground plane

Approximate Trace Inductance

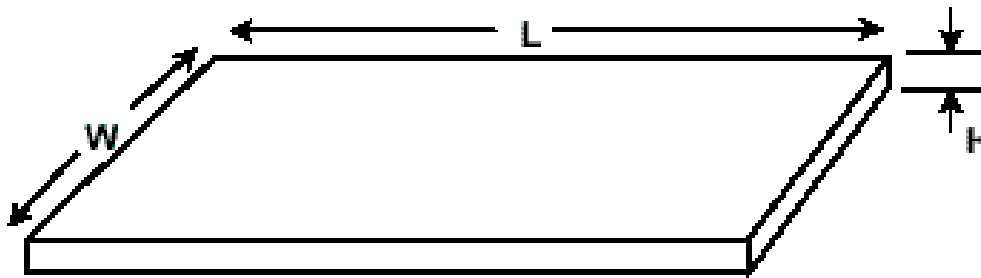

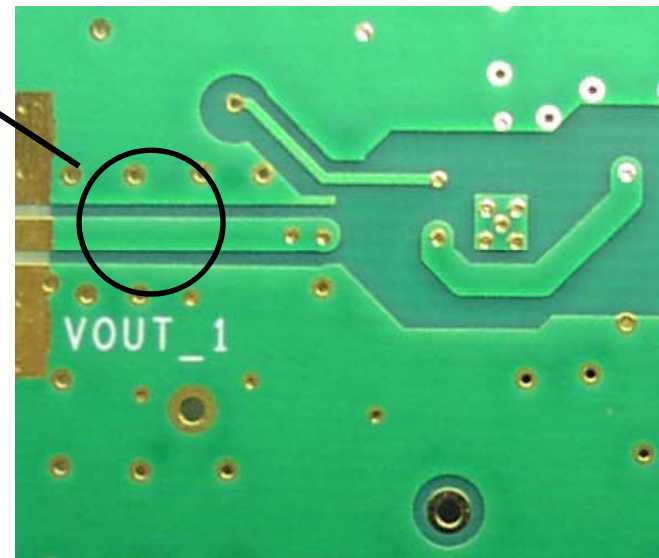
$$\text{STRIP INDUCTANCE} = 0.0002L \left[\ln \left(\frac{2L}{W+H} \right) + 0.2235 \left(\frac{W+H}{L} \right) + 0.5 \right] \mu\text{H}$$



All dimensions are in mm

Approximate Trace Inductance

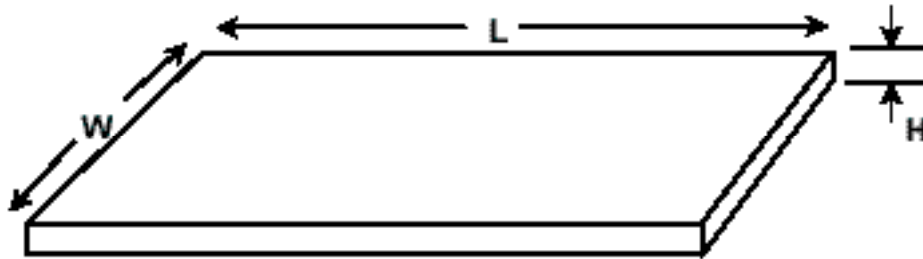

$$\text{STRIP INDUCTANCE} = 0.0002L \left[\ln \left(\frac{2L}{W+H} \right) + 0.2235 \left(\frac{W+H}{L} \right) + 0.5 \right] \mu\text{H}$$

All dimensions are in mm

Example

$$L = 25.4\text{mm}$$


$$W = .25\text{mm}$$

$$H = .035\text{mm (1oz copper)}$$

$$\text{Strip Inductance} = 28.8\text{nH}$$

At 10MHz $Z_L = 1.86 \Omega$ a 3.6% error
in a 50Ω system

Approximate Trace Inductance

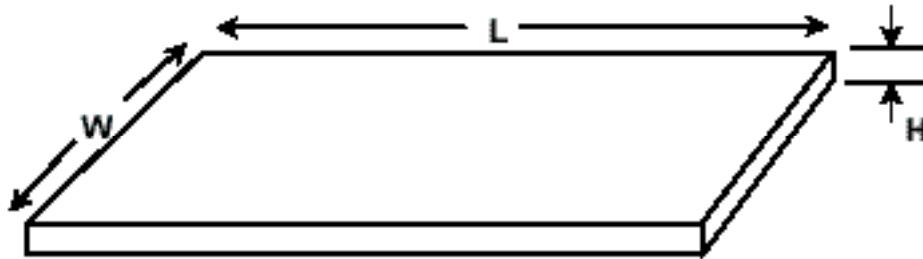

$$\text{STRIP INDUCTANCE} = 0.0002L \left[\ln \left(\frac{2L}{W+H} \right) + 0.2235 \left(\frac{W+H}{L} \right) + 0.5 \right] \mu\text{H}$$

All dimensions are in mm

Example

$$L = 2.54\text{cm} = 25.4\text{mm}$$

$$W = .25\text{mm}$$

$$H = .035\text{mm (1oz copper)}$$

$$\text{Strip Inductance} = 28.8\text{nH}$$

At 10MHz $Z_L = 1.86 \Omega$ a 3.6% error
in a 50Ω system

Minimize Inductance

- 1) Use Ground plane
- 2) Keep length short (halving the length reduces inductance by 44%)
- 3) Doubling width only reduces inductance by 11%

Via Parasitics

Via Inductance

$$L \approx 2h \left[\ln \left(\frac{4h}{d} \right) + 1 \right] nH$$

L = inductance of the via, nH

H = length of via, cm

D = diameter of via, cm

Given:

$H = 0.157$ cm thick board,

$D = 0.041$ cm

$$L \sim 1.2nH$$

Via Capacitance

$$C \approx \frac{0.55 \epsilon_r T D_1}{D_2 - D_1} \text{ pF}$$

D_2 = diameter of clearance hole in the ground plane, cm

D_1 = diameter of pad surrounding via, cm

T = thickness of printed circuit board, cm

ϵ_r = relative electric permeability of circuit board material

C = parasitic via capacitance, pF

Given:


$T = 0.157$ cm,

$D_1 = 0.071$ cm


$D_2 = 0.127$

$$C \sim 0.51pF$$

Via Cross Section

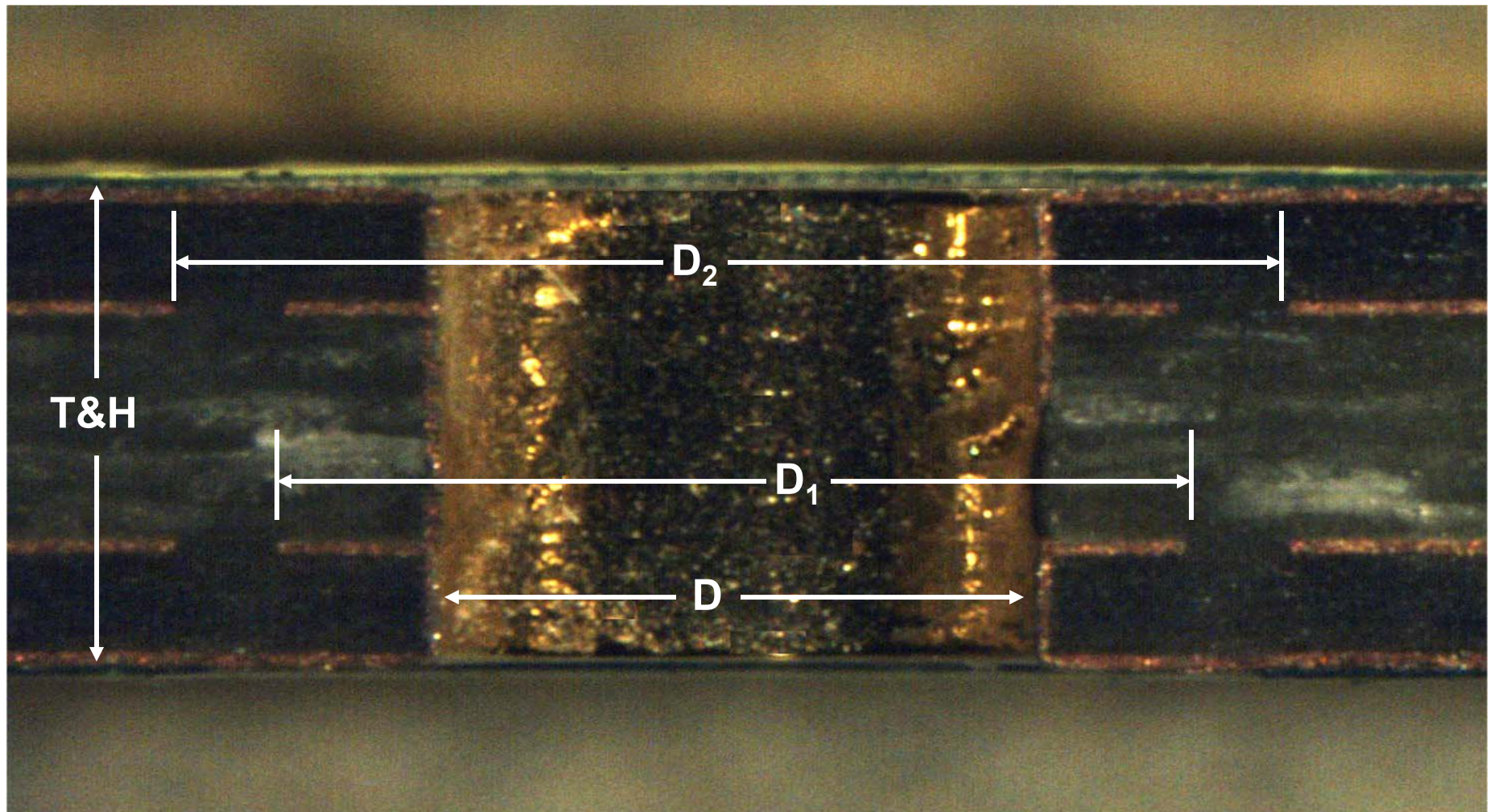

Capacitor Parasitic Model

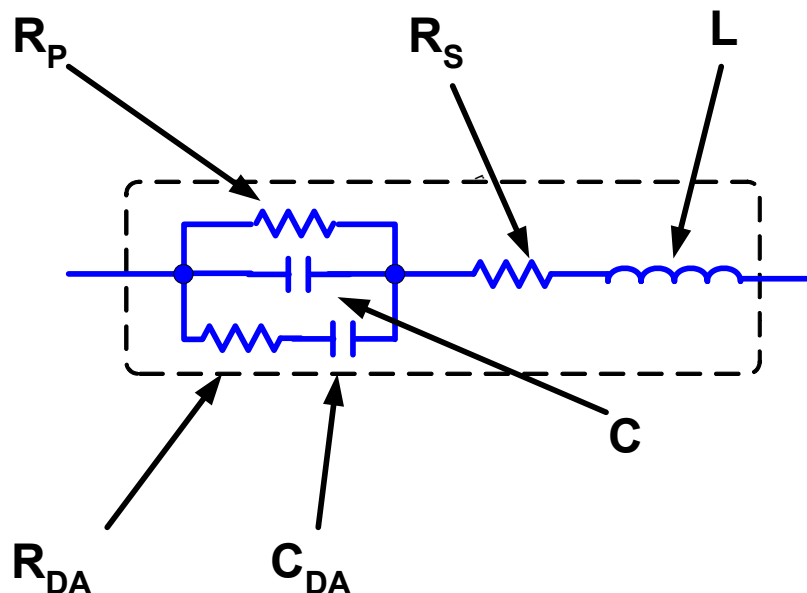

C = Capacitor

R_p = insulation resistance


R_s = equivalent series resistance (ESR)

L = series inductance of the leads and plates

R_{DA} = dielectric absorption

C_{DA} = dielectric absorption

Resistor Parasitic Model

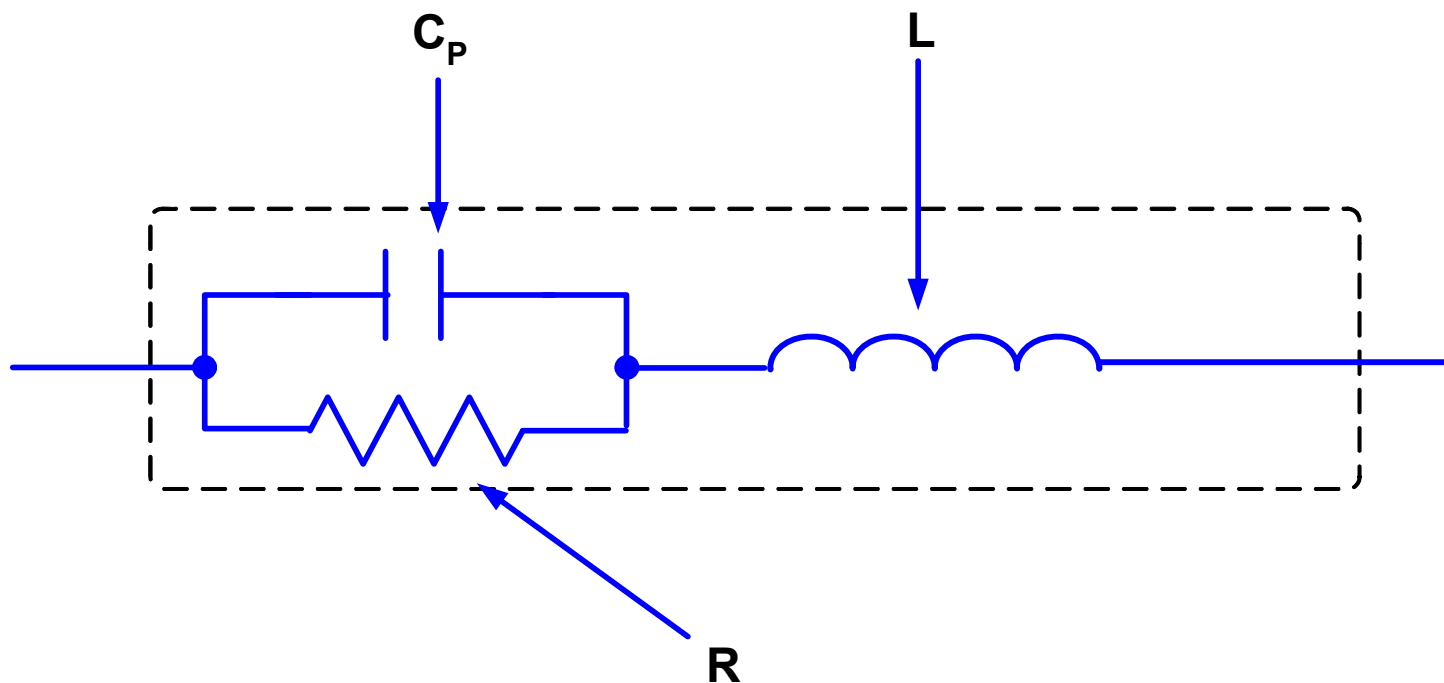


R = Resistor


C_p = Parallel capacitance

L = equivalent series inductance (ESL)

Low Frequency Op Amp Schematic

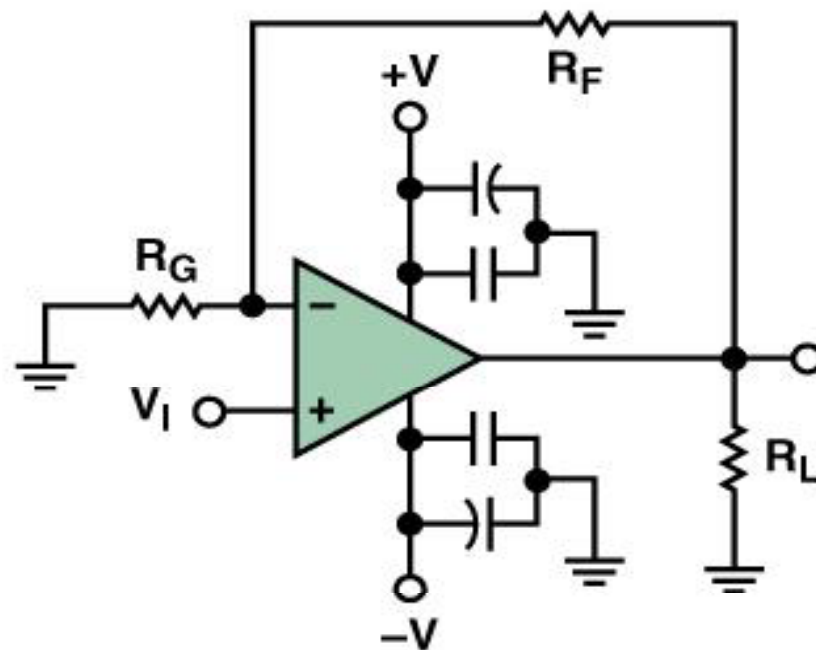


High Speed Op Amp Schematic

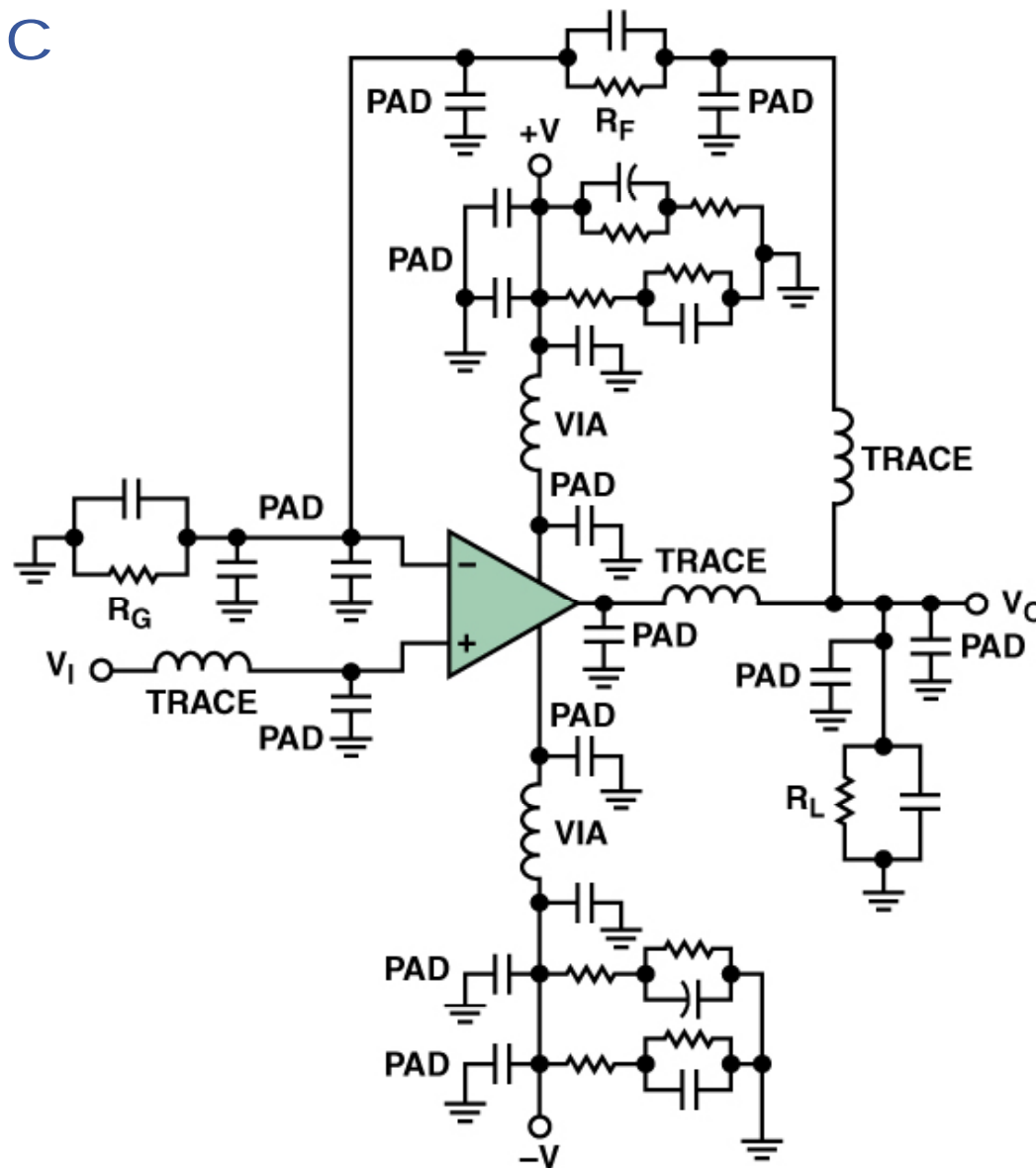

High Speed Op Amp Schematic

Parasitic Capacitance

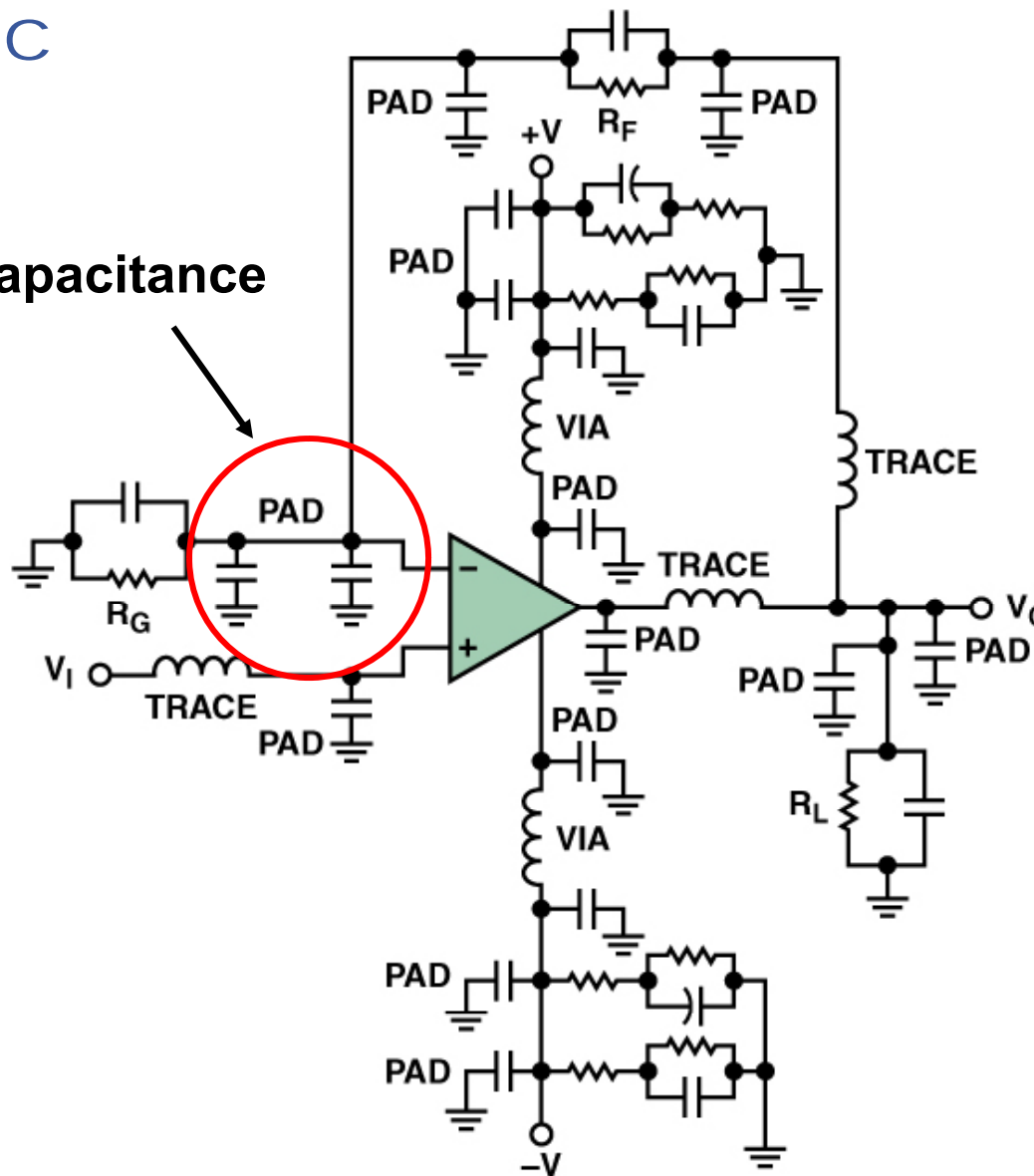

[All Product Categories >](#)
[Design Center >](#)
[All Solutions/
Applications >](#)
[Buy Online >](#)

NI Multisim Analog Devices Edition



*Free downloadable SPICE simulator
for Analog Devices component evaluation.*

With NI Multisim™ Analog Devices® Edition, ADI and the NI Electronics Workbench Group equip circuit board designers with a free, downloadable version of NI Multisim tailored for evaluating ADI components. Avoid costly and time consuming prototyping work by using this easy-to-use interactive SPICE simulator.

With the NI Multisim Analog Devices Edition, engineers can:

- Build simulated component evaluation circuits to quickly assess behavior of over 800 Analog Devices operational amplifiers, switches and voltage references
- Examine the unit under test in the intended circuit topology with up to 25 components
- Use built-in instruments and analyses including oscilloscopes and worst-case analysis
- Swap components easily to pinpoint best design options
- Link to the Analog Devices Design Center for more online evaluation tools
- Instantly access product pages and datasheets of each Analog Devices component
- Upgrade to a full edition of NI Multisim to complete designs and transfer to board layout with NI Ultiboard


Start building circuits now: Download the [NI Multisim Analog Devices Edition](#) (.exe, 183 MB)

Other Resources:


- Application Circuits: [Ready-built reference designs](#) (.zip, 2,913,219 bytes)
- [Upgrade to the NI Multisim Professional Edition](#)
- [Multisim Technical Support](#)

<http://www.analog.com/en/design-tools/dt-multisim-spice-program-download/design-center/index.html>


Stray Capacitance Simulation Schematic

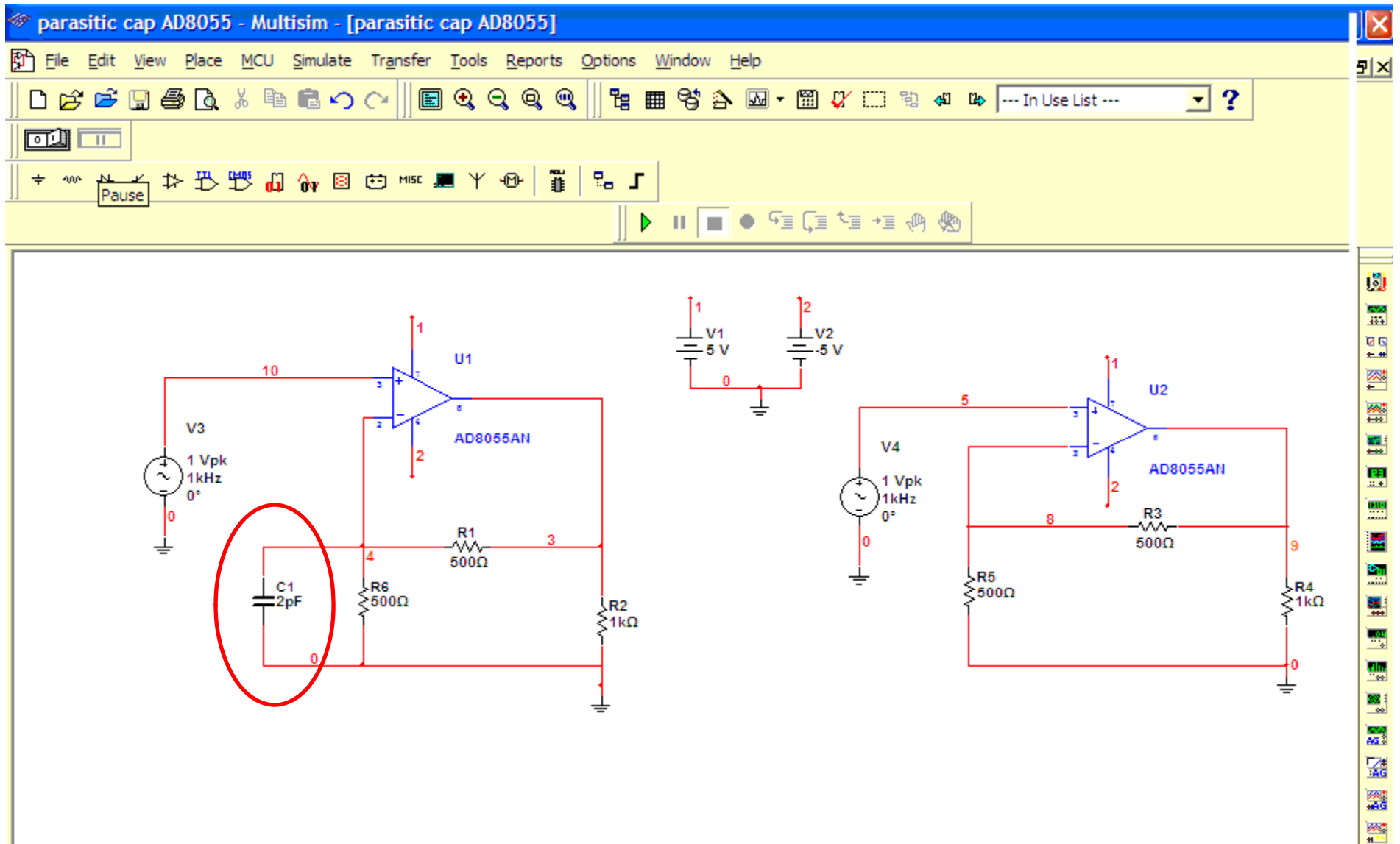

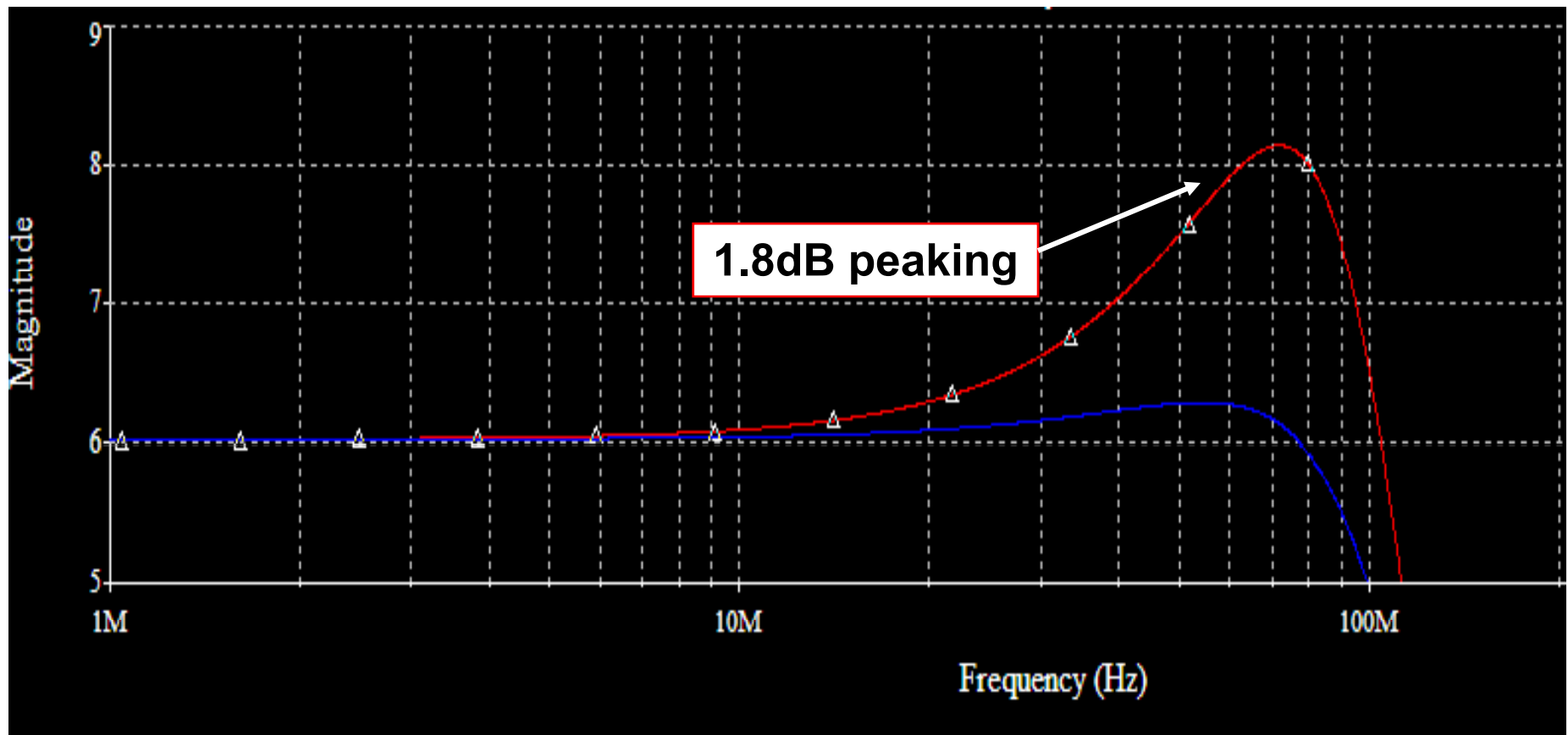Frequency Response with 2pF Stray Capacitance




Stray Inductance

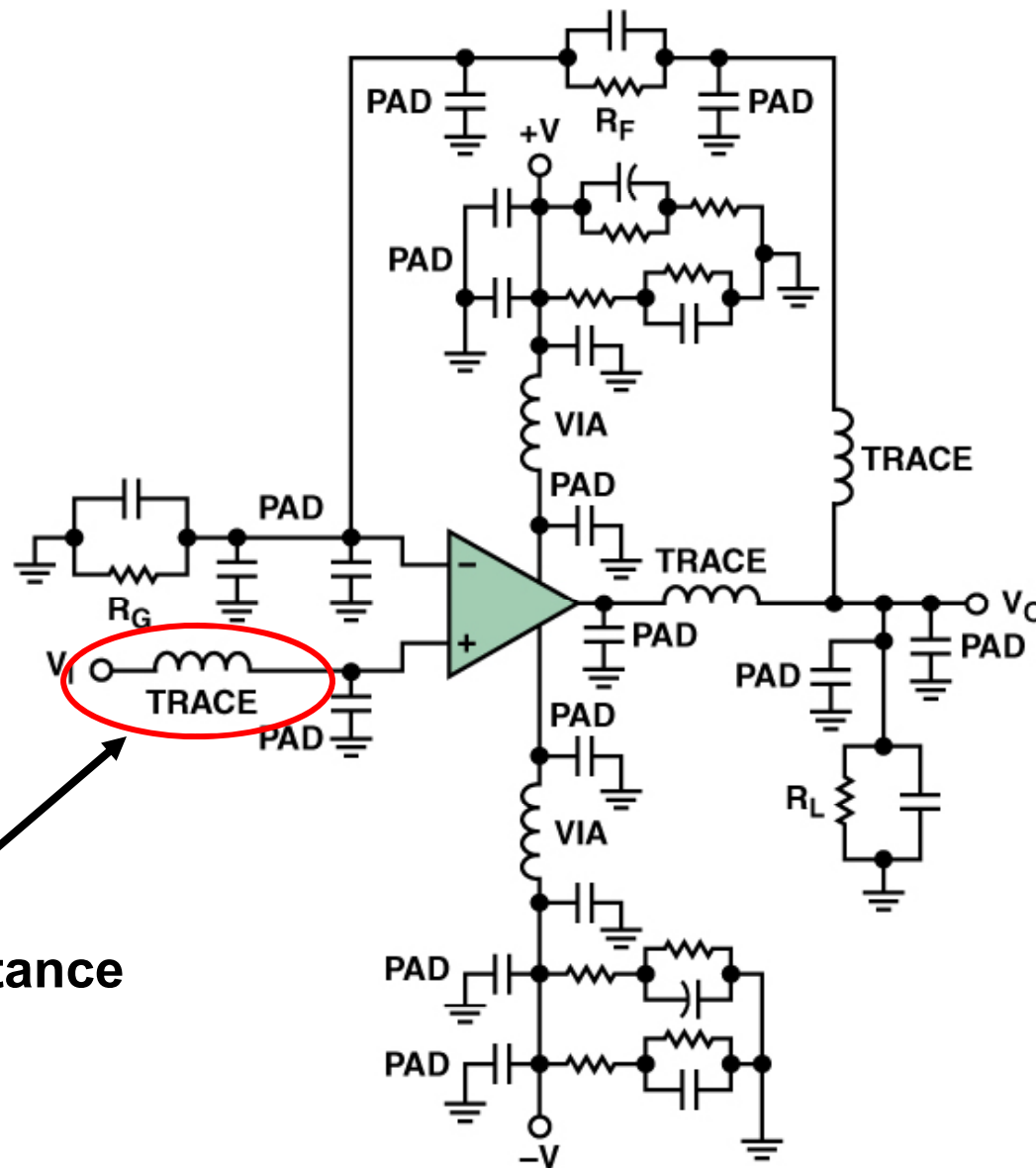


Parasitic Inductance

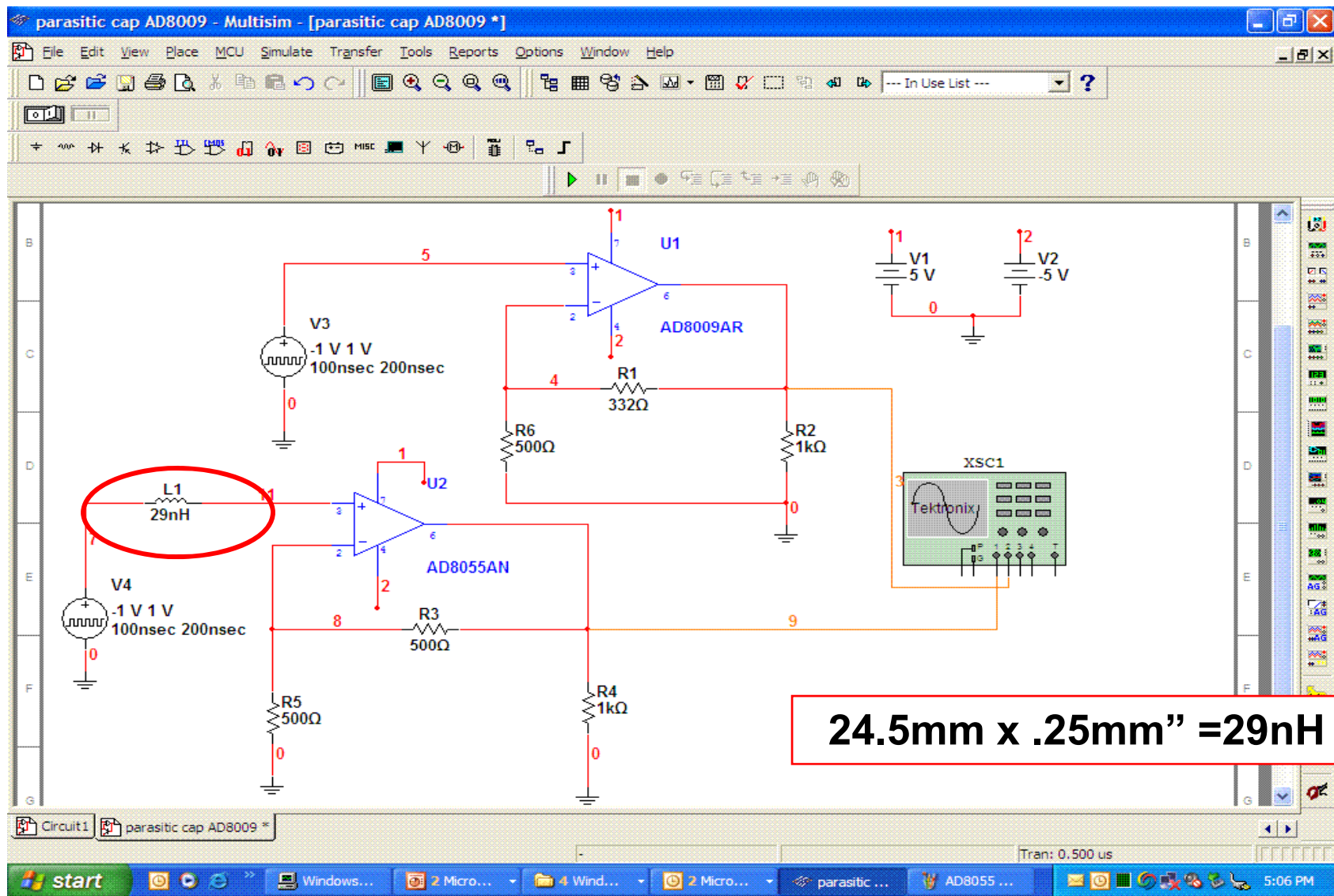
Parasitic Inductance Simulation Schematic



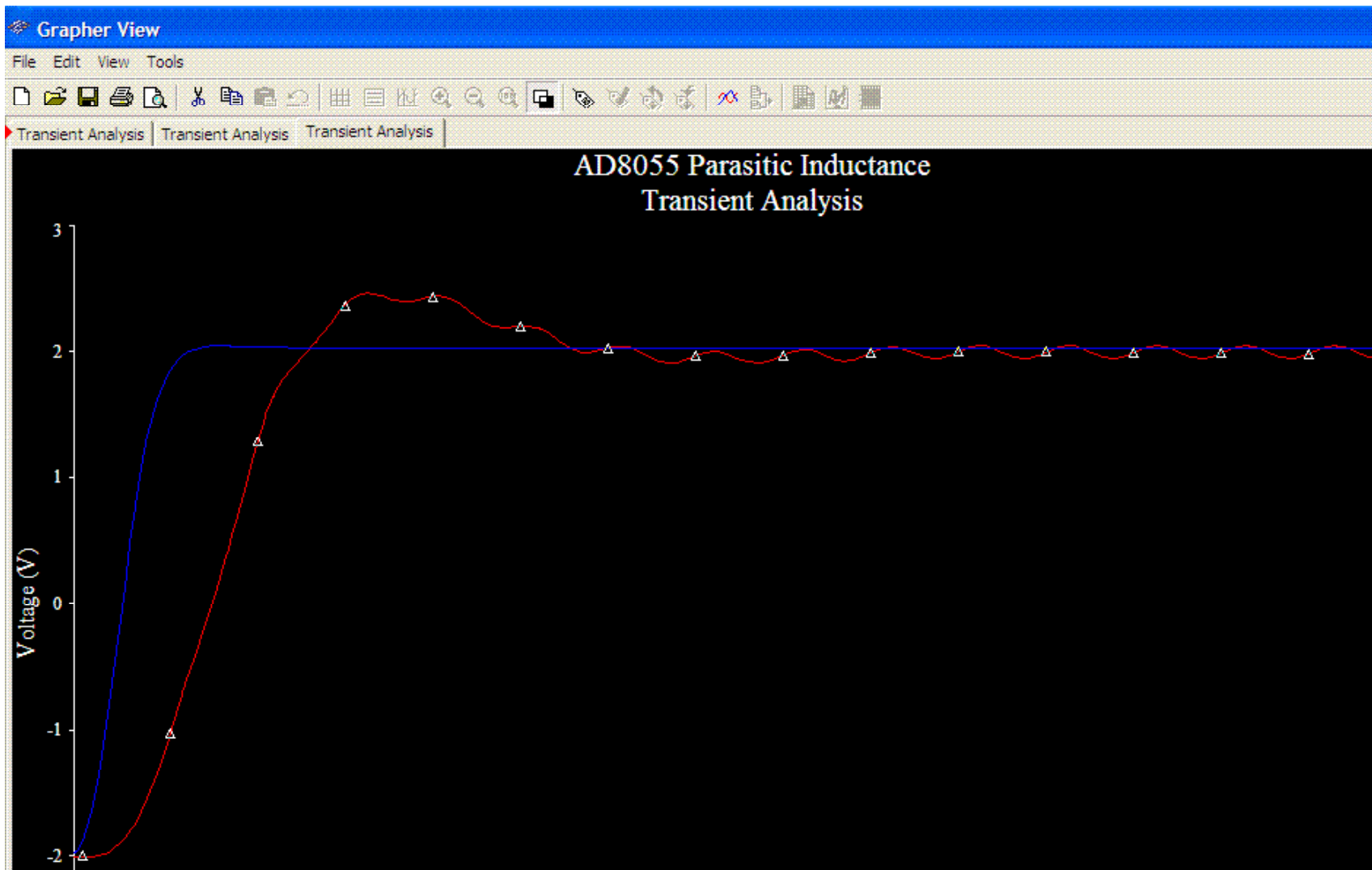
Pulse Response With and Without Ground Plane



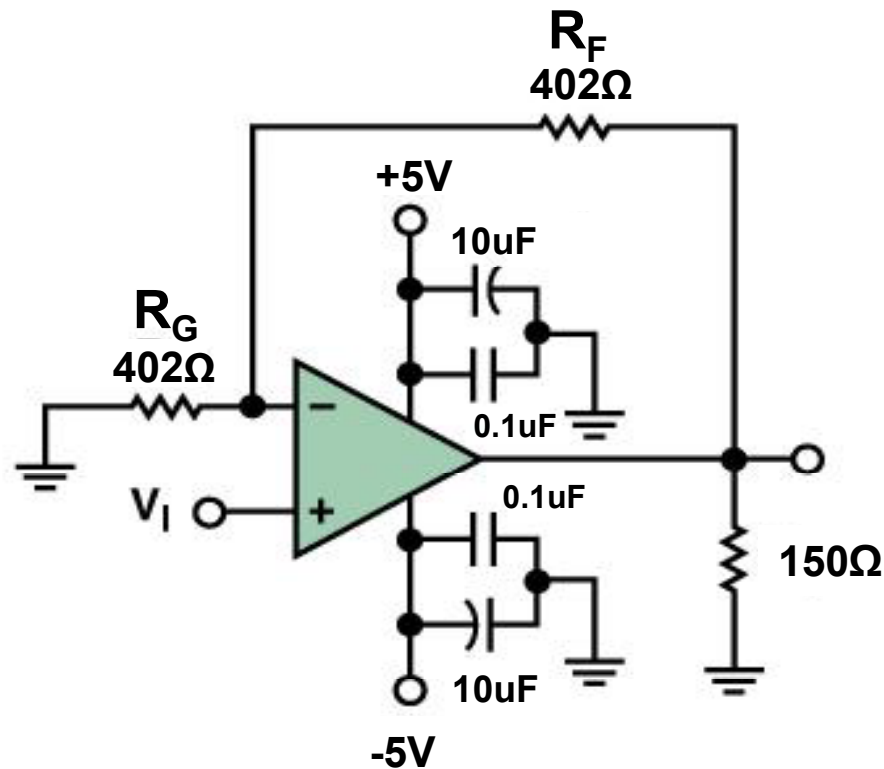
Transient Response AD8009 1GHz Current Feedback Amplifier



Small Changes Can Make a Big Difference!

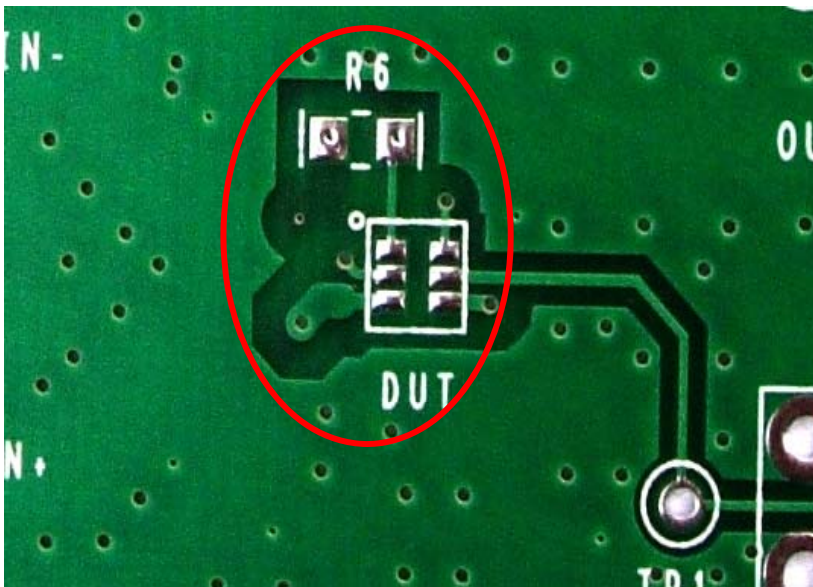


Circuit A

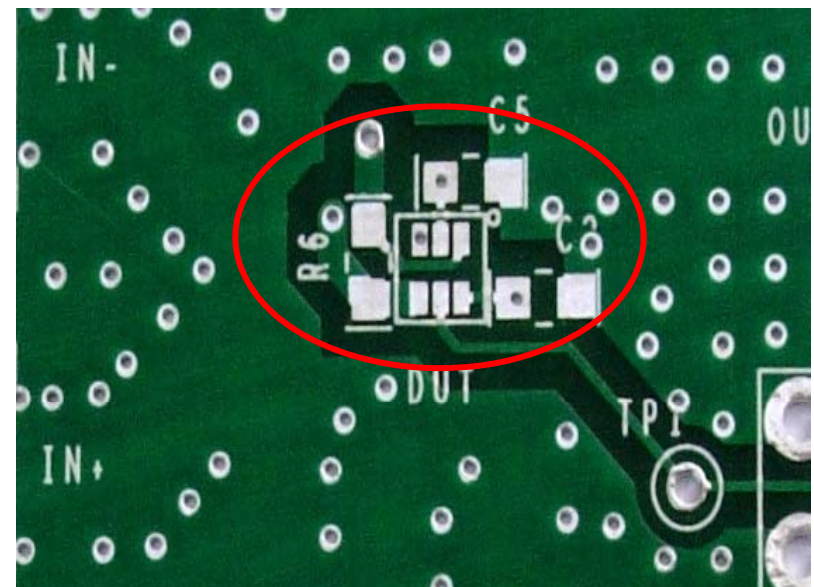


Circuit B

Improper Use of Scope Probe Ground Clip

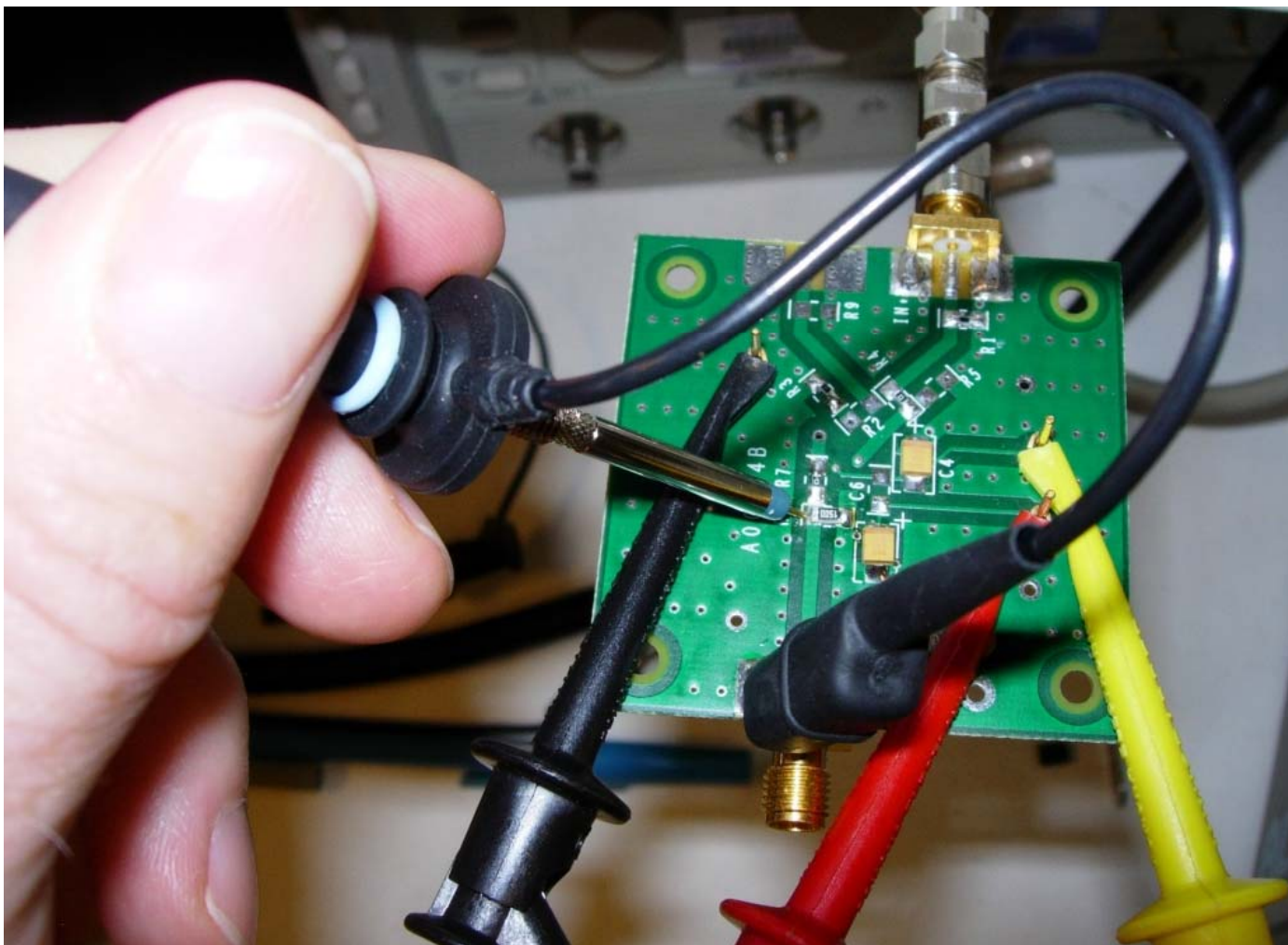


Effect of Clip Lead Inductance

Tek Run: 10.0GS/s ET Sample

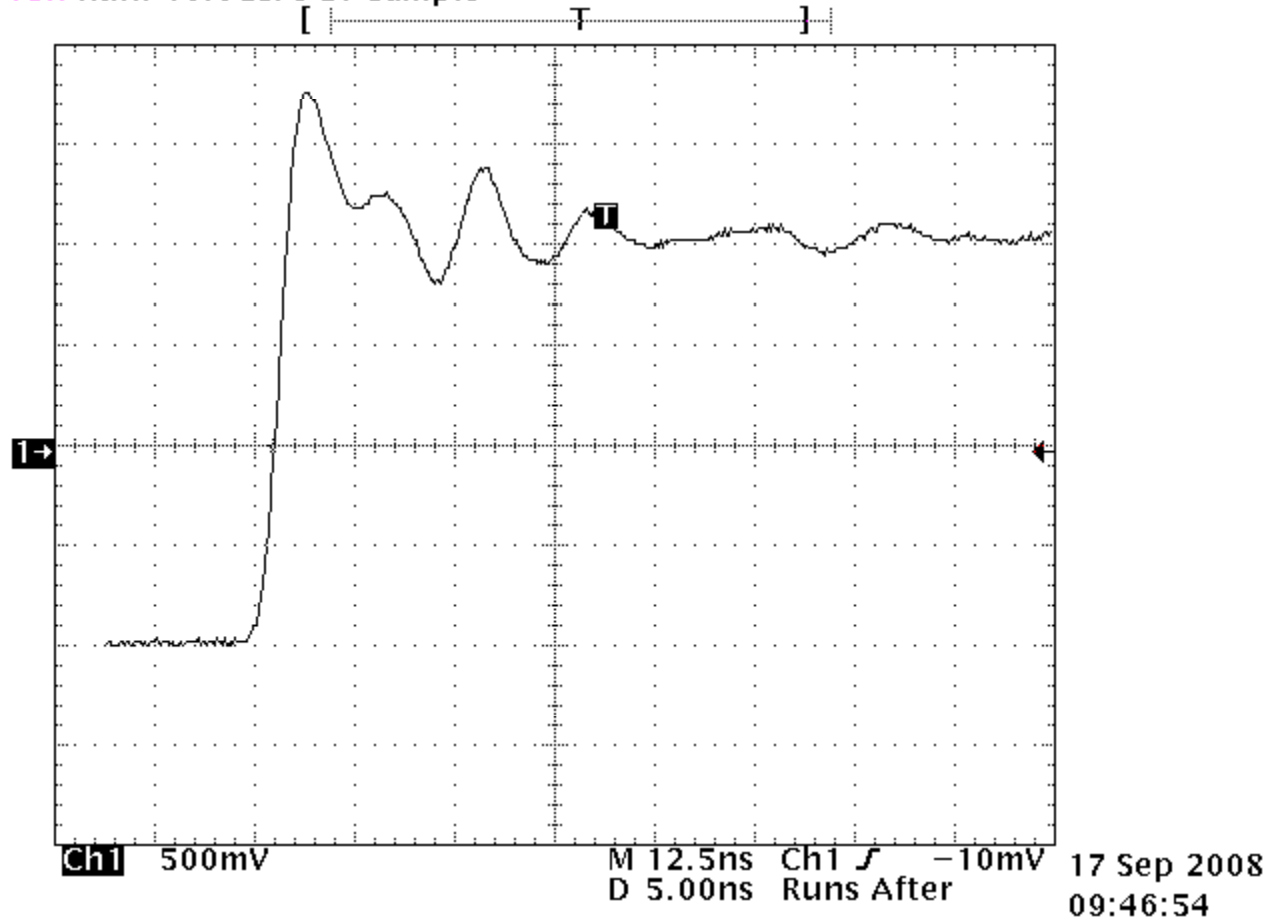


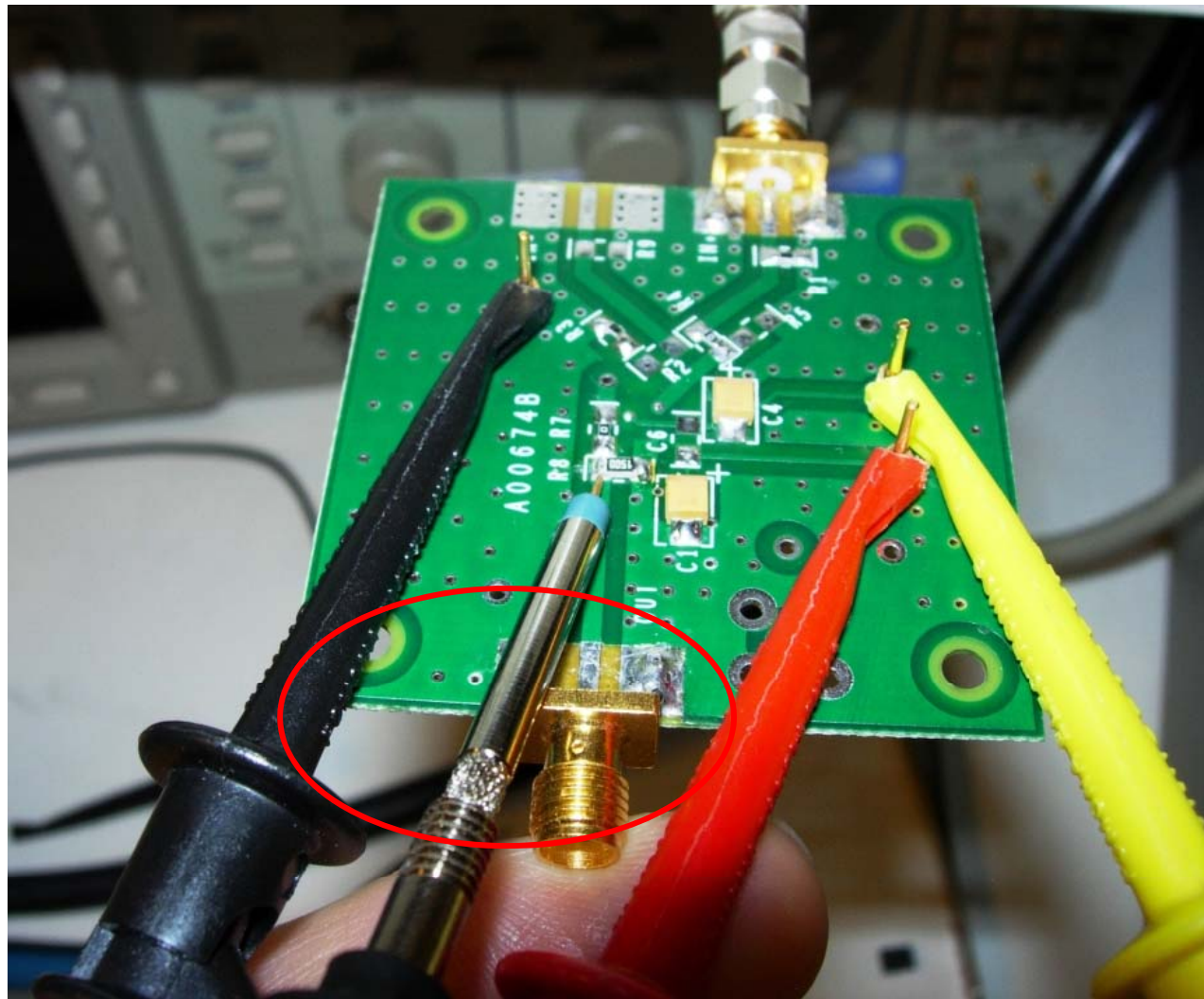Proper Grounding for Scope Probe in High-Speed Measurements




Small Changes Make Big Differences


Circuit A

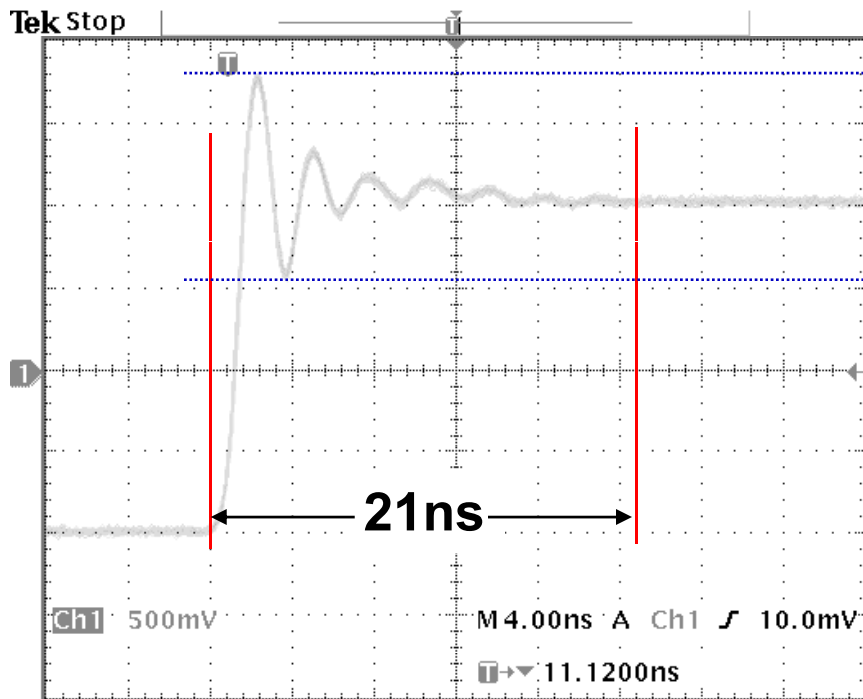

Circuit B

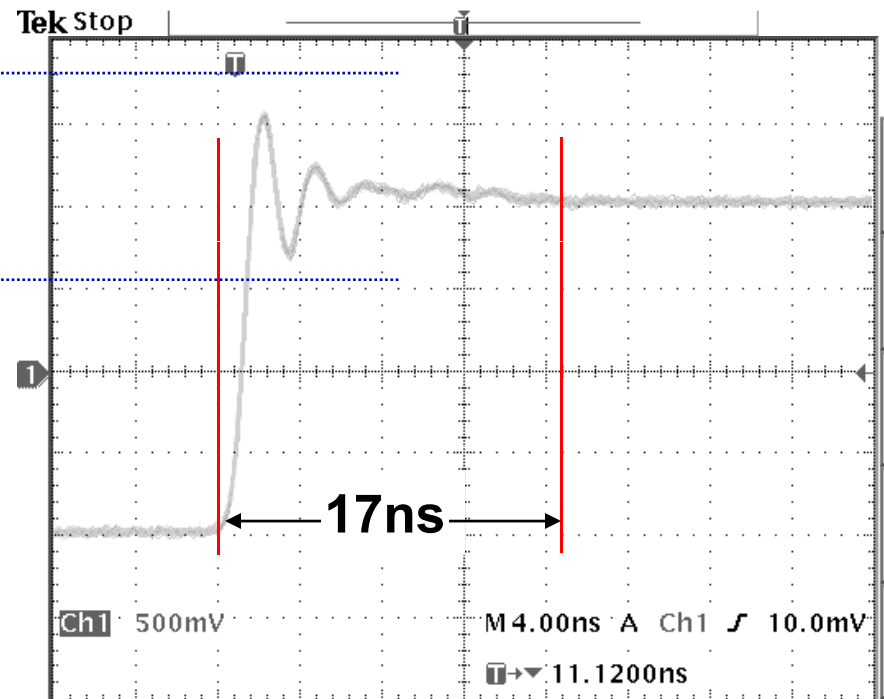

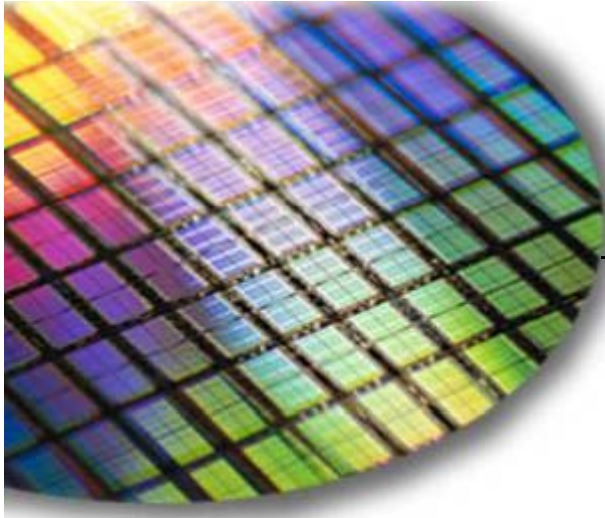25% reduction in ringing duration and amplitude



The World Leader in High Performance Signal Processing Solutions





Ground and Power Planes

Ground and Power Planes Provide



- ◆ **A common reference point**
- ◆ **Shielding**
- ◆ **Lower noise**
- ◆ **Lower resistance**
- ◆ **Lower impedance**
- ◆ **Reduces parasitics**
- ◆ **Heat sink**
- ◆ **Power distribution**

Ground Plane

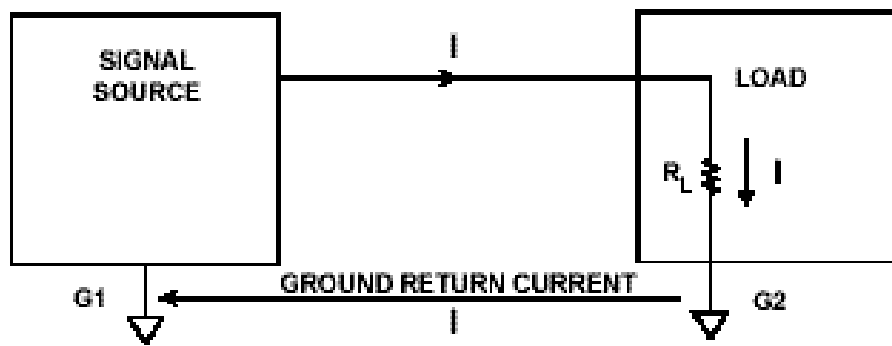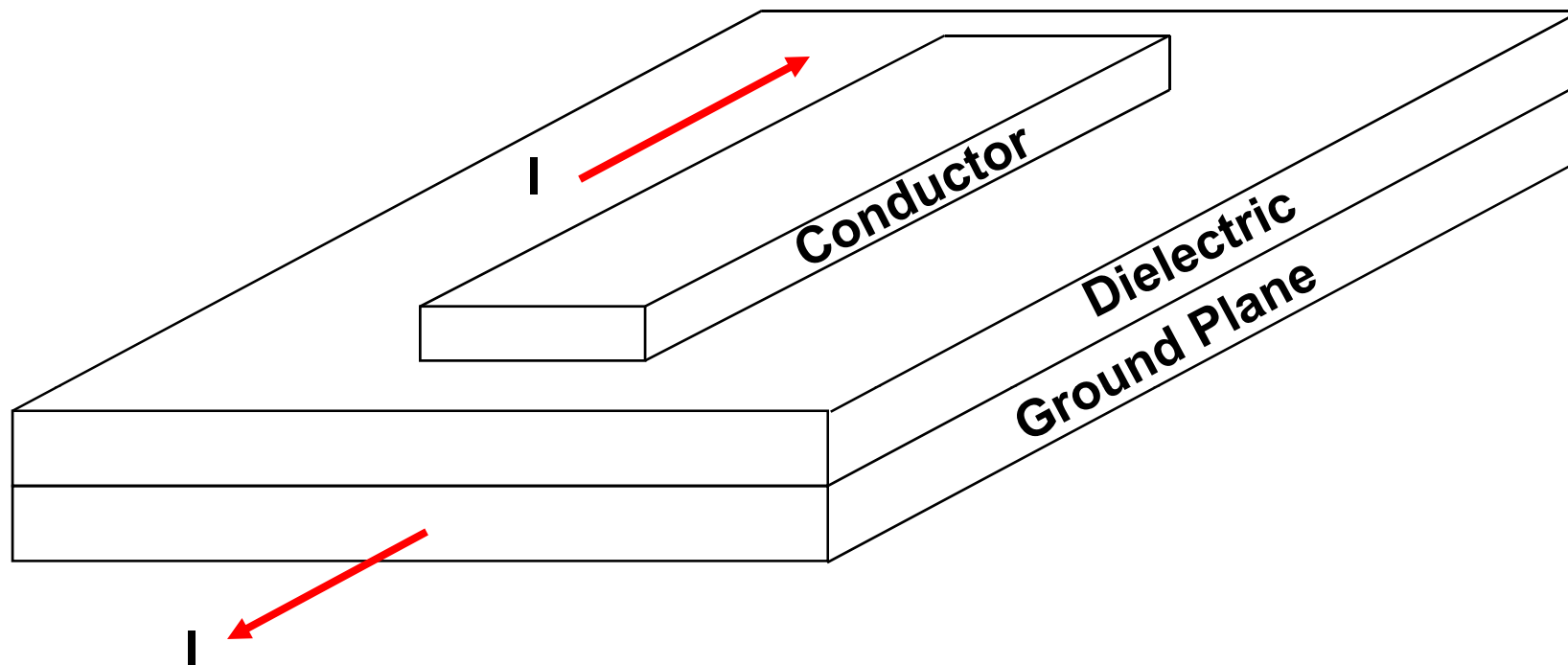



Ground Plane and Trace Routing

Wrong Way

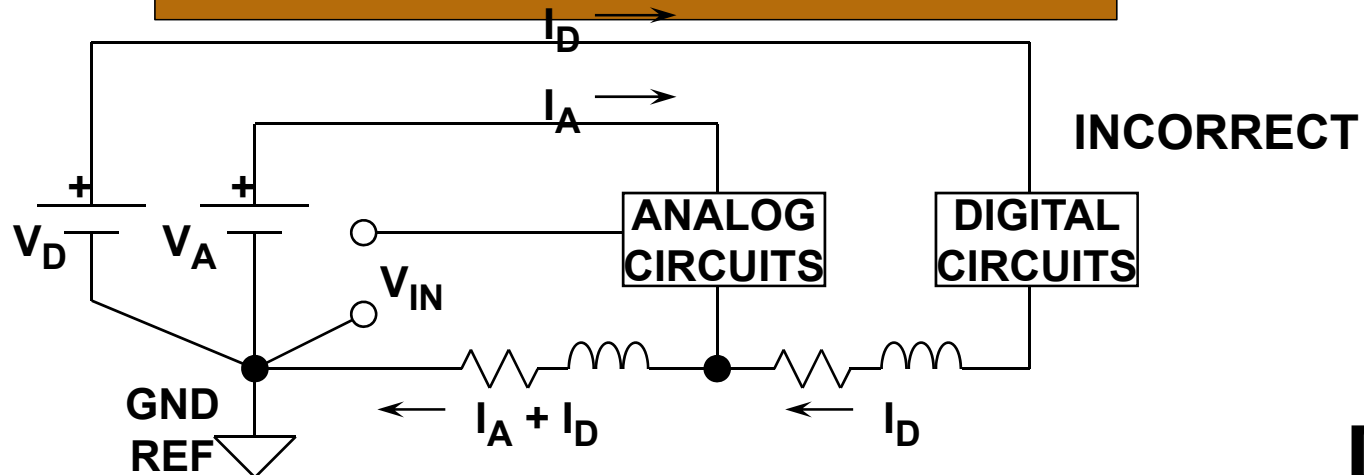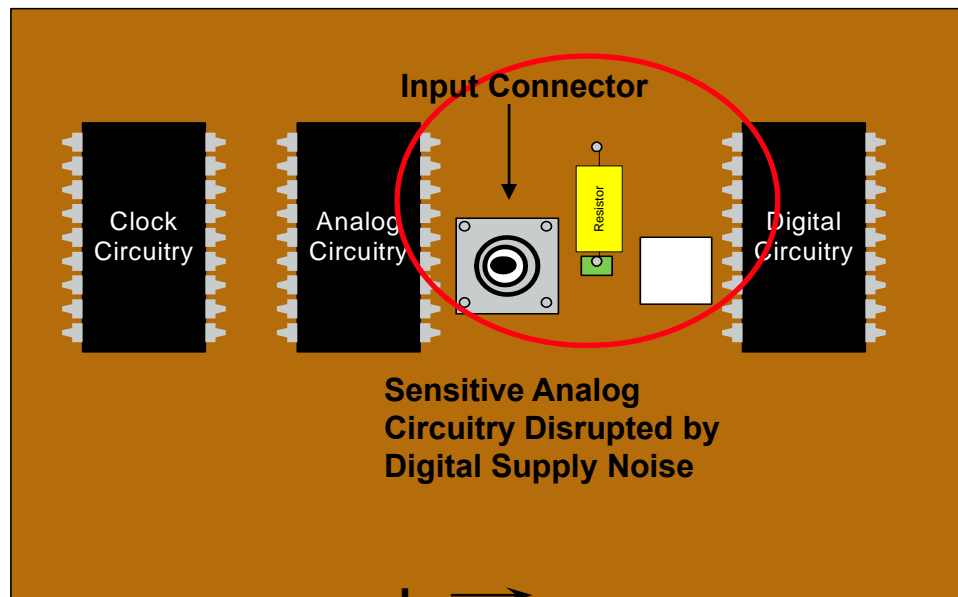



Ground Plane and Trace Routing

Wrong Way

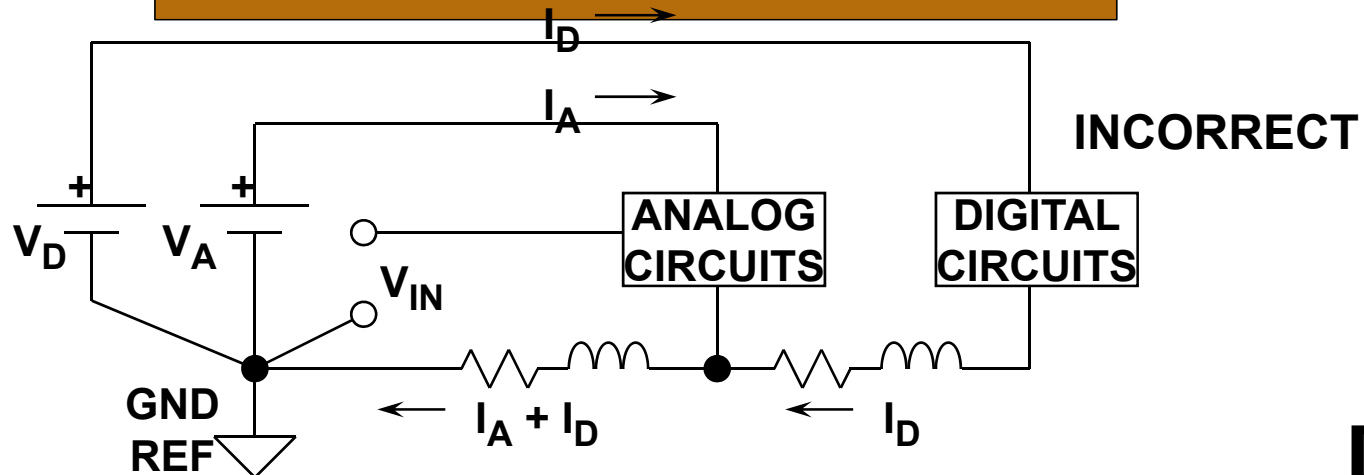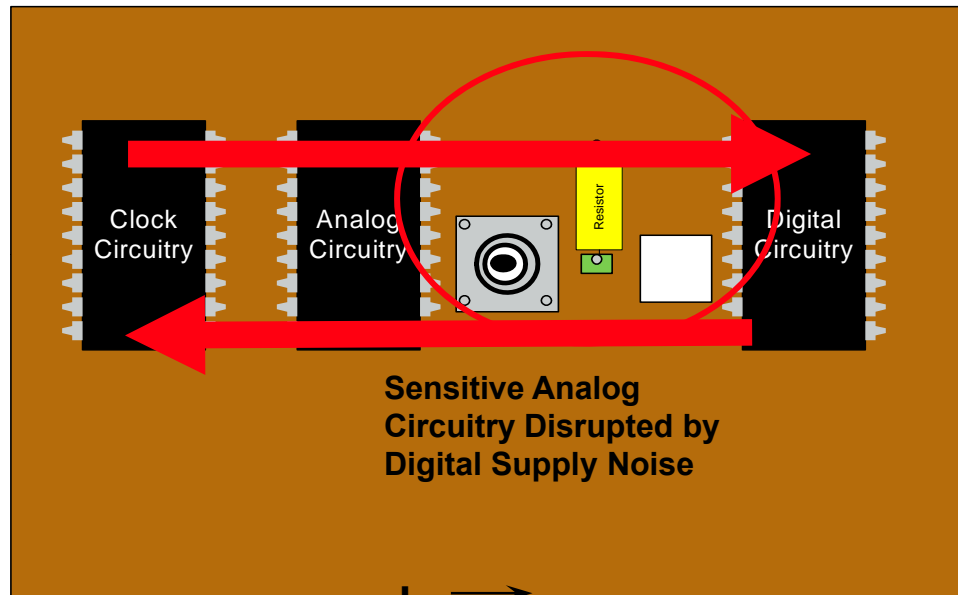



Ground Plane and Trace Routing

Right Way

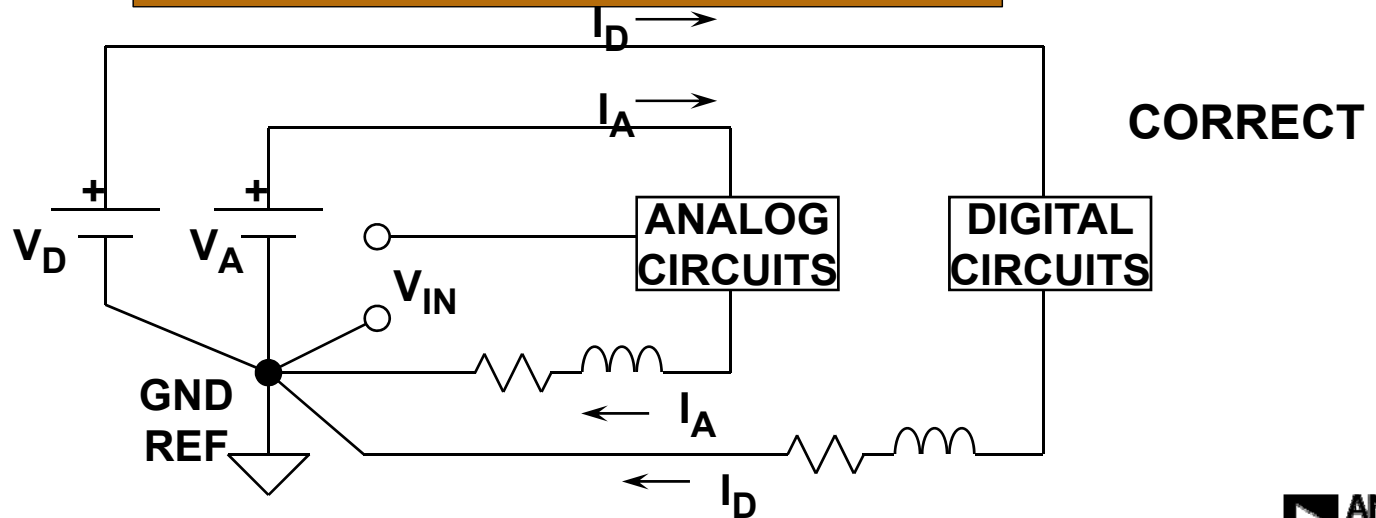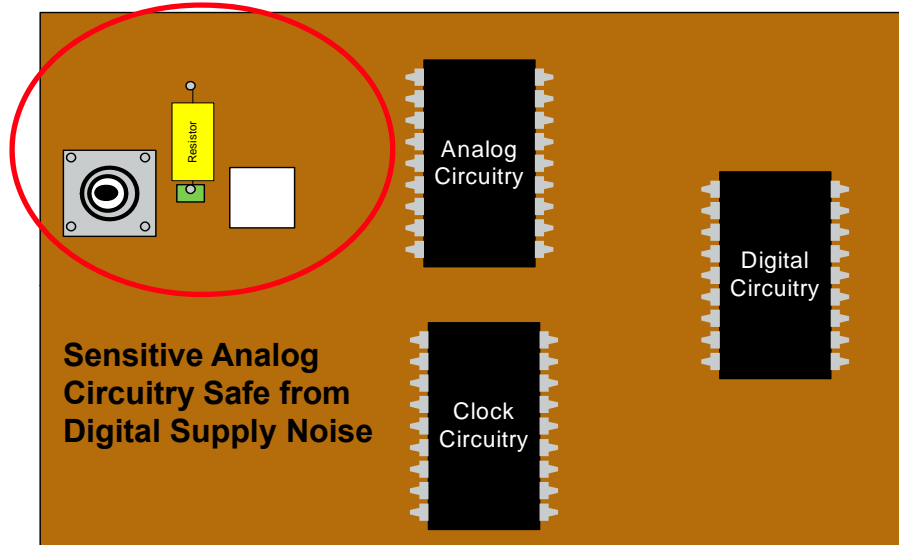

Ground Plane and Trace Routing


Right Way

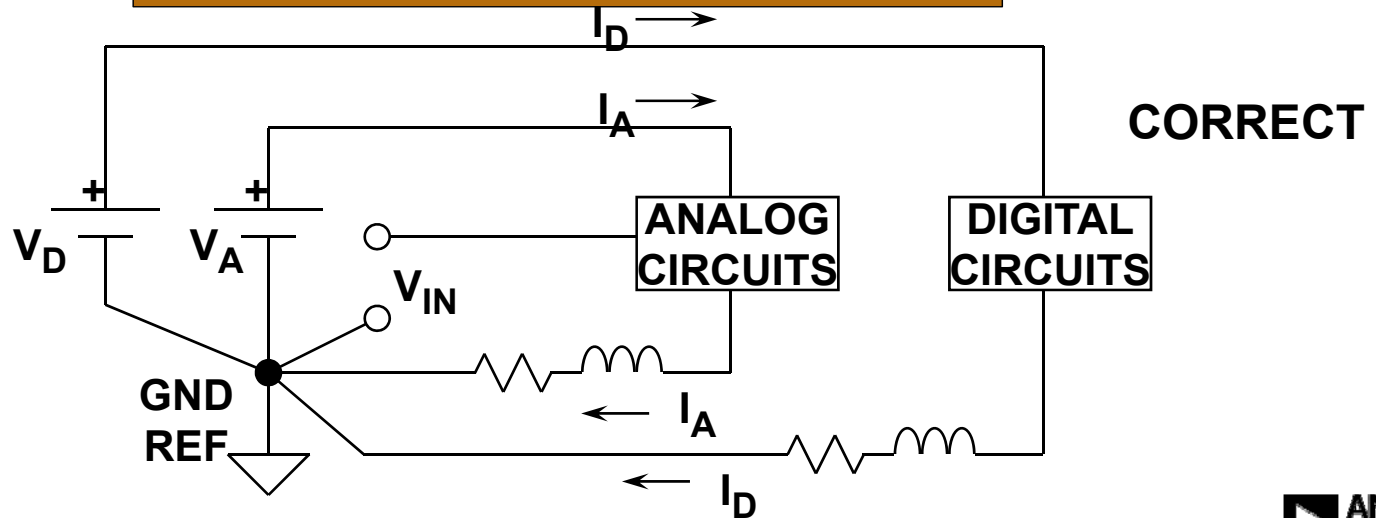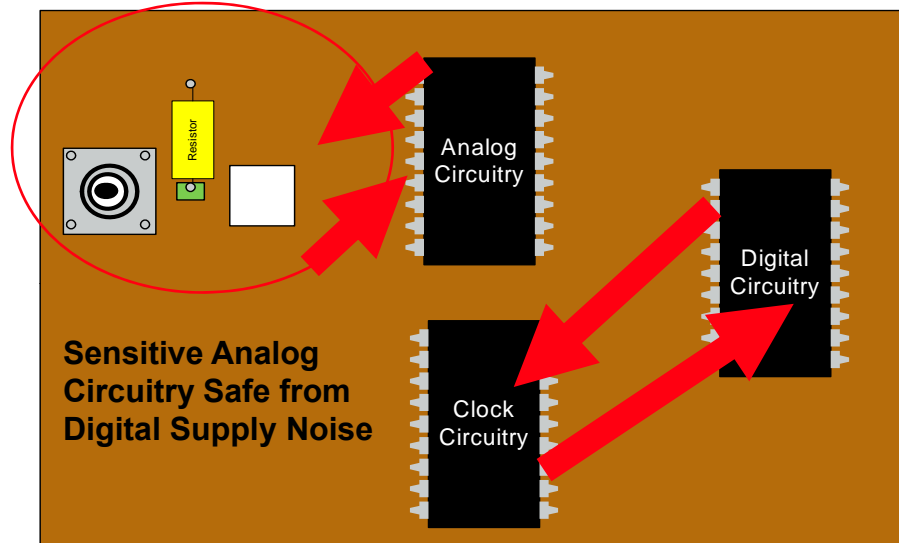

Ground Plane and Trace Routing

Grounding Example:

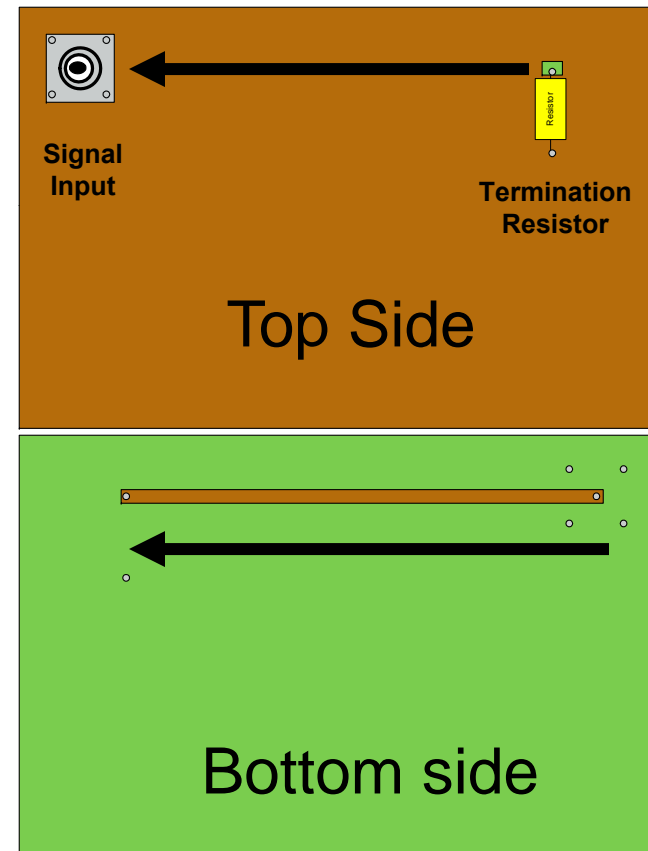
- ◆ Top layer is solid ground.
- ◆ Bottom has a trace/transmission line connecting the RF connector to the load.
- ◆ Return current flows in the top layer ground plane directly above the trace on the opposite side.




Ground Plane and Trace Routing

Grounding Example: DC Current vs. AC Current:

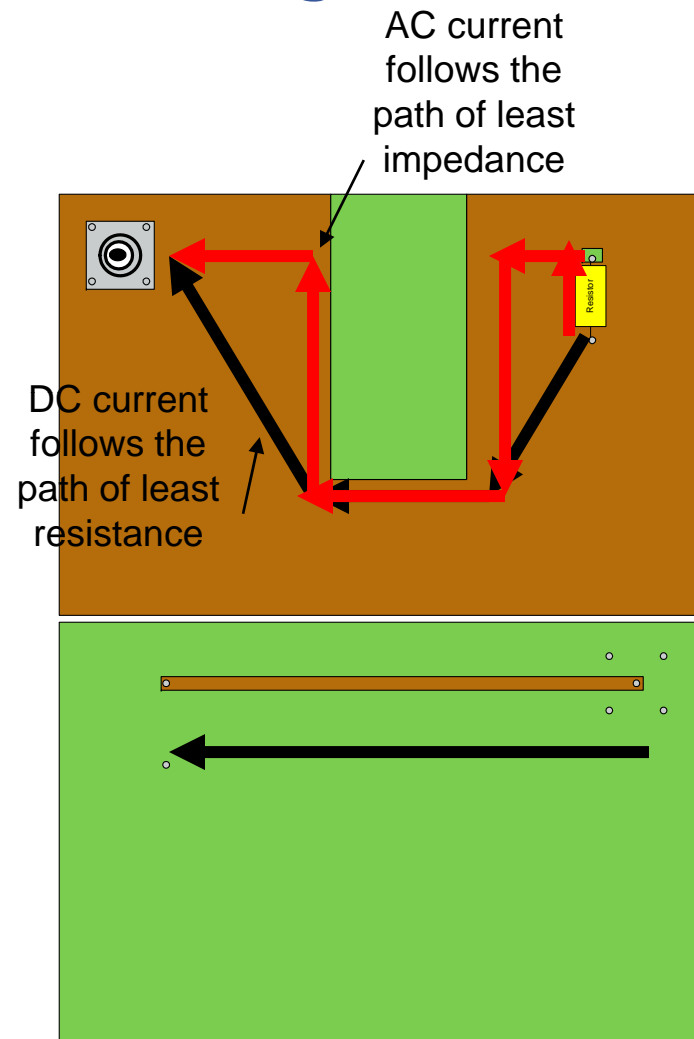- ◆ In a split or broken ground, the return currents follow the path of least impedance
- ◆ At DC, the current follows the path of least resistance
- ◆ As the frequency increases, the current follows the path of least inductance
- ◆ Since there is now a 'loop' the inductance can be quite high and the circuit can now propagate EMI/RFI




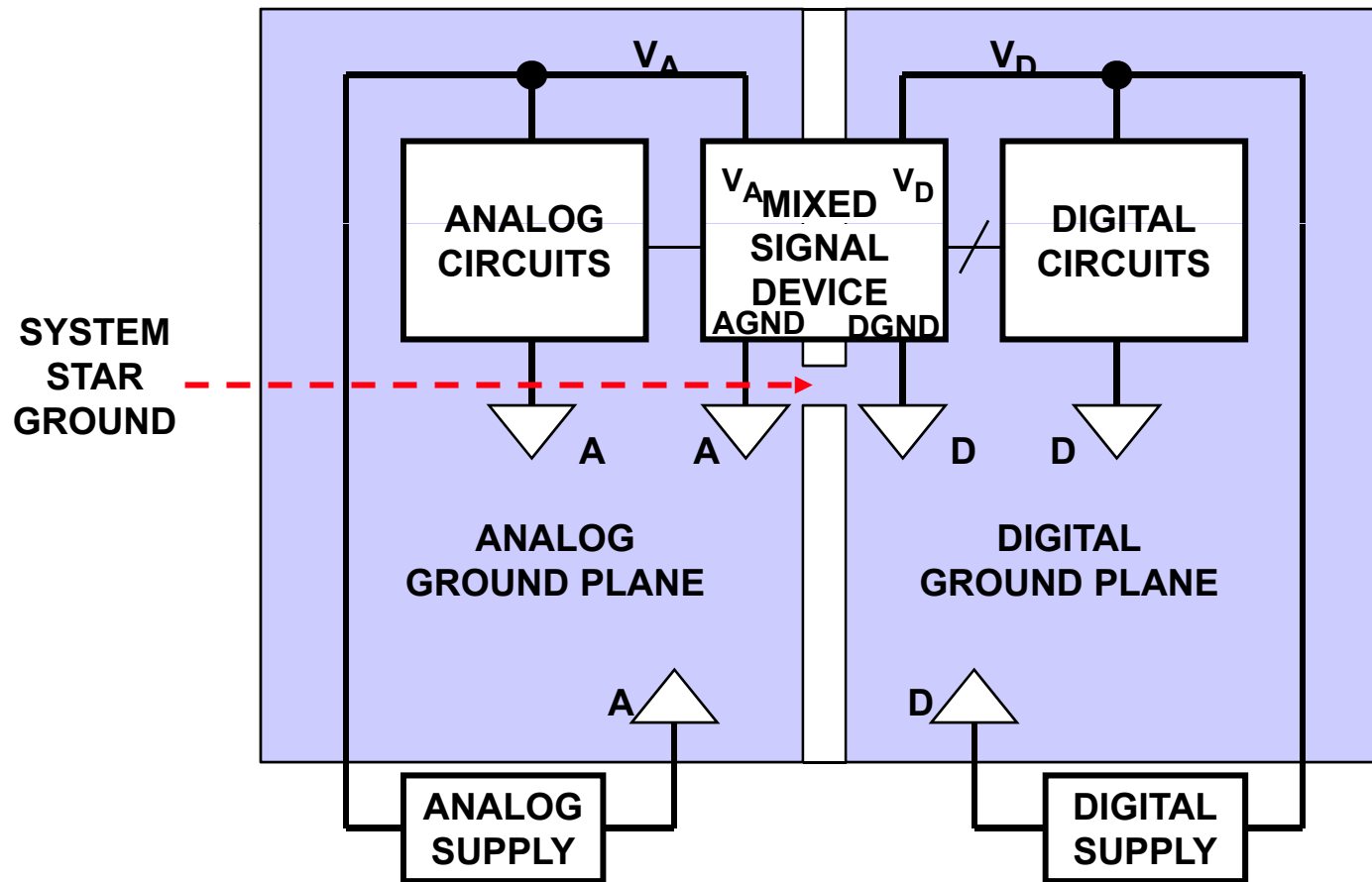Grounding Mixed Signal ICs: Single PC Board



Ground Plane Recommendations

- ◆ **There is no single grounding method which is guaranteed to work 100% of the time!**
- ◆ **Remove ground plane under op amps to reduce parasitic capacitance**
- ◆ **At least one layer on each PC board MUST be dedicated to ground plane!**
- ◆ **Provide as much ground plane as possible especially under traces that operate at high frequency**
- ◆ **Use thickest metal as feasible (reduces resistance and provides improved thermal transfer)**
- ◆ **Use multiple vias to connect same ground planes together**
- ◆ **Do initial layout with split analog and digital ground planes**
- ◆ **Follow recommendations on device data sheet (read datasheet)**
- ◆ **Keep bypass capacitors and load returns close to reduce distortion**
- ◆ **Connect analog, digital and RF grounds at one point**

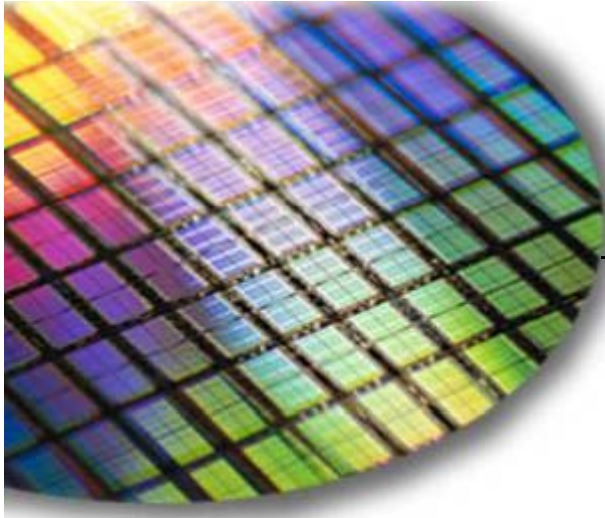

The World Leader in High Performance Signal Processing Solutions



Packaging and Pinout

Op Amp Packaging and Pinout

◆ Packaging plays a large role in high-speed applications

Smaller packages



- Better at higher speeds
- Less parasitics
- Compact layout

◆ Analog Devices Low Distortion Pinout

- Intuitively makes more sense
- Compact layout
- Streamline signal flow
- Lower distortion



Op Amp SOIC Packaging

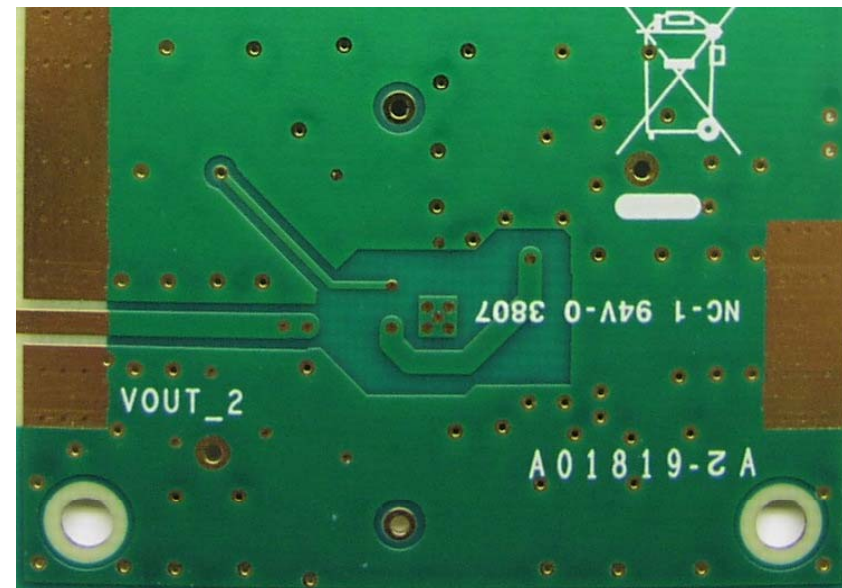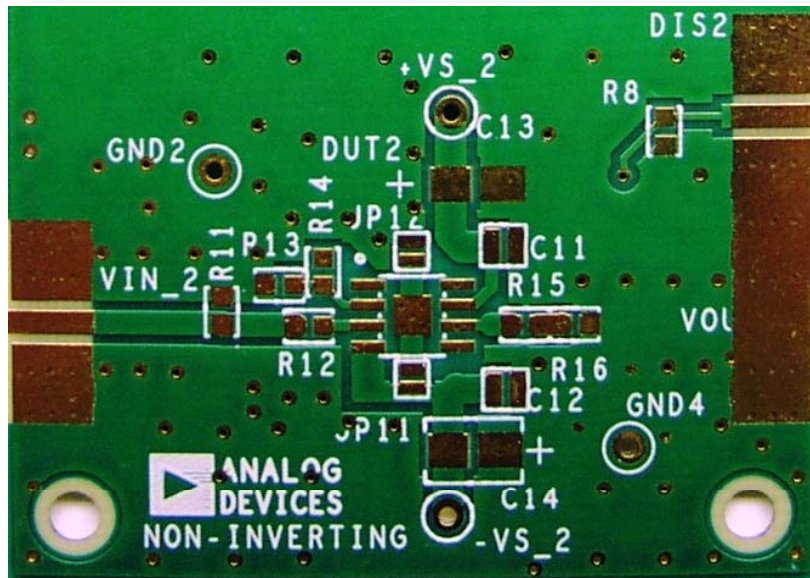- ◆ Traditional SOIC-8 layout
- ◆ Feedback routed around or underneath amplifier





Op Amp SOIC Packaging

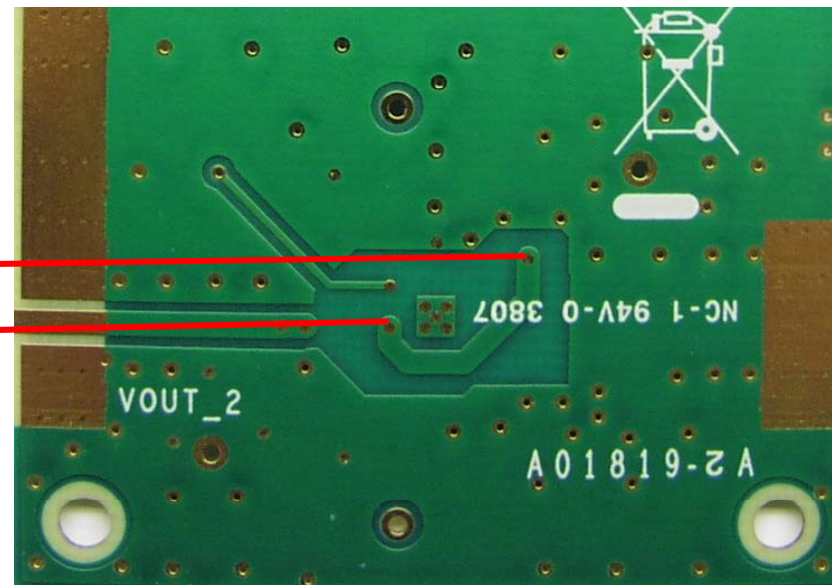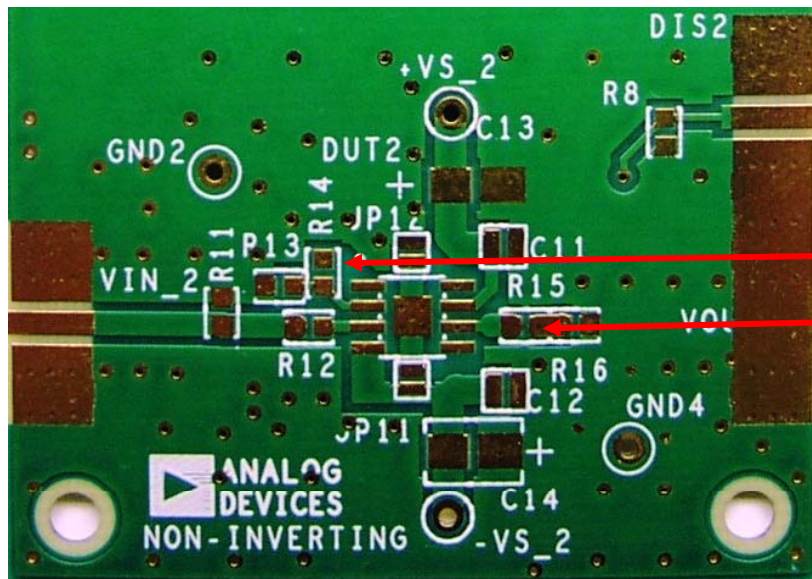- ◆ Traditional SOIC-8 layout
- ◆ Feedback routed around or underneath amplifier



Analog Devices Low Distortion Pinout


◆ Pinout enables compact layout

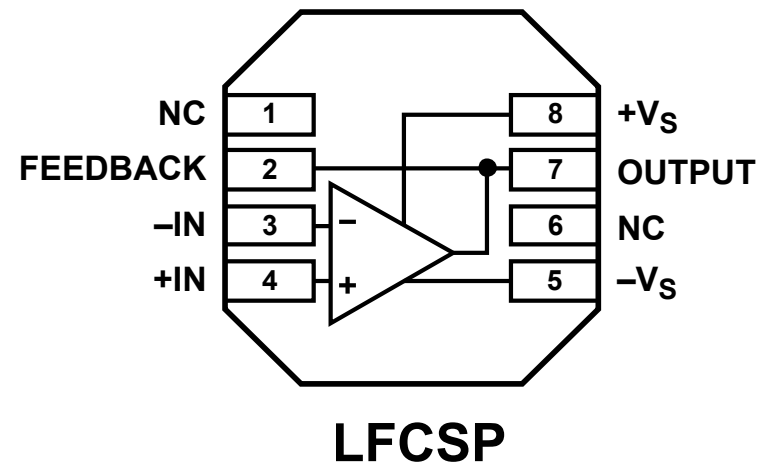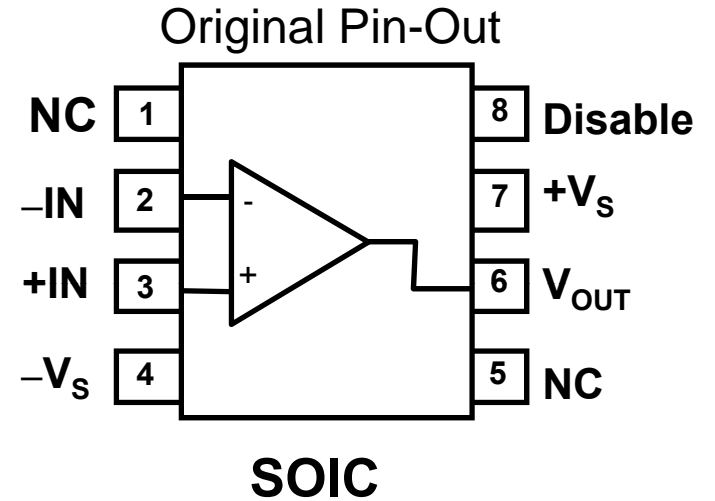

04814-0-001

Analog Devices Low Distortion Pinout


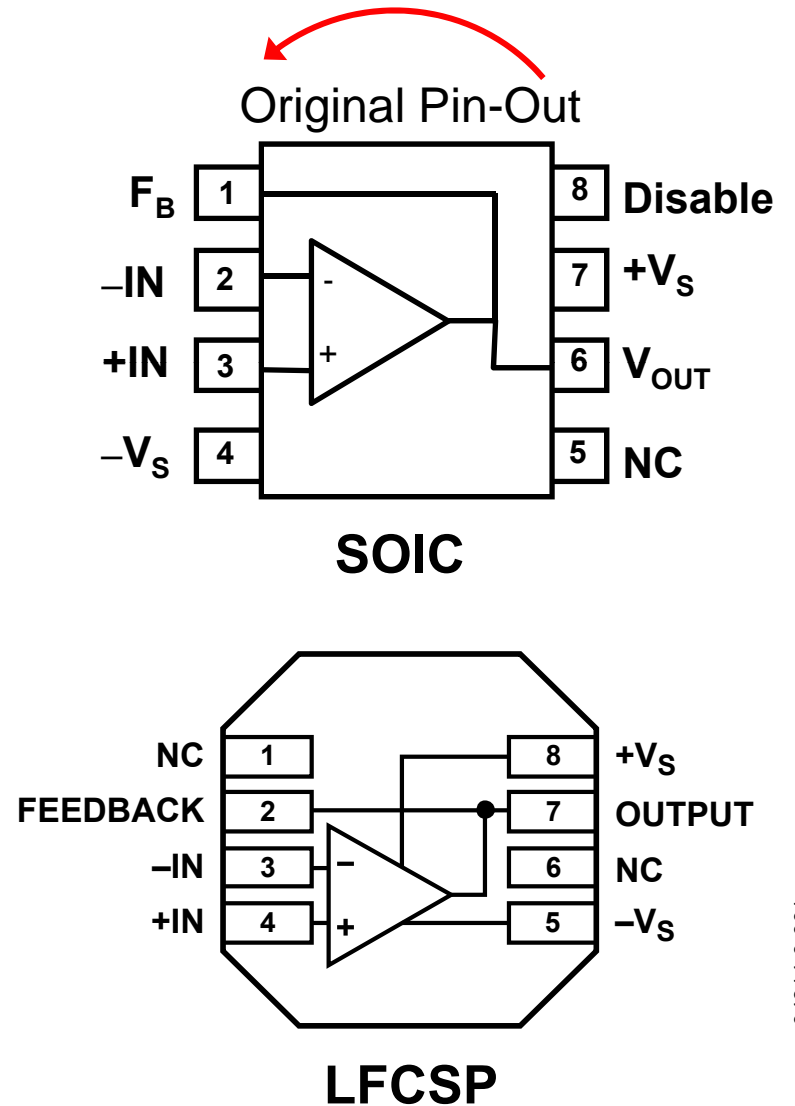
- ◆ Pinout enables compact layout
- ◆ Lower distortion



04814-0-001

Analog Devices Low Distortion Pinout

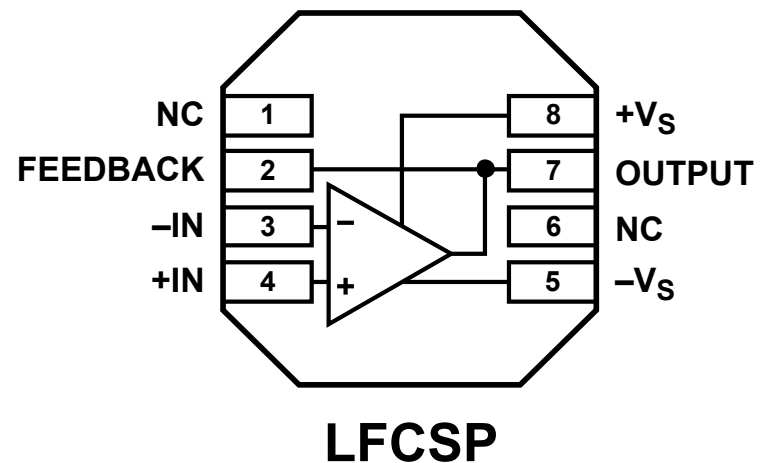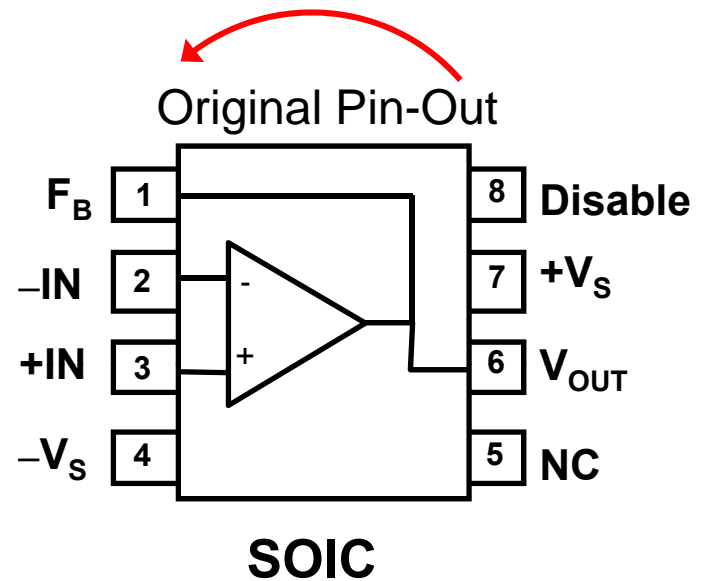
- ◆ Pinout enables compact layout
- ◆ Lower distortion
- ◆ Improved thermal performance



04814-0-001


Analog Devices Low Distortion Pinout

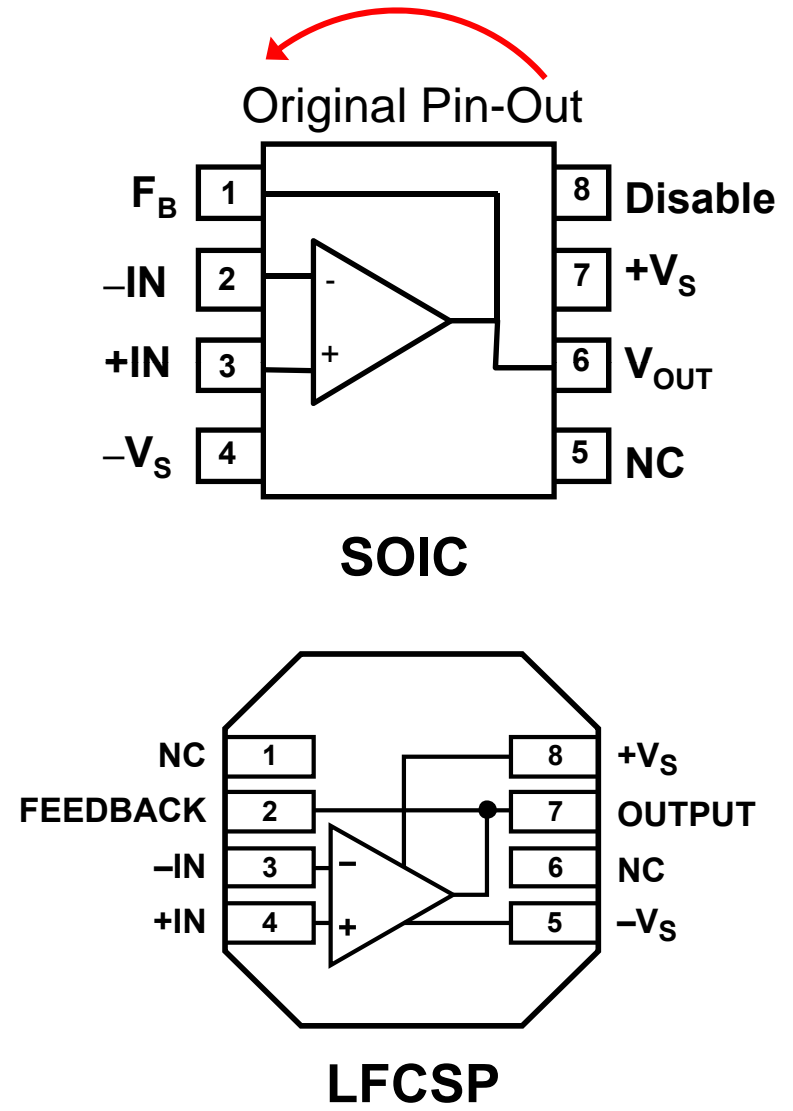- ◆ Pinout enables compact layout
- ◆ Lower distortion
- ◆ Improved thermal performance
- ◆ LFCSP
 - AD8099, AD8045, AD8000, ADA4899, ADA4857, ADA4817






04814-0-001

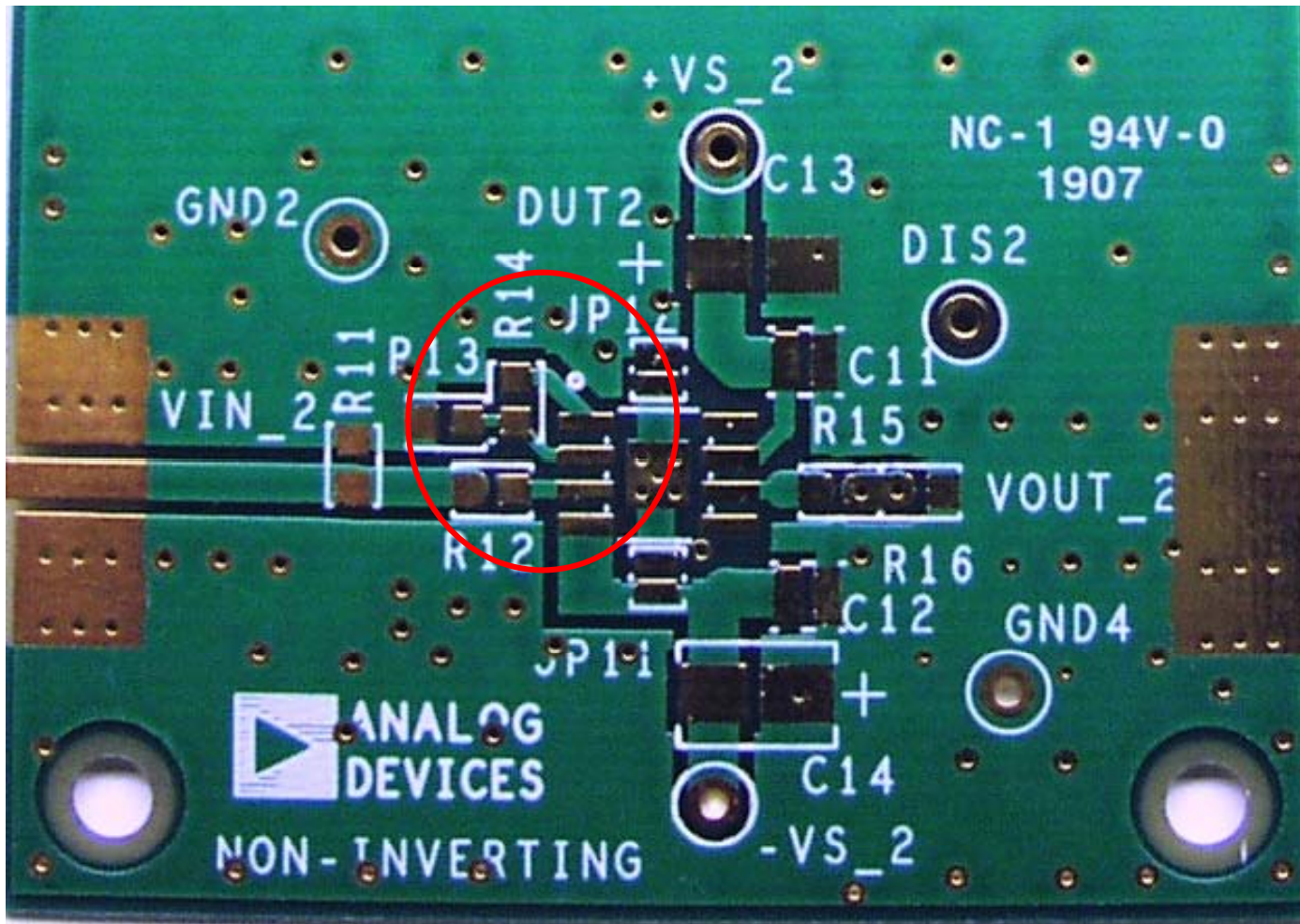Low distortion pinout enables compact and streamline layout



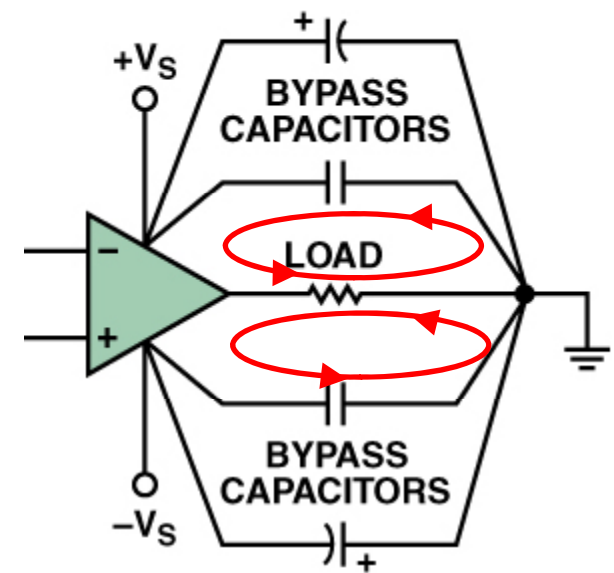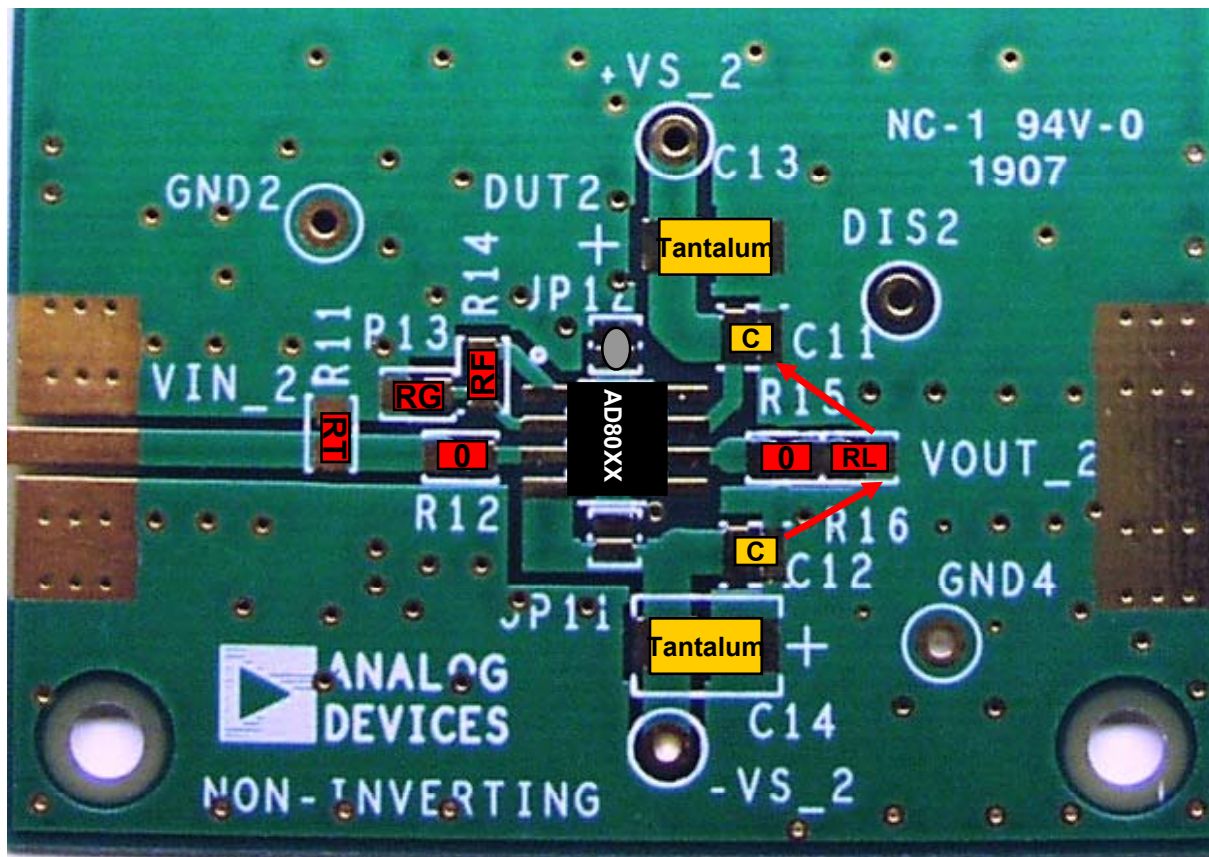Low distortion pinout enable compact and streamline layout



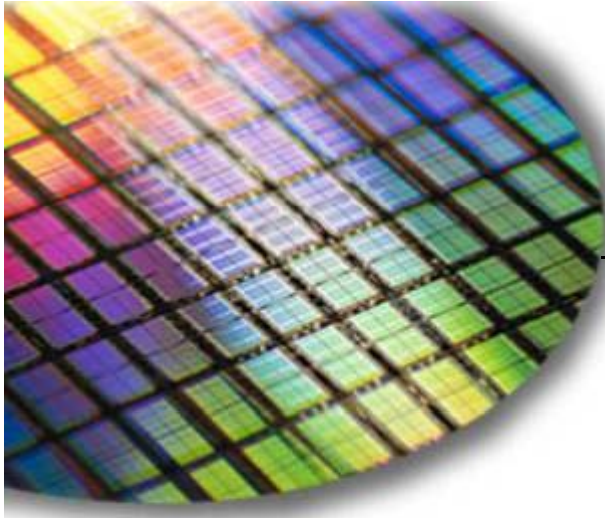

The World Leader in High Performance Signal Processing Solutions



RF Signal Routing and Shielding

In This Section

- ◆ **RF Components from Analog Devices**
- ◆ **PC Board Circuit Material Types and Minimizing Losses**
- ◆ **Microstrip and Stripline Transmission Lines**
- ◆ **Ground Plane Layout Considerations**
- ◆ **Developing a RF Printed Circuit Board**
- ◆ **Using Discrete Components with RF Devices**
- ◆ **Shielding of RF Circuit Boards**

RF Components from Analog Devices

ANALOG DEVICES Search [] GO English [] GO

View Cart | myAnalog | Log In | Contact ADI

ADI Home

Welcome. [Log in](#) to access your preferences.

Save to myAnalog Print Email this Page

RF/IF Components

DDS Modulators

Digital Up / Down Converters

Direct Digital Synthesis (DDS)

Log Amps / Detectors

Mixers / Multipliers

Modulators / Demodulators

PLL Synthesizers/VCOs

RF / IF Amplifiers

RF / IF Transceivers

RF Switches

RMS Detectors

RX / TX Subsystems

Short Range Transceivers

All Product Categories ▶

All Applications ▶

Design Tools & Support ▶

Buy Online ▶

RF/IF Components

The ADF9010 is a fully integrated RF Tx modulator and Rx analog baseband front end that operates in the frequency range from 840 MHz to 960 MHz. The receive path consists of a fully differential IQ baseband PGA, low pass filter, and general signal conditioning before connecting to an Rx ADC for baseband conversion. Learn more about the [ADF9010](#).

Product Categories

- ▶ **DDS Modulators**
- ▶ **Digital Up / Down Converters**
- ▶ **Direct Digital Synthesis (DDS)**
- ▶ **Log Amps / Detectors**
- ▶ **Mixers / Multipliers**
- ▶ **Modulators / Demodulators**
- ▶ **PLL Synthesizers/VCOs**
- ▶ **RF / IF Amplifiers**
- ▶ **RF / IF Transceivers**
- ▶ **RF Switches**
- ▶ **RMS Detectors**
- ▶ **RX / TX Subsystems**
- ▶ **Short Range Transceivers**

News **New Products** **Design Tools**

- ▶ Analog Devices Introduces [High-Performance Analog Front End for 900 MHz Band RF Applications](#).
- ▶ [ADI's Digitally Programmable Variable Gain Amplifier and Driver](#) is First to Drive Low Impedances from a Single Power Supply
- ▶ [ADI's High-Performance RF Driver Amplifier](#) Reduces Power, Size, and Cost of WIMAX and Wireless Applications

Integrated High Performance RF Front End

ADF9010

<http://www.analog.com/en/rfif-components/products/index.html>

Privacy/Security My Analog Contact ADI Site Map Registration Technical Support Terms of Use

© 1995-2008 Analog Devices, Inc. All Rights Reserved



Analog Devices Components Requiring Matched RF Interfaces

- ◆ **AD60x, AD8xxx and ADL533x series of RF/IF and Variable Gain Amplifiers**
- ◆ **ADF70xx and 702x series Radio Transmitters and Transceivers**
- ◆ **AD4xxx and ADF7xxx series of PLL Synthesizers and VCO's**
- ◆ **AD84xx and ADL53xx series of Modulators and Demodulators**
- ◆ **AD83xx and ADL539x series of Mixers and Multipliers**
- ◆ **AD83xx and ADL5519 series of Log Amps and Detectors**
- ◆ **AD836x and ADL550x series of RMS Detectors**
- ◆ **ADG9xx series of RF Switches**

PC Board Circuit Material Type and Minimizing Losses

- ◆ **PC board material selection is usually based on price verses performance**
- ◆ **Select PC board dielectric material to have the lowest loss tangent**
- ◆ **Some types of “FR4” dielectric materials are low loss below 8-10 GHz**
- ◆ **PTFE(Teflon) dielectric material is usually used for the lowest loss at the higher RF and microwave frequency ranges, but at a much higher price**
- ◆ **Be sure that the correct impedance transmission line is used for the interconnection of the RF devices**
- ◆ **Use as wide of a transmission line as possible for the correct impedance, and try to keep it short to reduce “Skin Effect” losses**
- ◆ **Use high “Q”, or low loss passive components for all RF matching, coupling, and bypassing requirements**

Microstrip and Stripline Transmission Lines


- ◆ **50 ohm interfaces are most often used between most “integrated” RF devices**
- ◆ **Interconnects less than $1/20$ of a wavelength long can usually be made without a matched transmission line**
- ◆ **Avoid long microstrip lines as they could become “antennas”(microstrip) and radiate RF**
- ◆ **To minimize coupling to the transmission line, DO NOT place other traces or ground plane closer than three times of the dielectric height**
- ◆ **Use proper technique for making bends in microstrip lines**
- ◆ **Locate the microstrip lines on the component side of the board if possible**

Microstrip Transmission Lines

◆ Microstrip Controlled Impedance Line Cross Section

- ◆ Advantages:
- ◆ Transmission line on outside layer of board
- ◆ Easy to attach components to trace
- ◆ Components can be placed at different locations along the line to aid in tuning
- ◆ Aid in RF testing as you are able to measure levels along the line

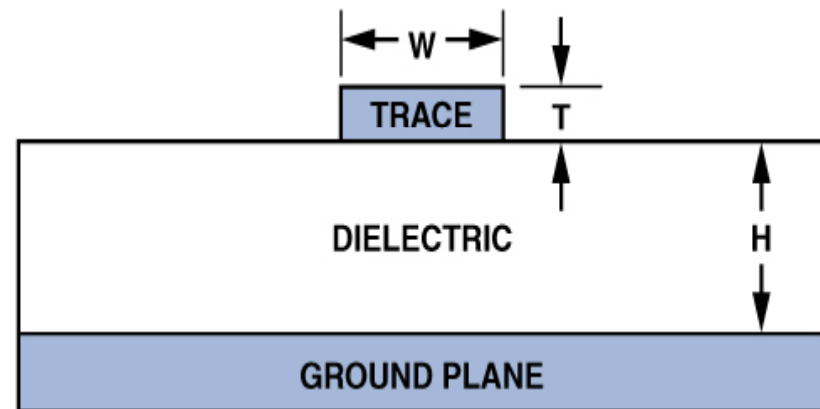- ◆ Disadvantages:
- ◆ Slightly higher loss
- ◆ Not shielded and could radiate RF signal




$$Z_o = \frac{87}{\sqrt{\epsilon_r} + 1.41} \ln \left[\frac{5.98H}{(0.8W + T)} \right]$$

Stripline Transmission Lines

◆ Stripline

Controlled Impedance Line Cross Section

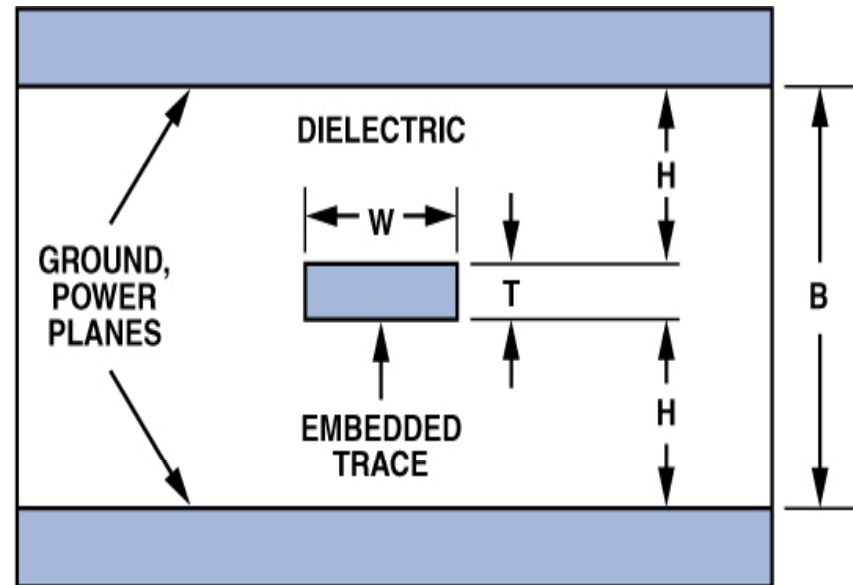- ◆ **Advantages:**
- ◆ **Lower loss at higher microwave frequencies**
- ◆ **Shielded transmission line, no RF radiation from board**
- ◆ **Disadvantages:**
- ◆ **Requires vias to connect to line**
- ◆ **No ability to connect tuning or termination components to line**
- ◆ **No access to line to make adjustments or connections to line for RF testing**
- ◆ **Higher PCB cost**




$$Z_o (\Omega) = \frac{60}{\sqrt{\epsilon_r}} \ln \left[\frac{1.9(B)}{(0.8W + T)} \right]$$

Microstrip and Stripline Transmission Lines


◆ Bends in Microstrip and Stripline

- ◆ In order to preserve a constant impedance around a bend, some general layout rules **MUST** be followed
- ◆ **DO NOT** make a right angle bend as shown
- ◆ A right angle bend can be made with a “swept” bend, or a “Mitered” bend
- ◆ Bends in a transmission line that are less than 90 degrees can also be mitered as shown

Microstrip Bends

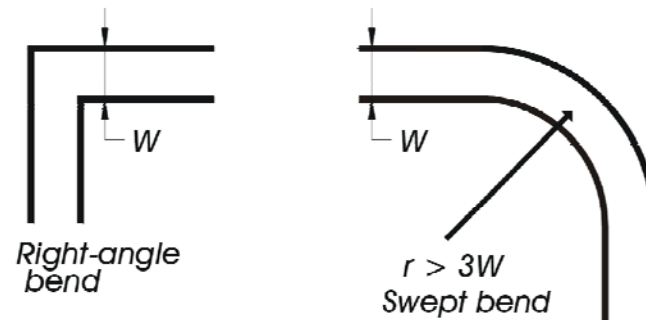


Mitered Bends

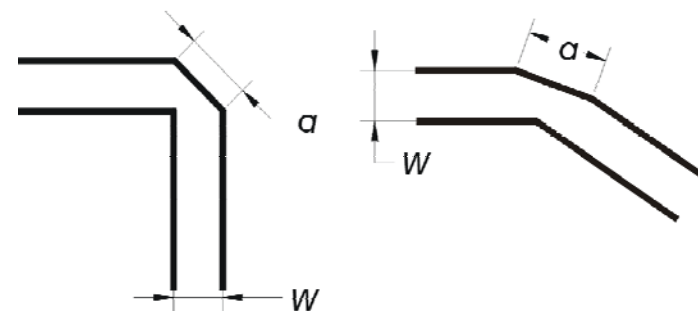

Ground Plane Layout Considerations

- ◆ **Do NOT have breaks or voids in the RF ground plane under, or over RF transmission lines**
- ◆ **Ground plane Vias around the RF circuits should be spaced closer than $1/20$ of a wavelength as a minimum, or closer if possible at the higher frequencies**
- ◆ **Use as large size vias as practical to minimize inductance**
- ◆ **“Stitch” the top and bottom ground planes together with as many vias as possible**
- ◆ **Signal and bias lines can be placed below RF ground plane layer followed by another “power” ground plane layer for the DC and digital returns**
- ◆ **Under components that require heat sinking, have solid ground plane with many closely spaced vias to transfer heat to all ground plane layers**

Ground Plane Layout Considerations

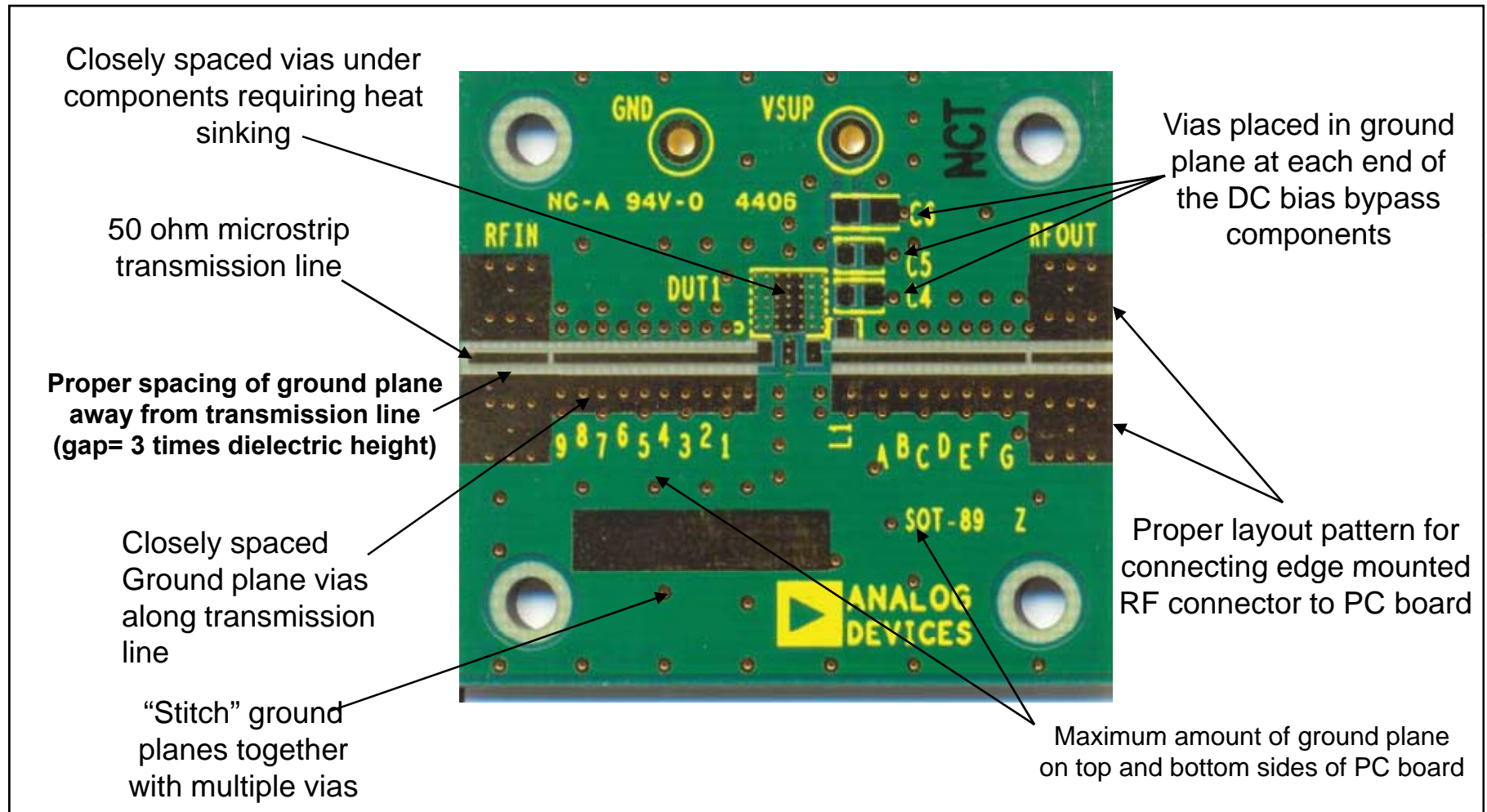




Developing a RF Printed Circuit Board


- ◆ **Draw Schematic of circuit to be placed on the PC board**
- ◆ **Have data sheets on components to indicate pkg size, pinouts, etc**
- ◆ **Determine location and orientation of active devices to optimize RF interfaces**
- ◆ **Place RF matching/terminating components around the device to provide the shortest possible connections**
- ◆ **Use as small of mounting pad as possible with discrete RF components to keep stray capacitance to a minimum**
- ◆ **Observe proper orientation of discrete components if placed next to each other to avoid coupling effects**
- ◆ **Separate inductors from each other in the layout, or place perpendicular to each other to prevent coupling of their magnetic fields**
- ◆ **Make sure that components that are connected to the ground plane have a via(s) as close to the end of the component as possible**
- ◆ **Use wide power traces if possible to lower DC losses and provide higher stray capacitance to ground(will also act as a RF bypass cap)**

Designing a RF Printed Circuit Board


- ◆ Draw Schematic of circuit

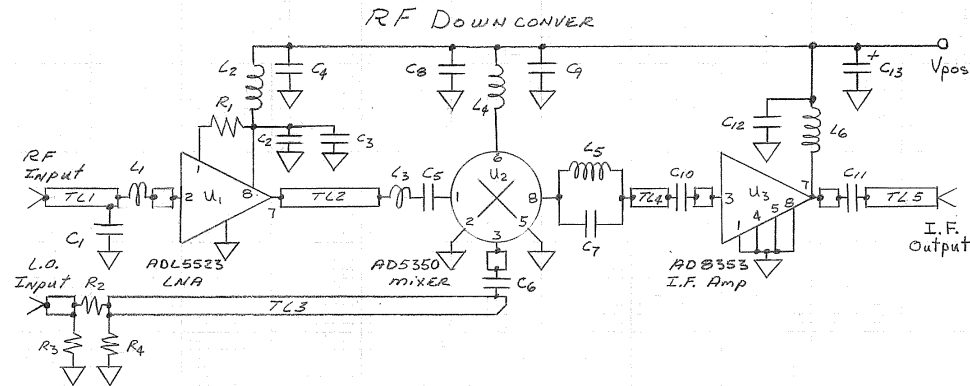

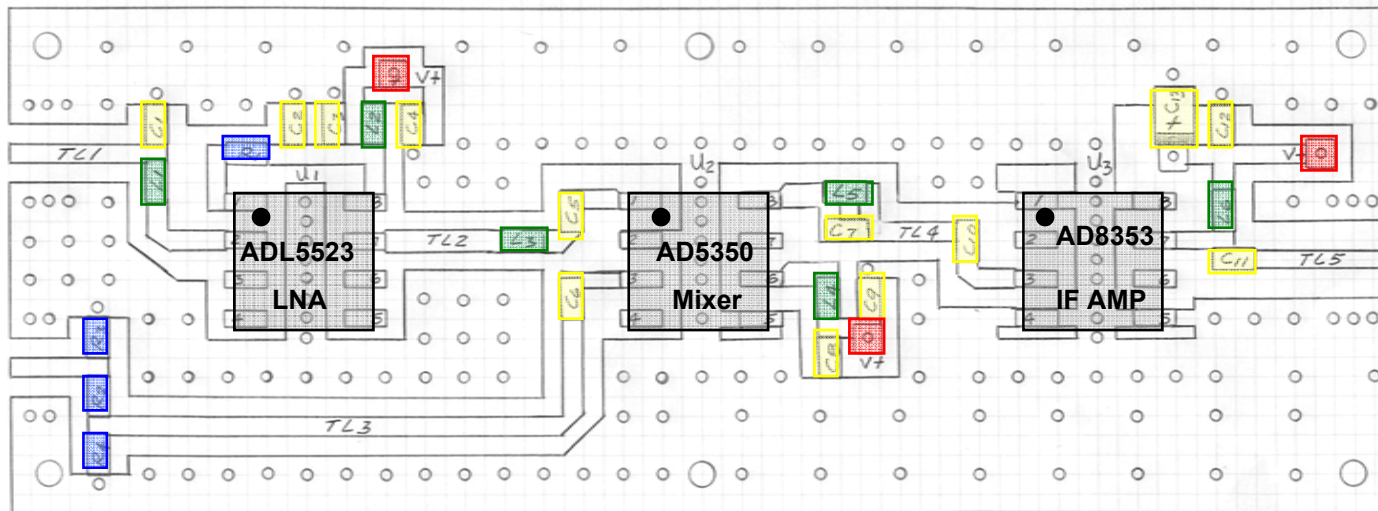- ◆ Draw layout of components to optimize parts placement and interconnections





Designing a RF Printed Circuit Board

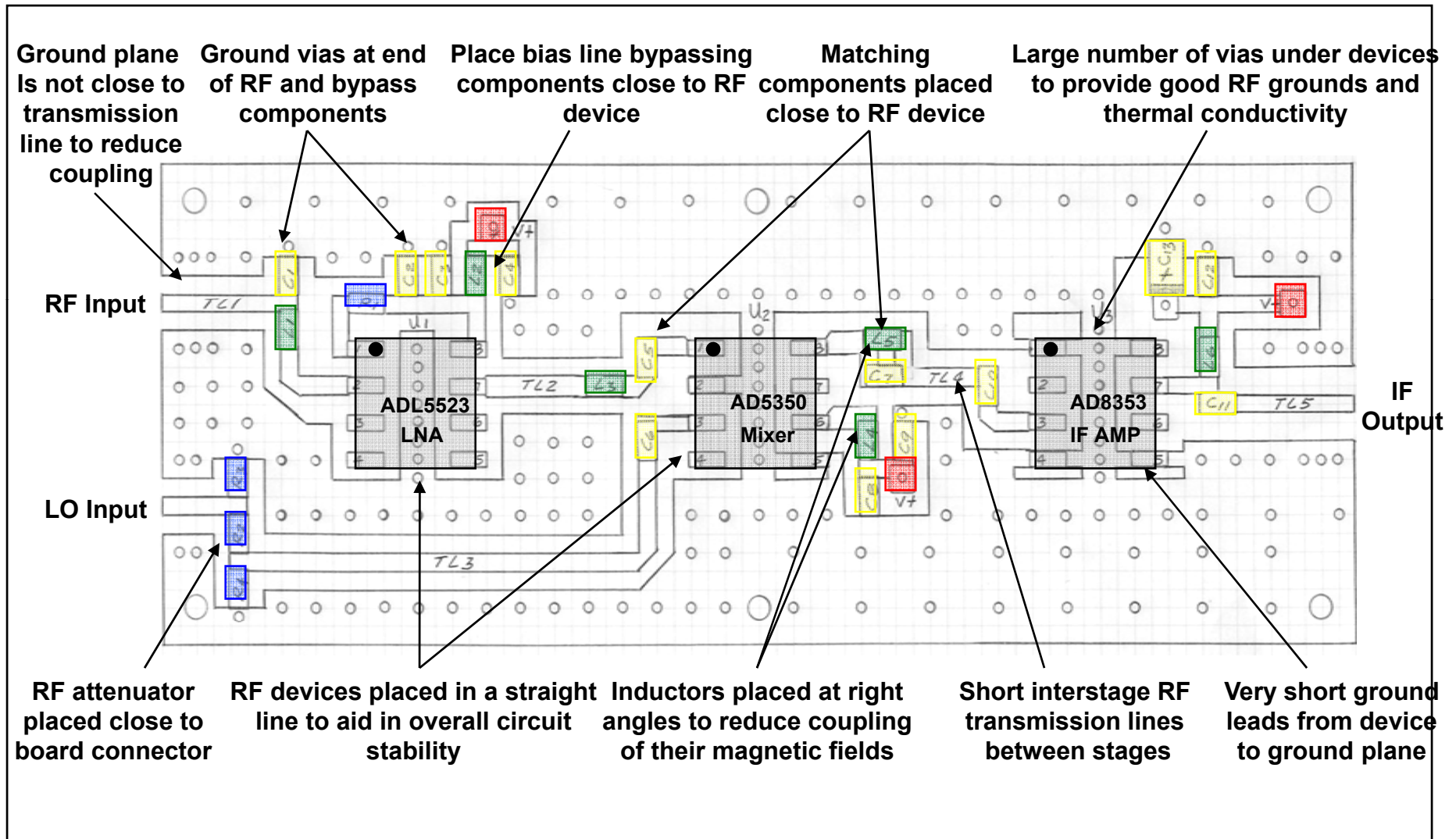

Shielding on RF Circuit Boards

- ◆ On multilayer circuit boards, use Stripline transmission lines if possible
- ◆ Route DC bias and signal traces on inner layers between the ground planes
- ◆ If required, place shielded enclosures around the RF stages on the board
- ◆ Be careful as to the physical size of the shielded enclosures, as it could become a resonate “cavity” at the higher frequencies
- ◆ Traces going to or from shielded sections should be routed on inner layers if possible

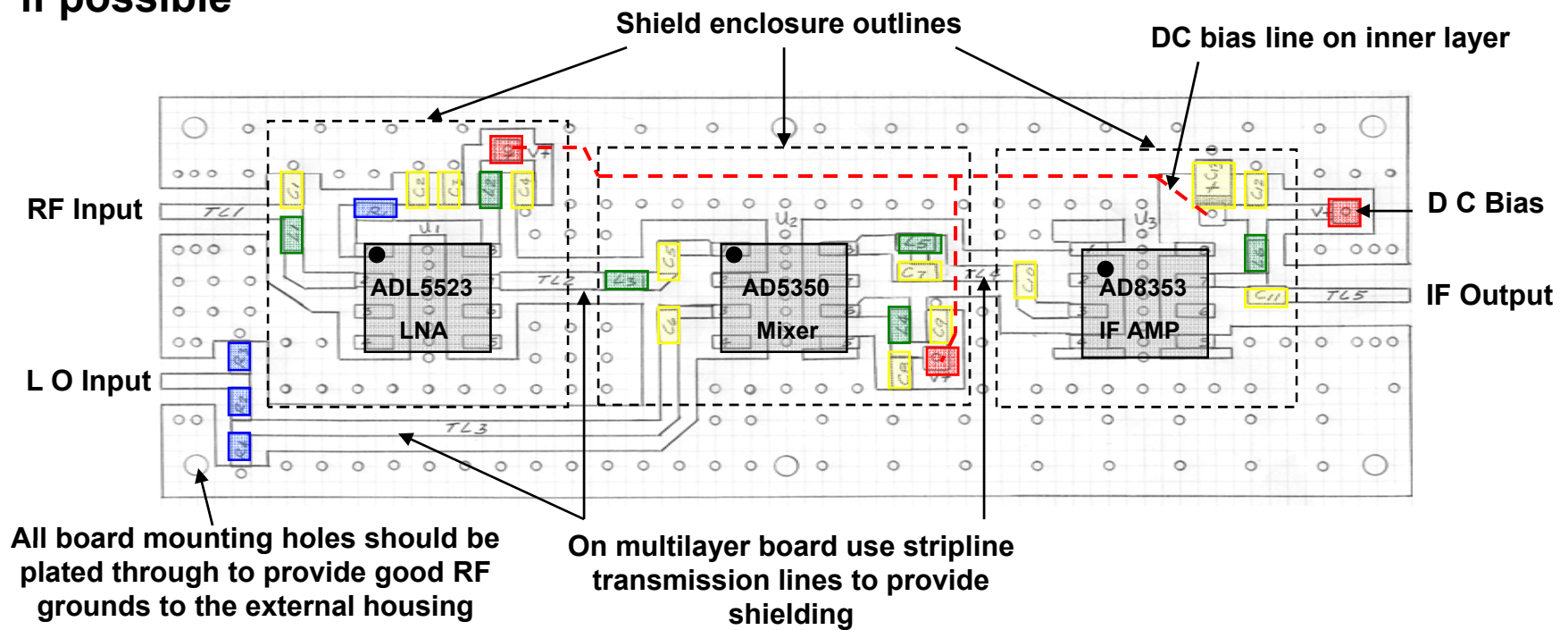

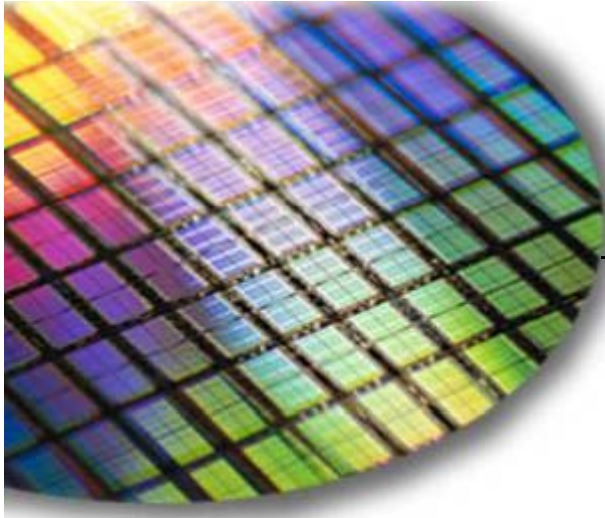

The World Leader in High Performance Signal Processing Solutions



Checking the Layout


Checking the Layout

- ◆ Design review
- ◆ Colleague review




Checking the Layout

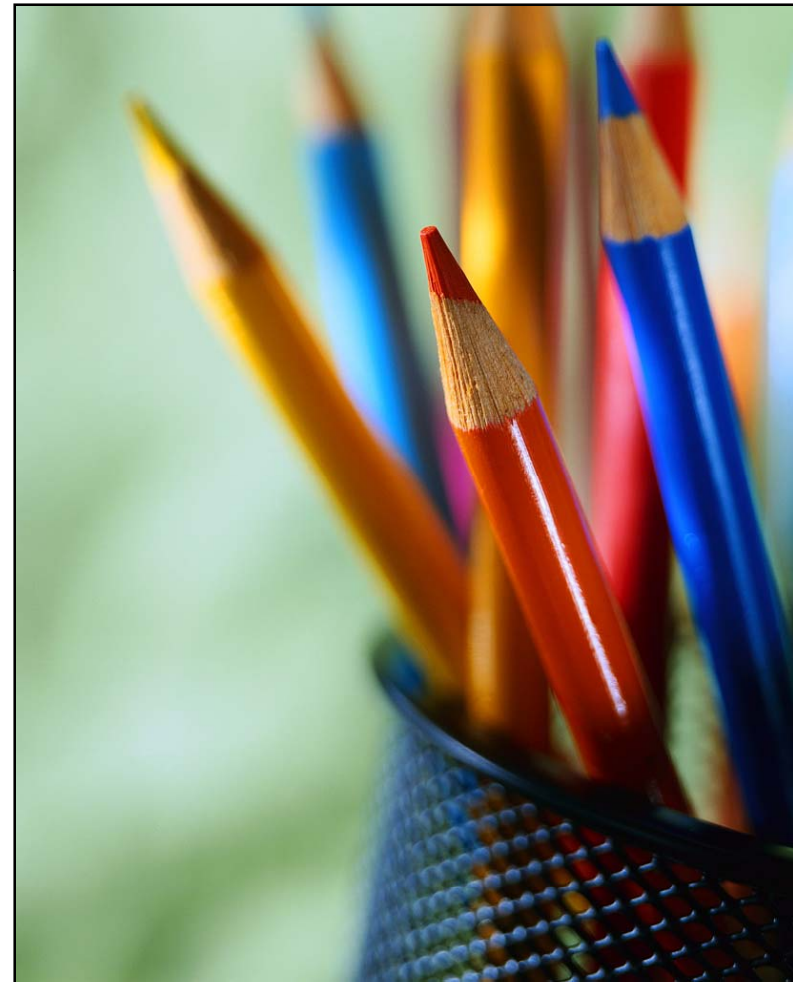- ◆ **Design review**
- ◆ **Colleague**
- ◆ **Colored pencils**
 - **Old School**
 - **Helps trace signal path on schematic and PCB**



Checking the Layout

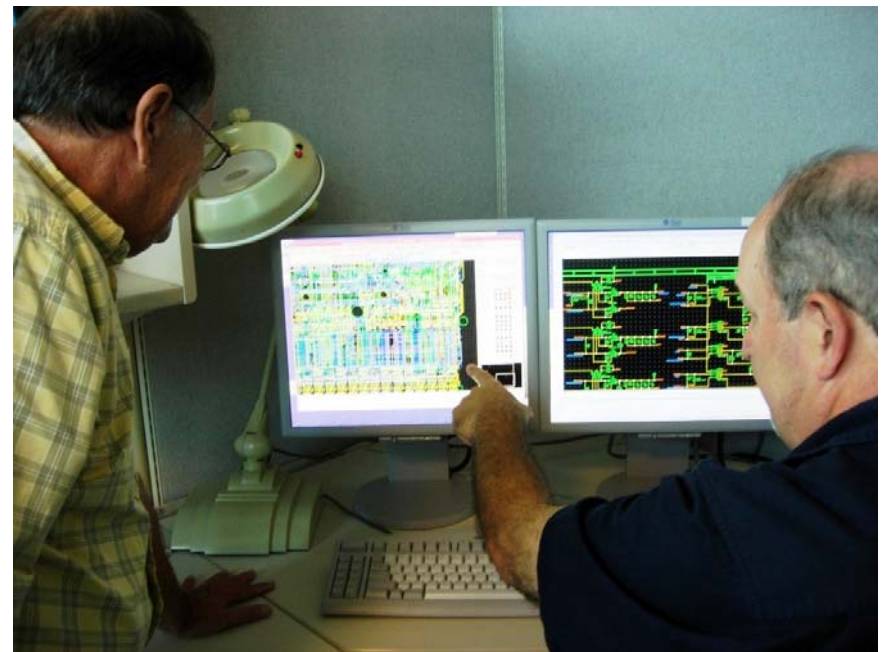
- ◆ **Design review**
- ◆ **Colleague**
- ◆ **Colored pencils**
 - Old School
 - Helps trace signal path on schematic and PCB
- ◆ **Sit with the designer when board corrections are made**
 - Trust no one
 - A change in one area of the board could inadvertently change another part of the board





Next Steps

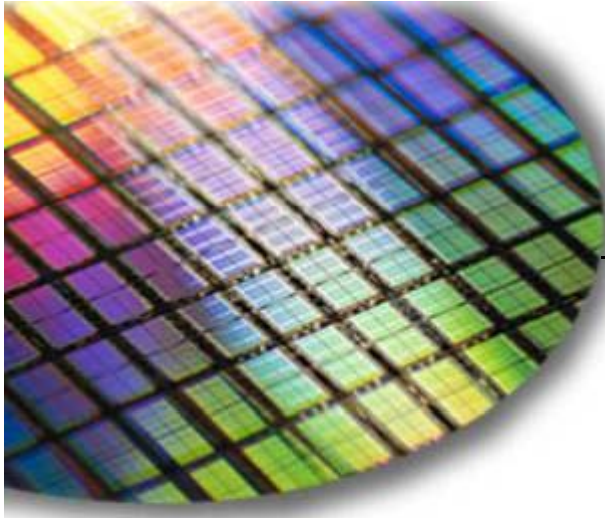- ◆ **Order Boards**
- ◆ **Build and test**
- ◆ **Evaluate performance**
- ◆ **Iterate and try again if required**
- ◆ **Successful High Speed/RF PCB design is a combination of education and experience**



The World Leader in High Performance Signal Processing Solutions



Summary



Summary

- ◆ **High speed PCB design requires deliberate thought and attention to detail!**
- ◆ **Load the schematic with as much information as possible**
- ◆ **Where you put individual components on the board is just as important as to where you put entire circuits**
- ◆ **Take the lead when laying out your board, don't leave anything to chance**
- ◆ **Use multiple capacitors for power supply bypassing**
- ◆ **Parasitics must be considered and dealt with**
- ◆ **Ground and Power planes play a key role in reducing noise and parasitics**
- ◆ **New packaging and pinout options allow for improved performance and more compact layouts**
- ◆ **There are many options for signal distribution, make sure you choose the right one for your application**
- ◆ **Check the layout and check it again**
- ◆ **Successful High Speed PCB design is a combination of education and experience and sometimes a little luck!**

Summary

- ◆ **Work directly with PC board designer as they most likely will not understand proper RF layout techniques**
- ◆ **Provide designer with a drawing of the location of the critical high frequency components and transmission lines**
- ◆ **Instruct the board designer that transmission line widths and lengths are very critical and must be exactly as calculated**
- ◆ **Place the components to minimize the length of RF interconnections**
- ◆ **Generally try to place components in a “straight line” to avoid feedback loops and instabilities**
- ◆ **Place circuit blocks such as oscillators, mixers, amplifiers in separate sections on the board if possible**
- ◆ **Do NOT mix digital, low level analog, or bias traces with RF interconnects to avoid unwanted coupling**
- ◆ **Locate the components operating at the highest frequencies close to board interconnects**
- ◆ **With the PC board designer, check, and recheck the layout before sending out for fabrication**

References

- ◆ Ardizzoni, John “**A Practical Guide to High-Speed Printed-Circuit-Board Layout**”
- ◆ Ardizzoni, John, “**Keep High-Speed Circuit-Board Layout on Track,**” *EE Times*, May 23, 2005.
- ◆ Brokaw, Paul, “**An IC Amplifier User’s Guide to Decoupling, Grounding, and Making Things Go Right for a Change,**” Analog Devices Application Note [AN-202](#).
- ◆ Brokaw, Paul and Jeff Barrow, “**Grounding for Low- and High-Frequency Circuits,**” Analog Devices Application Note [AN-345](#).
- ◆ Buxton, Joe, “**Careful Design Tames High-Speed Op Amps,**” Analog Devices Application Note [AN-257](#).
- ◆ DiSanto, Greg, “**Proper PC-Board Layout Improves Dynamic Range,**” *EDN*, November 11, 2004.
- ◆ Grant, Doug and Scott Wurcer, “**Avoiding Passive-Component Pitfalls,**” Analog Devices Application Note [AN-348](#)
- ◆ Johnson, Howard W., and Martin Graham, **High-Speed Digital Design, a Handbook of Black Magic,** Prentice Hall, 1993.
- ◆ Jung, Walt, ed., **Op Amp Applications Handbook,** Elsevier-Newnes, 2005 available on Amazon.com
- ◆ Kester, Walt, **The Data Conversion Handbook,** Elsevier-Newnes, 2005 available on Amazon.com

References

- ◆ Hartley, Rick, “[RF / Microwave PC Board Design and Layout](#)”
- ◆ Reed, Dale, [RF and Microwave Basics Impact PCB Design](#)
- ◆ Mercer, Sean, “[Minimizing RF PCB Electromagnetic Emissions](#),” RF Design, January 1999.
- ◆ Fabian Kung Wai Lee, “[Open notes on High-Speed Printed Circuit Board \(PCB\) Design \(August 2008\)](#)” Available at <http://persona.mmu.edu.my/~wllkung/ADS/ads.htm>”
- ◆ Howe, Harlan, “[Stripline Circuit Design](#)”
- ◆ Rogers Corporation, “[A Low cost Laminate for Wireless Applications](#),” Microwave Journal, Sept 1996
- ◆ Rogers Corporation, “[Microwave Impedance Calculator \(MWIJ 1.0\)](#)”



Contact Information

John Ardizzoni
Analog Devices, Inc.
804 Woburn Street
Wilmington, MA 01887-1017


Email:

john.ardizzoni@analog.com

Dennis Falls
Avnet Electronics Marketing
9200 Indian Creek Parkway
Suite 600
Overland Park, Kansas 66210

E-mail:

Dennis.falls@avnet.com

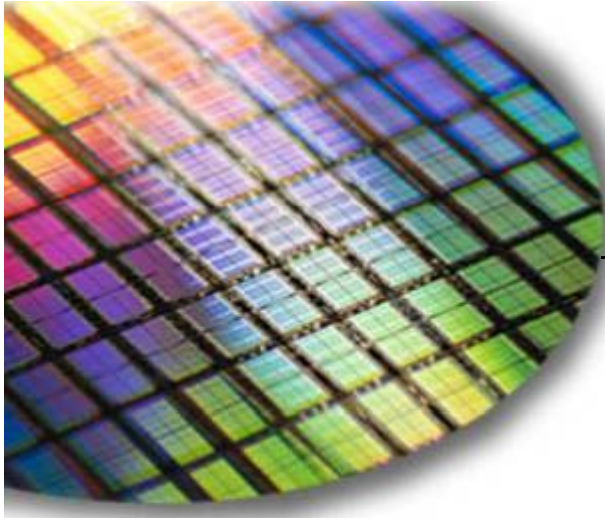

The World Leader in High Performance Signal Processing Solutions



Thank You