

PCB Power Decoupling Myths Debunked


Bruce Archambeault, PhD

Jay Diepenbrock

IBM, RTP, NC

barch@us.ibm.com


jaydiep@us.ibm.com

 

Conventional Wisdom

- Need a variety of capacitance values to maintain low impedance over frequency range
- Many capacitors of one value is better than many values
- Place capacitors close to ICs as possible
- Location does not matter
- Spread capacitors over entire board

Power Plane Noise Control

 

What is Capacitance?

$$C = \frac{Q}{V}$$


$$Q = CV$$

- Capacitance is the ability of a structure to hold charge (electrons) for a given voltage
- Amount of charge stored is dependant on the size of the capacitance (and voltage)

Note: Capacitance has no frequency dependence!

High Frequency Capacitors

- Myth or Fact?

 


It's really the inductance that matters!

Capacitance and Inductance


- **Capacitance** → amount of charge stored
- **Inductance** → speed that the charge can be delivered from capacitor

Decoupling Capacitor Mounting

 - Keep planes as close to capacitor pads as possible




0603 Size Cap Typical Mounting

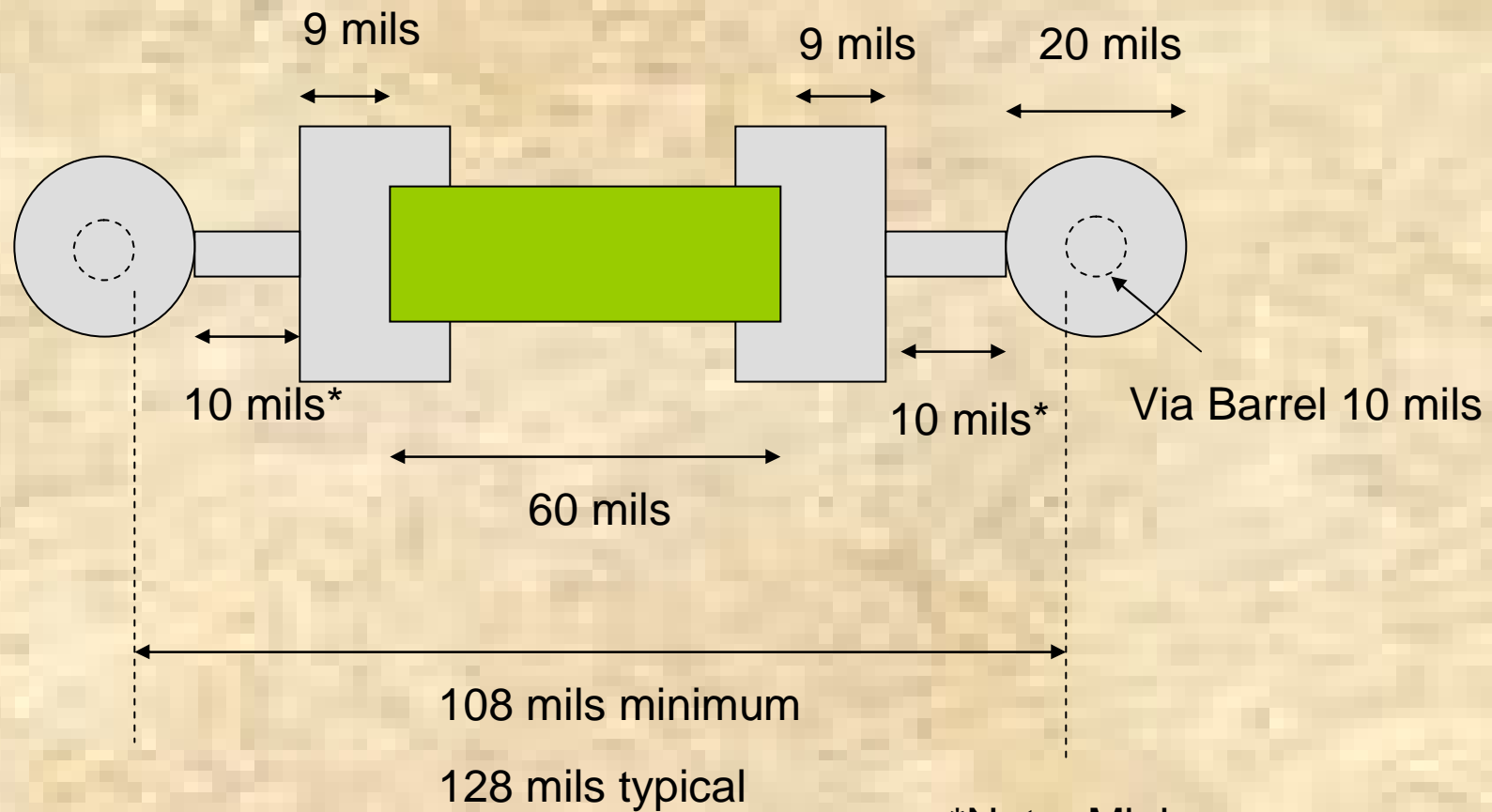

*Note: Minimum distance is 10 mils but more typical distance is 20 mils

0402 Size Cap Typical Mounting

 

*Note: Minimum distance is 10 mils but more typical distance is 20 mils


Connection Inductance for Typical Capacitor Configurations with 10 mils from Capacitor Pad to Via Pad

| Distance into board to planes (mils) | 0805 typical (148 mils between via barrels) | 0603 typical (128 mils between via barrels) | 0402 typical (106 mils between via barrels) |
|--------------------------------------|---|---|---|
| 10 | 1.2 nH | 1.1 nH | 0.9 nH |
| 20 | 1.8 nH | 1.6 nH | 1.3 nH |
| 30 | 2.2 nH | 1.9 nH | 1.6 nH |
| 40 | 2.5 nH | 2.2 nH | 1.9 nH |
| 50 | 2.8 nH | 2.5 nH | 2.1 nH |
| 60 | 3.1 nH | 2.7 nH | 2.3 nH |
| 70 | 3.4 nH | 3.0 nH | 2.6 nH |
| 80 | 3.6 nH | 3.2 nH | 2.8 nH |
| 90 | 3.9 nH | 3.5 nH | 3.0 nH |
| 100 | 4.2 nH | 3.7 nH | 3.2 nH |

Connection Inductance for Typical Capacitor Configurations with 50 mils from Capacitor Pad to Via Pad


| Distance into board to planes (mils) | 0805 (208 mils between via barrels) | 0603 (188 mils between via barrels) | 0402 (166 mils between via barrels) |
|--------------------------------------|--|--|--|
| 10 | 1.7 nH | 1.6 nH | 1.4 nH |
| 20 | 2.5 nH | 2.3 nH | 2.0 nH |
| 30 | 3.0 nH | 2.8 nH | 2.5 nH |
| 40 | 3.5 nH | 3.2 nH | 2.8 nH |
| 50 | 3.9 nH | 3.5 nH | 3.1 nH |
| 60 | 4.2 nH | 3.9 nH | 3.5 nH |
| 70 | 4.5 nH | 4.2 nH | 3.7 nH |
| 80 | 4.9 nH | 4.5 nH | 4.0 nH |
| 90 | 5.2 nH | 4.7 nH | 4.3 nH |
| 100 | 5.5 nH | 5.0 nH | 4.6 nH |

Via Configuration Can Change Inductance

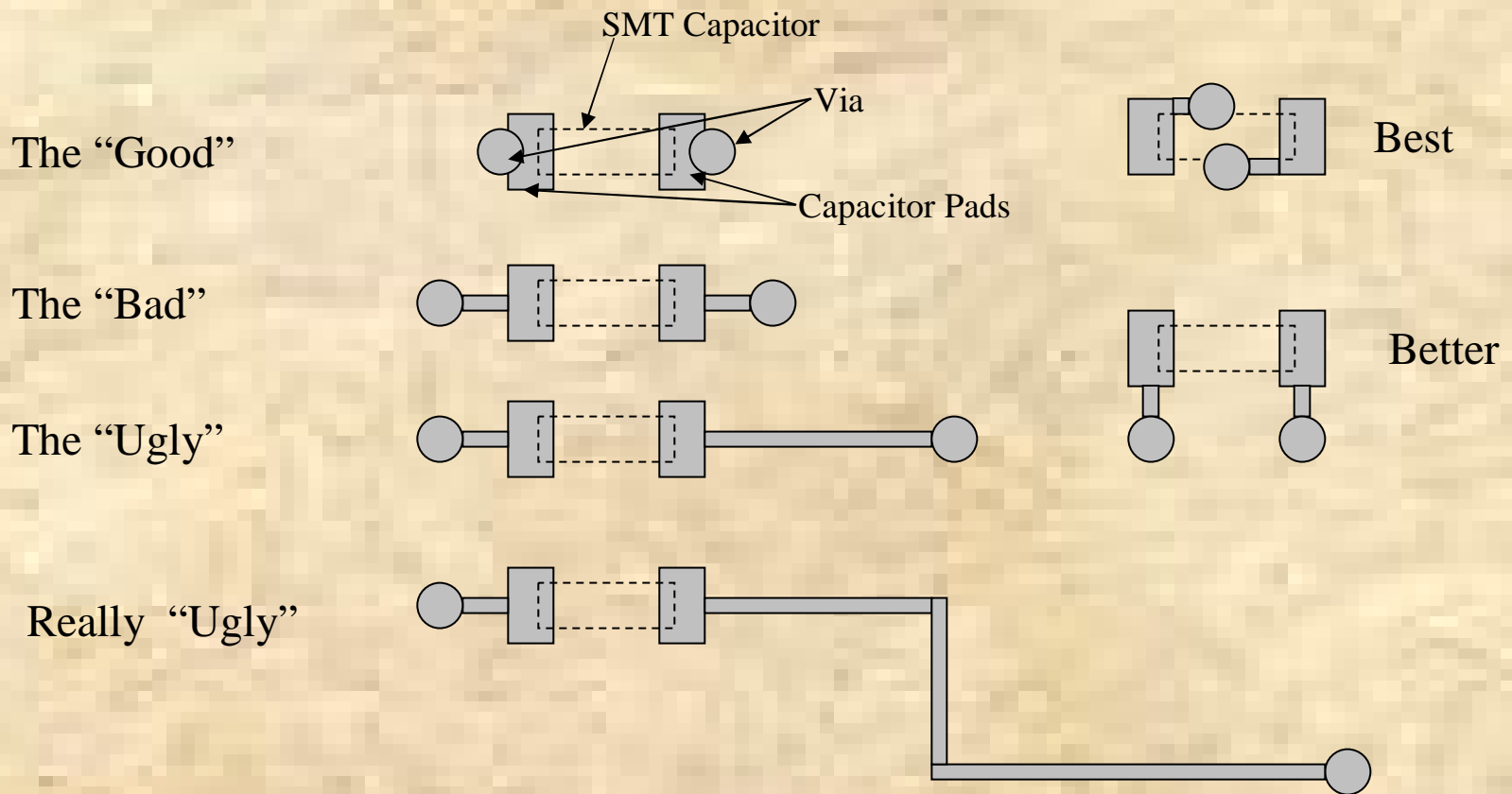

Comparison of Decoupling Capacitor Via Separation Distance Effects


0.1 μF Capacitor

 

| Via separation, mils | Inductance, nH | Impedance @1 GHz, Ohms |
|----------------------|----------------|------------------------|
| 20 | 0.06 | 0.41 |
| 40 | 0.21 | 1.3 |
| 60 | 0.36 | 2.33 |
| 80 | 0.5 | 3.1 |
| 100 | 0.64 | 4.0 |
| 150 | 1.0 | 6.23 |
| 200 | 1.4 | 8.5 |
| 300 | 2.1 | 12.7 |
| 400 | 2.75 | 17.3 |
| 500 | 3.5 | 21.7 |


Example #1

Low Cap Connection Inductance

 


Example #2

Hi Cap Connection Inductance

 


Example #3

Lower Cap Connection Inductance

 


Example #4

High Cap Connection Inductance

 

Capacitor Connection Inductance Ratio

 

| Power/GND plane spacing, (mils) | via diameter, (mils) | L ₂ (nH) |
|---------------------------------|----------------------|---------------------|
| 10 | 10 | 0.32 |
| 10 | 13 | 0.304 |
| 10 | 25 | 0.27 |
| 35 | 10 | 1.1 |
| 35 | 13 | 1.07 |
| 35 | 25 | 0.95 |

| 62mil brd centered plane spacing, mils | 0603 SMT L3' (nH) | L3/L2 | L3/L2 w/extra 100 mil trace length | L3/L2 w/extra 200 mil trace length | L3/L2 w/extra 300 mil trace length |
|--|-------------------|-------|------------------------------------|------------------------------------|------------------------------------|
| 10 | 1.66 | 6.75 | 9.13 | 11.50 | 13.88 |
| 35 | 0.92 | 1.29 | 1.98 | 2.67 | 3.36 |

For local decoupling need L3/L2 < 3

Decoupling Must be Analyzed in Different Ways for Different Functions


- EMC
 - Resonance big concern
 - Requires STEADY-STATE analysis
 - Frequency Domain
 - Transfer function analysis
 - Eliminate noise along edge of board due to ASIC/IC located far away

Decoupling Must be Analyzed in Different Ways for Different Functions




- Provide Charge to ASIC/IC
 - Requires time-limited analysis
 - Charge must get to the IC **during the time it is needed!**
 - Charge will NOT travel from far corners of the board fast enough
 - Local decoupling capacitors dominate

Decoupling Capacitor Mounting

 
- Keep as to planes as close to capacitor pads as possible



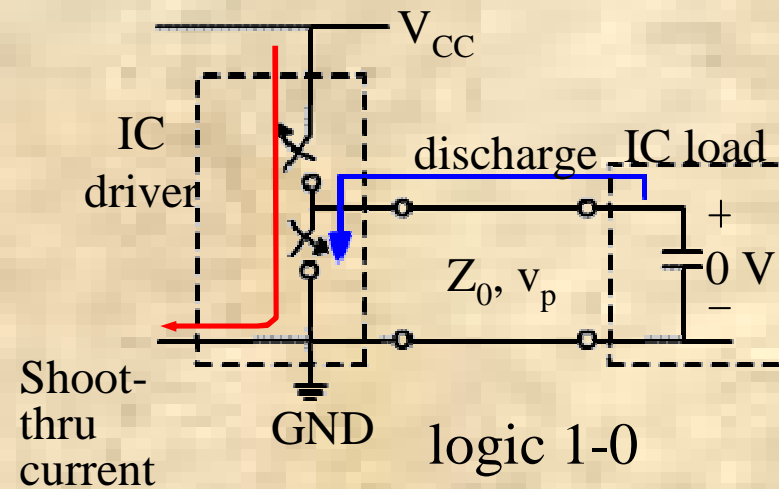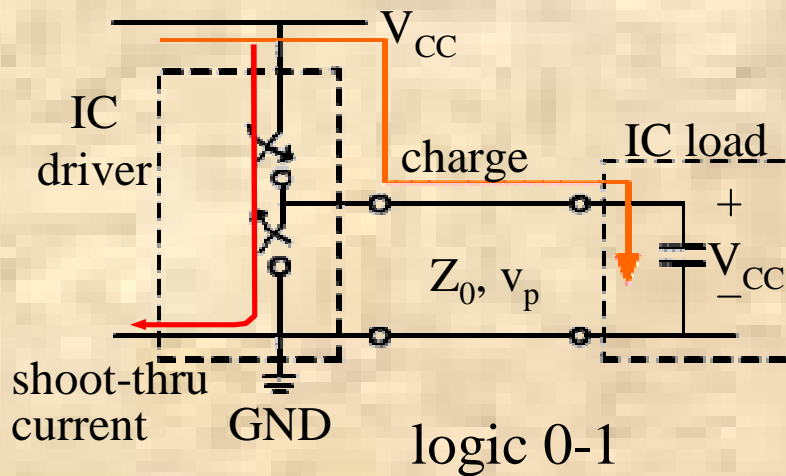 
Current in IC During Logic Transitions (CMOS)




Typical PCB Power Delivery

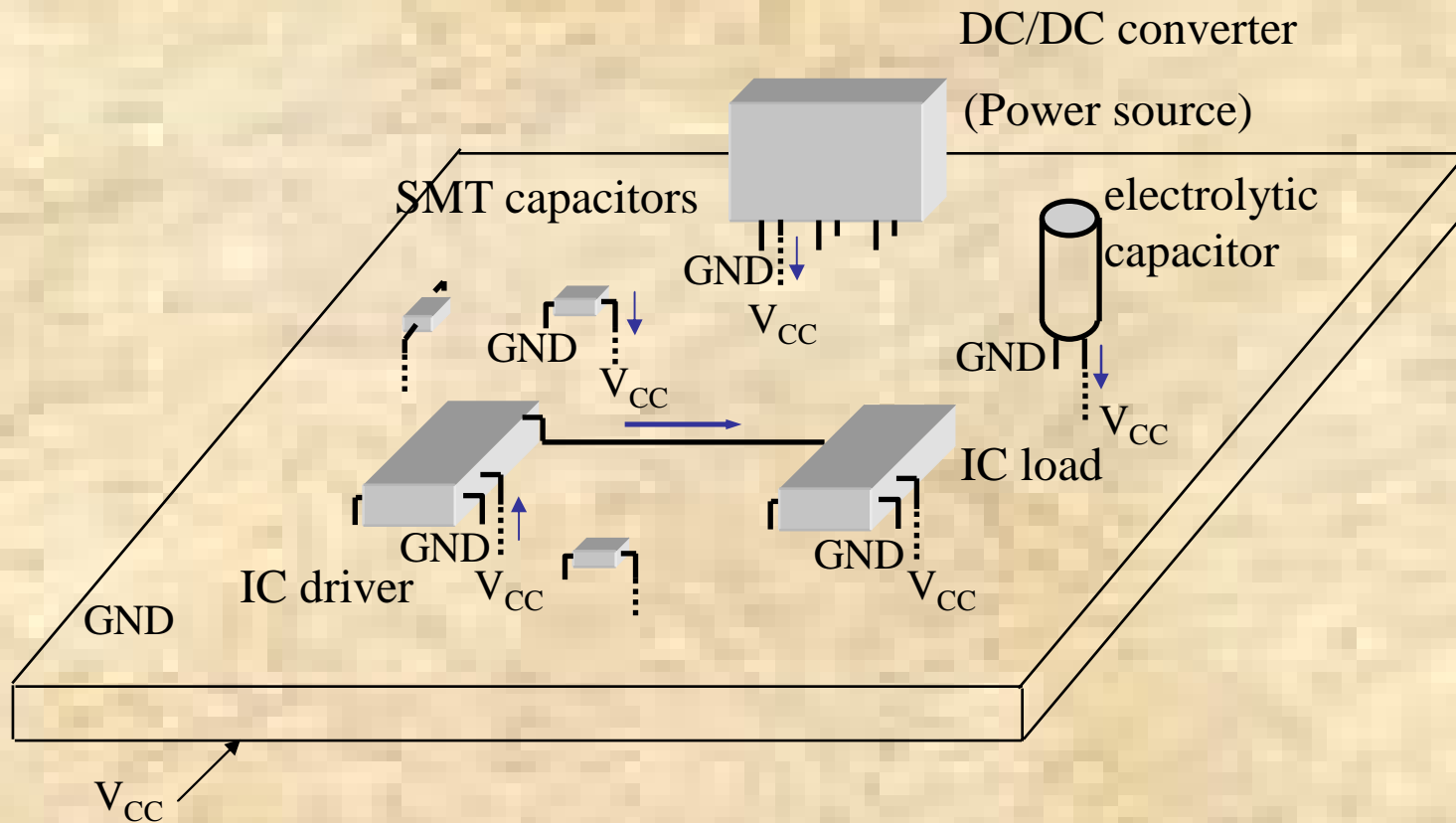

 Equivalent Circuit for Power Current Delivery to IC




Power Bus Charging Hierarchy

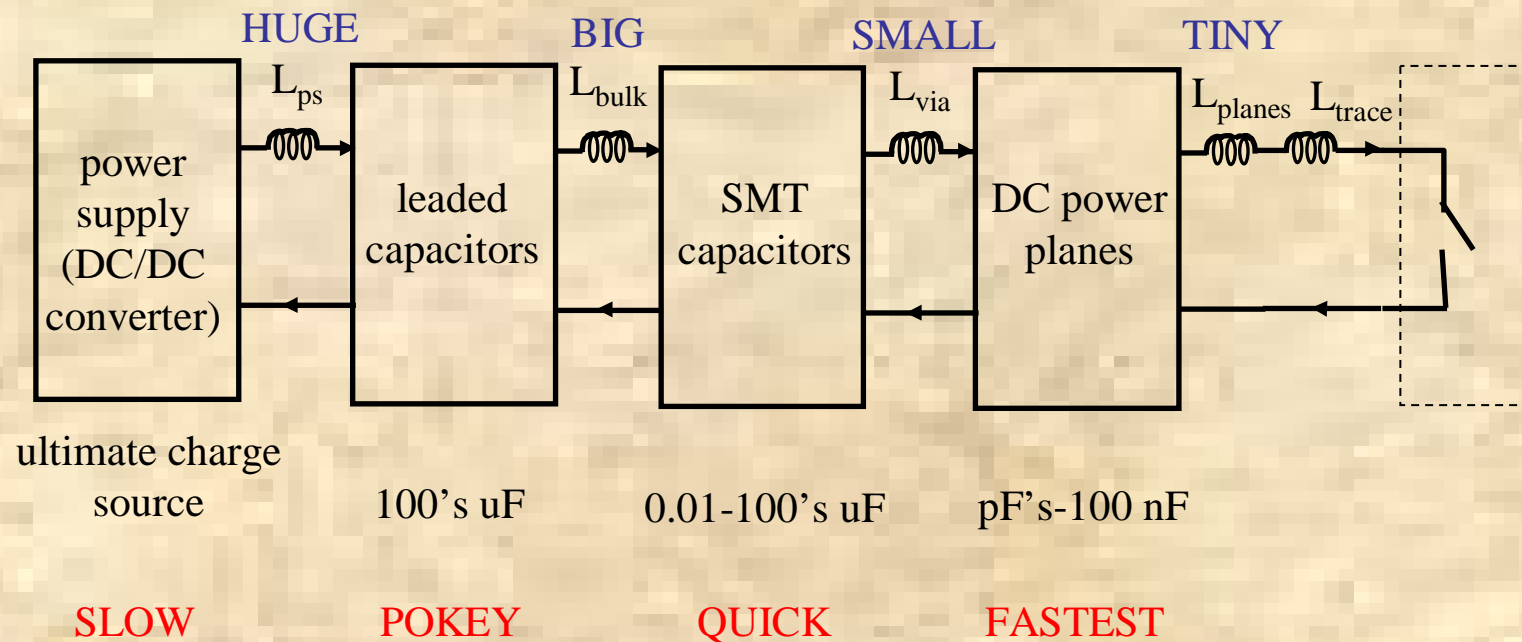

Traditional Analysis #1

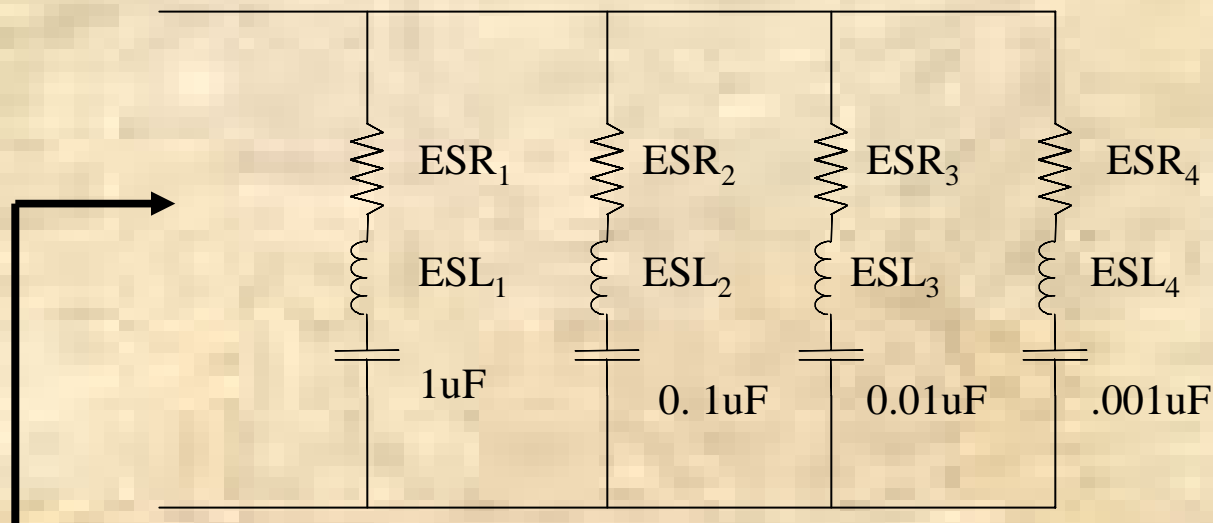
- Use impedance of capacitors in parallel



Impedance to IC
power/gnd pins


**No Effect of Distance Between Capacitors
and IC Included!**

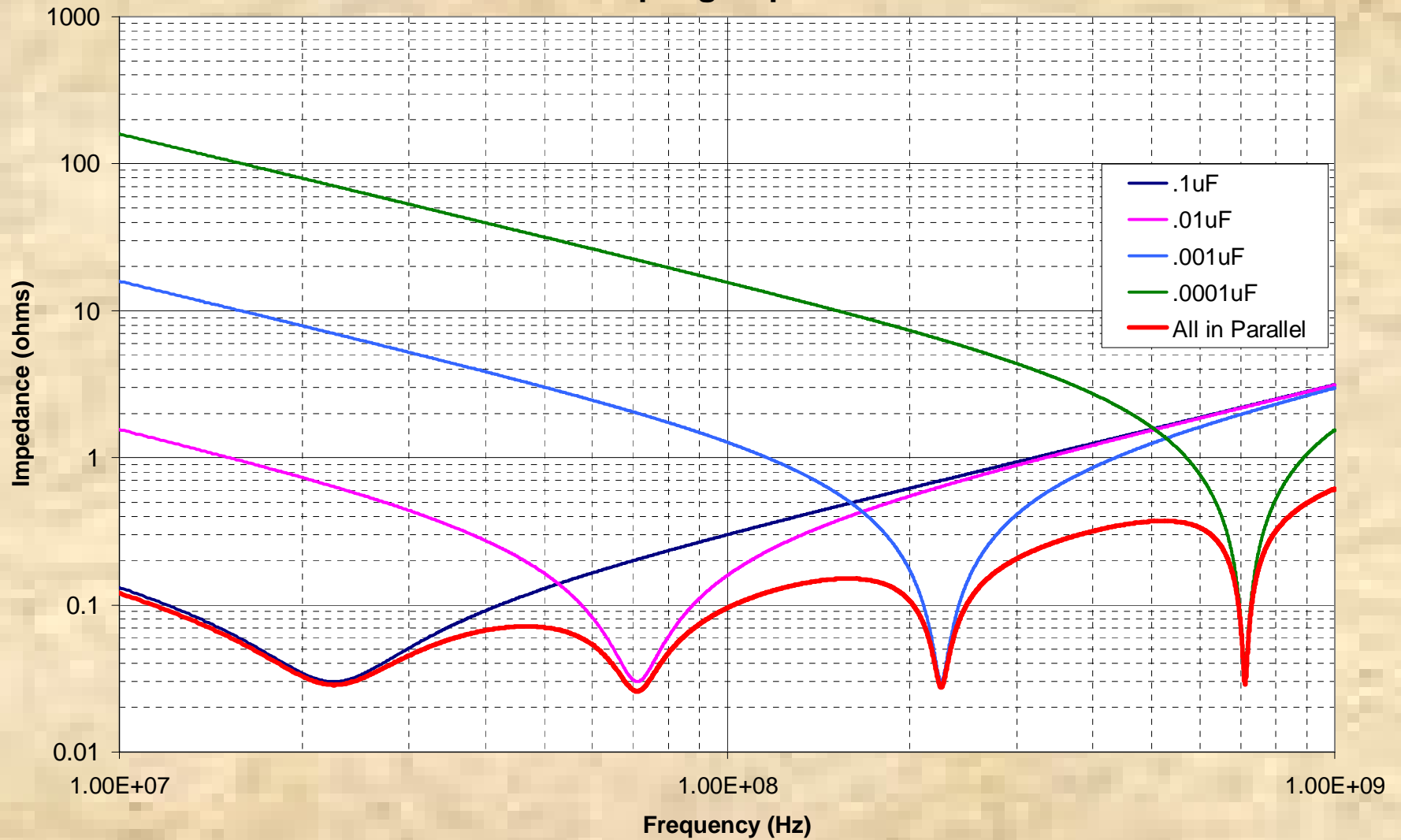Traditional Impedance Calculation for Four Decoupling Capacitor Values




Traditional Analysis #2

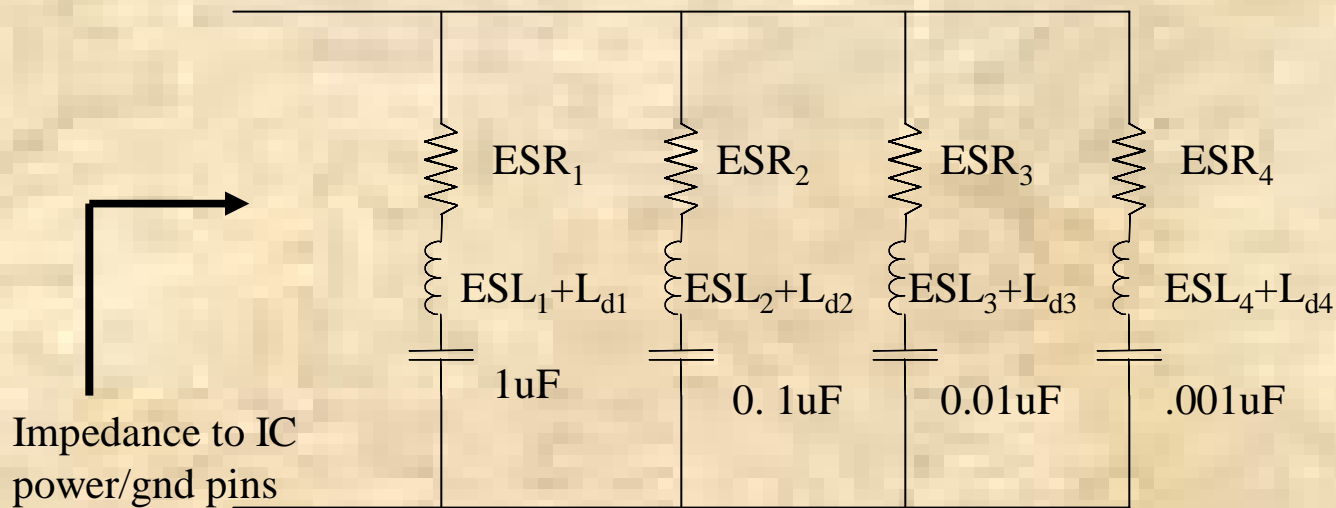- Calculate loop area – Traditional loop Inductance formulas
 - Which loop area? Which size conductor




Over Estimates L and Ignores Distributed Capacitance

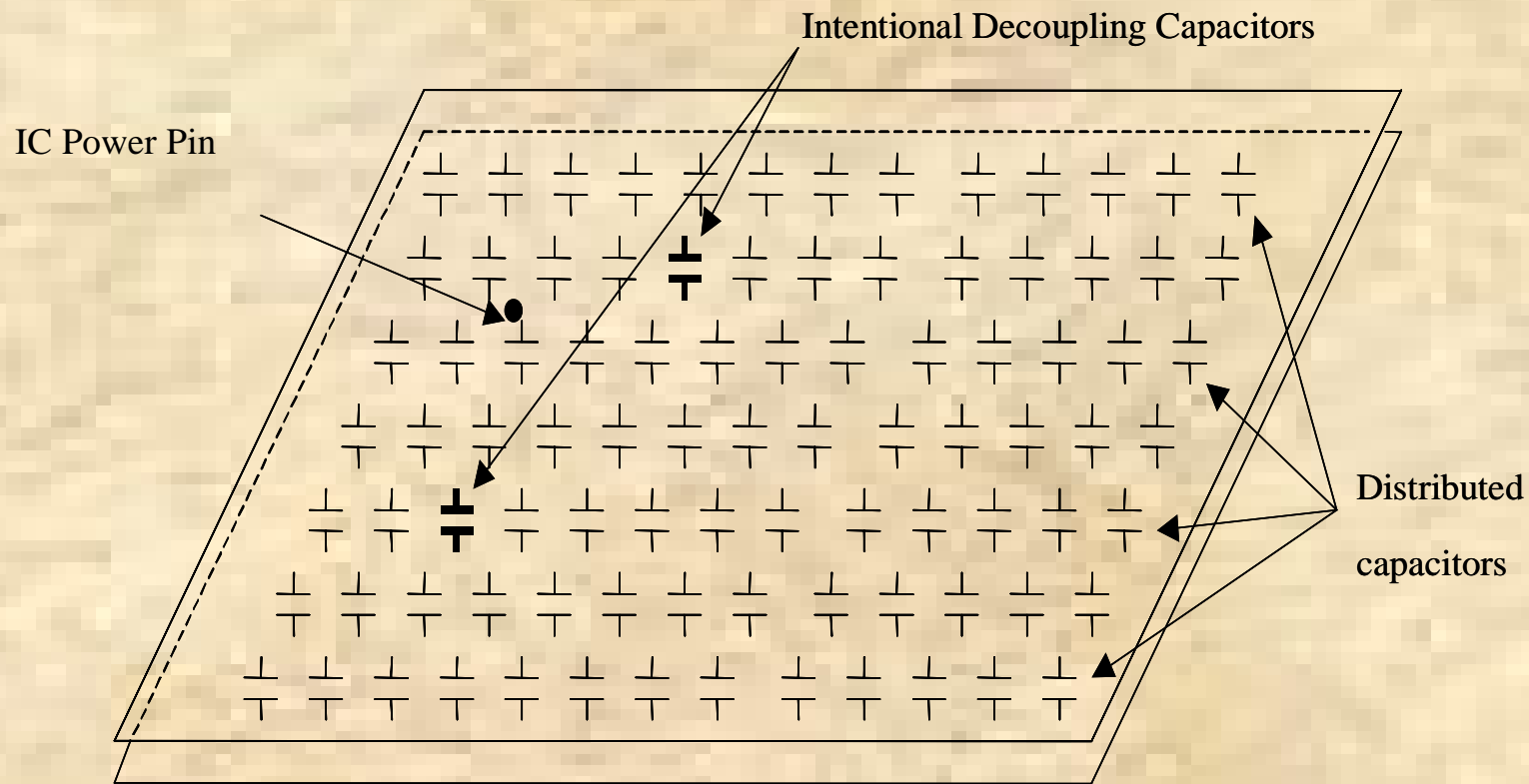More Accurate Model Includes Distributed Capacitance



Distributed Capacitance Schematic

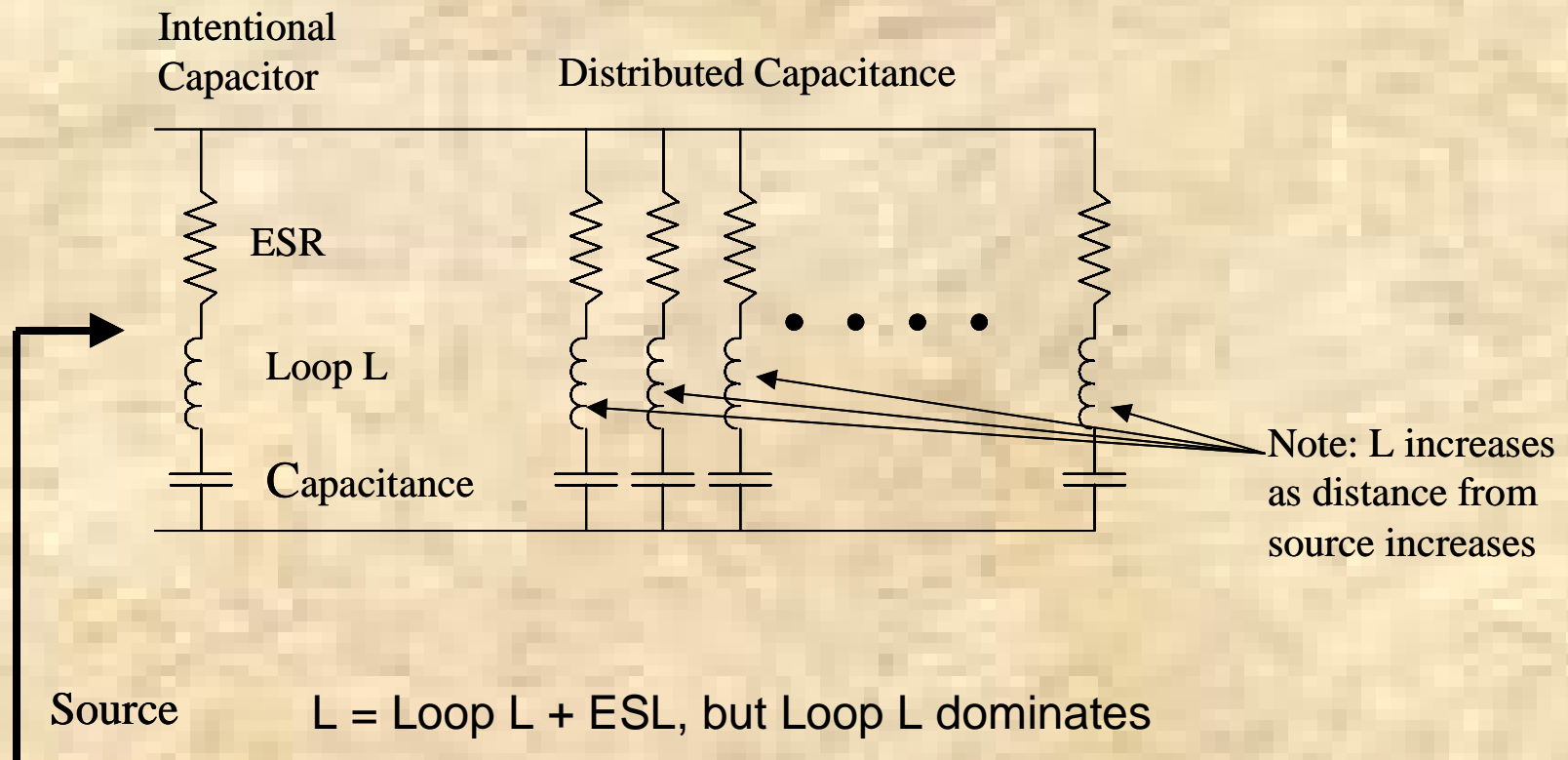


Effect of Distributed Capacitance

- Can NOT be calculated/estimated using traditional capacitance equation – need to use full-wave technique
- Displacement current amplitude changes with position and distance from the source


Sample Parameters for Comparison to Measurements

- Dielectric thickness = 35 mils
- Dielectric constant = 4.5, Loss tan = 0.02
- Copper conductivity = 5.8×10^7 S/m

 
Impedance at Port #1
Single 0.01 uF Capacitor at Various Distances (35mil Dielectric)



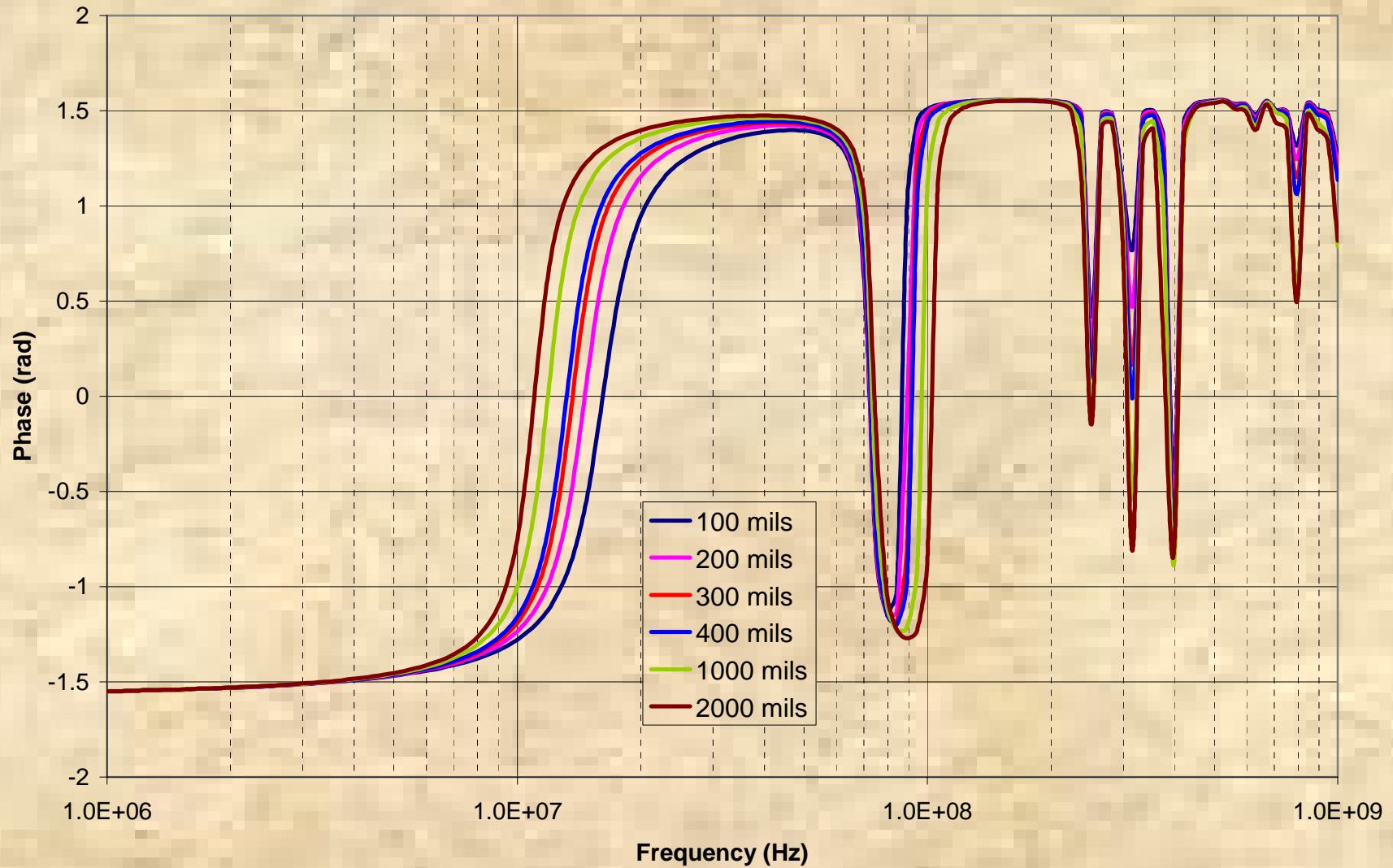Z11 Phase Comparison as Capacitor distance Varies for 35 mils FR4 ESL = 0.5nH



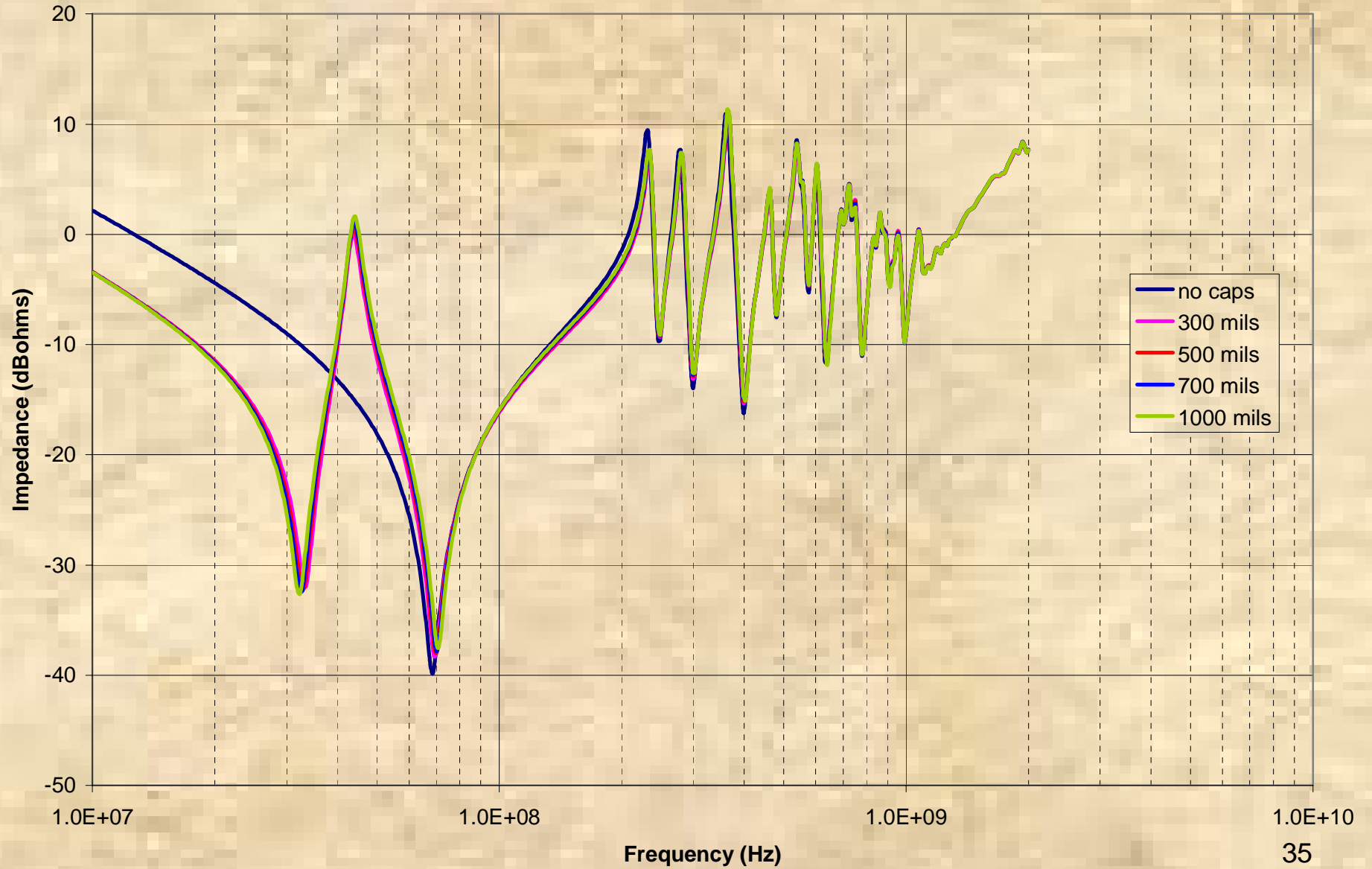Impedance at Port #1 Single 0.01 uF Capacitor at Various Distances (10mil Dielectric)




Effect of Capacitor Value??

- Need enough charge to supply need
- Depends on connection inductance

Charge Depletion

- IC draws charge from planes
- Capacitors will re-charge planes
 - Location **does** matter!

Model for Plane Recharge Investigations

 


Port 2 represents IC current draw

Charge Between Planes vs. Charge Drawn by IC


Board total charge : $C \cdot V = 3.5\text{nF} \cdot 3.3\text{V} = 11\text{nC}$

Pulse charge 5A peak : $I \cdot dt/2 = (1\text{ns} \cdot 5\text{A})/2 = 2.5\text{nC}$


Charge Depletion vs. capacitor distance

 

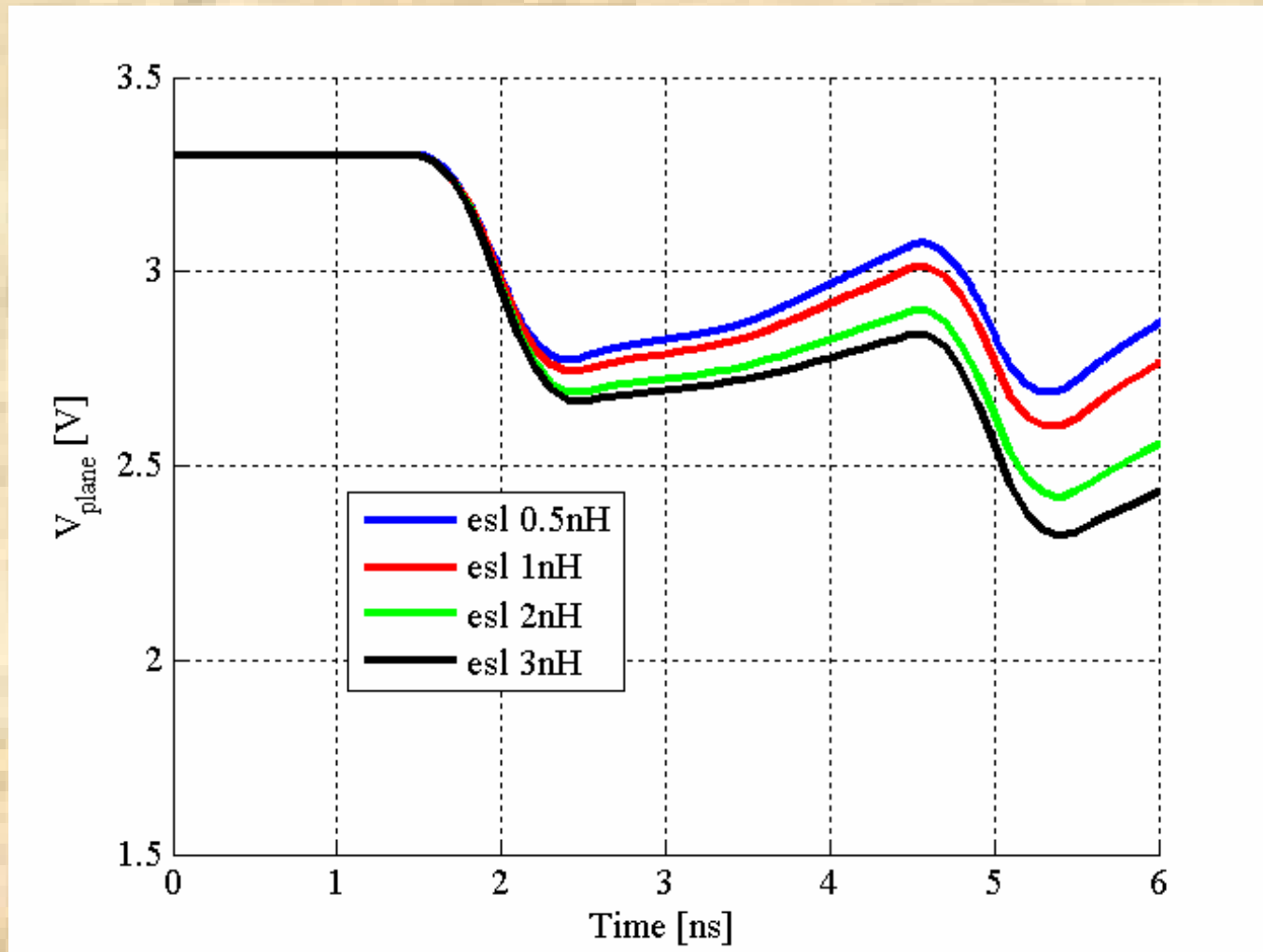Charge Depletion for Capacitor @ 400 mils for various connection Inductance



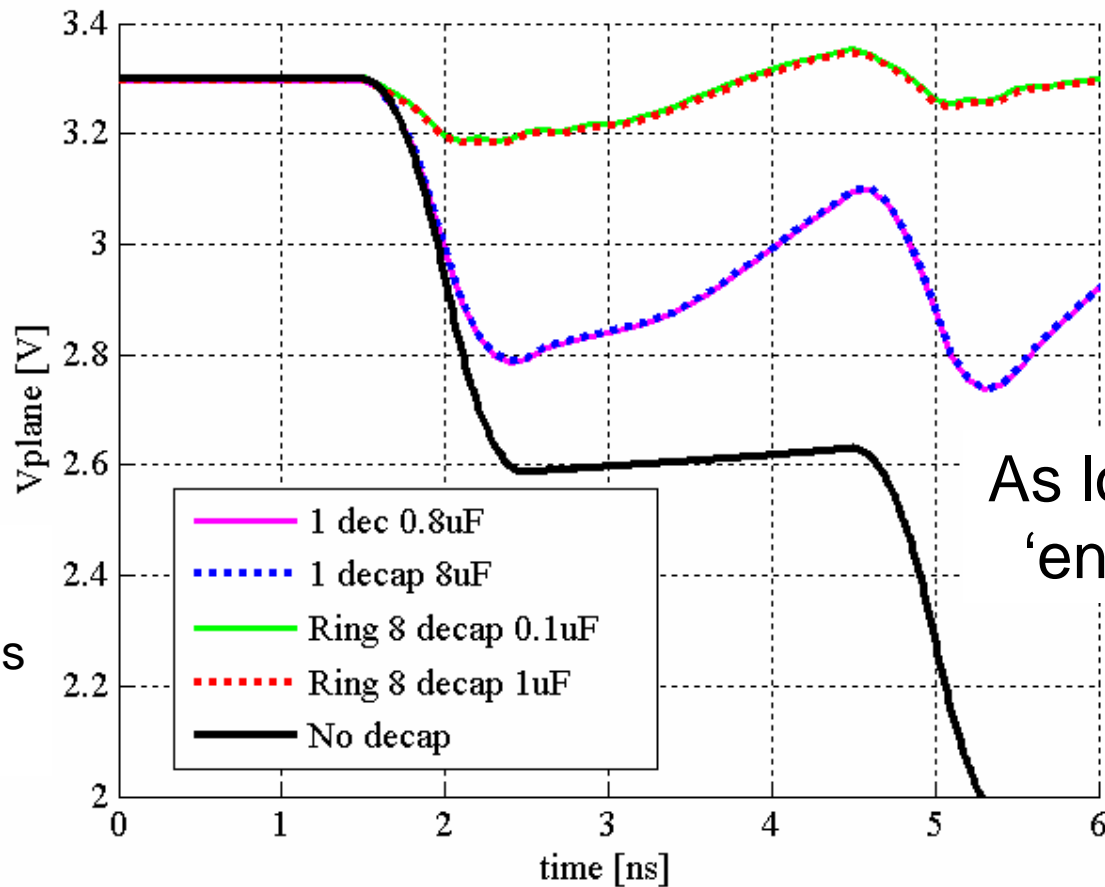Noise Voltage is INDEPENDENT of Amount of Capacitance!




As long as there is 'enough' charge

Dist=400 mils
ESR=30mOhms
ESL=0.5nH


Capacitor Locations and Orientation

- Many myths about decoupling capacitor design
- Proximity between capacitors has been shown to impact capacitors' performance
- Wish to quantify these various effects, not just show which is best
- Current (not voltage) important for decoupling capacitor analysis

 What Happens if a 2nd Decoupling Capacitor is placed near the First Capacitor?



Second Via Around a circle

 

$$d_1 = R$$

$$d_2 = 2R \sin \frac{\theta}{2}$$

$$\frac{\mu d}{4\pi} \ln \left(\frac{(R+r)^2 (d_1+r)^2}{r^3 (d_2+r)} \right) - \frac{\mu d}{4\pi} \frac{\ln^2 \left(\frac{d_1+r}{R+r} \right)}{\ln \left(\frac{d_2+r}{r} \right)}$$

$$= \frac{\mu d}{4\pi} \ln \left(\frac{(R+r)^4}{(2R \sin(\theta/2) + r)r^3} \right)$$

R : distance between Port 1 and Port 2
in mil

r : radius for all ports in mil

d : thickness of dielectric layer in mil

d_1 : distance between Port 3 and Port 1
in mil


d_2 : distance between Port 2 and Port 3
in mil

θ : angle as shown in the figure in
degree


Courtesy of Jinguok Kim, Jun
Fan, Jim Drewniak

Missouri University of Science
and Technology

 
**Effective Inductance for Various Distances to Decoupling Capacitor
With Second Capacitor (Via) Equal Distance Around Circle
Plane Separation = 35 mil -- Via Diameter = 20 mil**






 
**Effective Inductance for Various Distances to Decoupling Capacitor
With Second Capacitor (Via) Equal Distance Around Circle
Plane Separation = 5 mil -- Via Diameter = 20 mil**





 
Understanding Inductance Effects and Proximity




Current Density - simulation

    

   
DUT for Experimental Validation (Single Plane pair)




Shorting via

 

1 shorting


 


2 shorting with 30°

 

2 shorting with 180°

  Experimental Validation (Single Plane Pair)



- Even in the case with two shorting vias at opposite sides ($\theta=180^\circ$), the inductance value is 68.8% of that with one shorting via
- As two shorting vias get closer together, mutual inductance between two shorting vias increases.



$$\frac{\mu d}{4\pi} \ln \left(\frac{(R+r)^4}{(2R \sin(\theta/2) + r)r^3} \right)$$

Equation



Observations

- Added via (capacitor) does not lower effective inductance to 50%
 - 70-75% of original single via case
- Thicker dielectric results in higher inductance

Multiple Capacitors

 
 


Via Spacing

  


| Distance to Planes (mils) | 40 mil Spacing (nH) | 0402 SMT (nH) | 0603 SMT (nH) |
|---------------------------|---------------------|---------------|---------------|
| 10 | 0.3 | 0.9 | 1.1 |
| 20 | 0.5 | 1.3 | 1.6 |
| 30 | 0.75 | 1.6 | 1.9 |
| 40 | 0.95 | 1.9 | 2.2 |






Possible Configurations

  

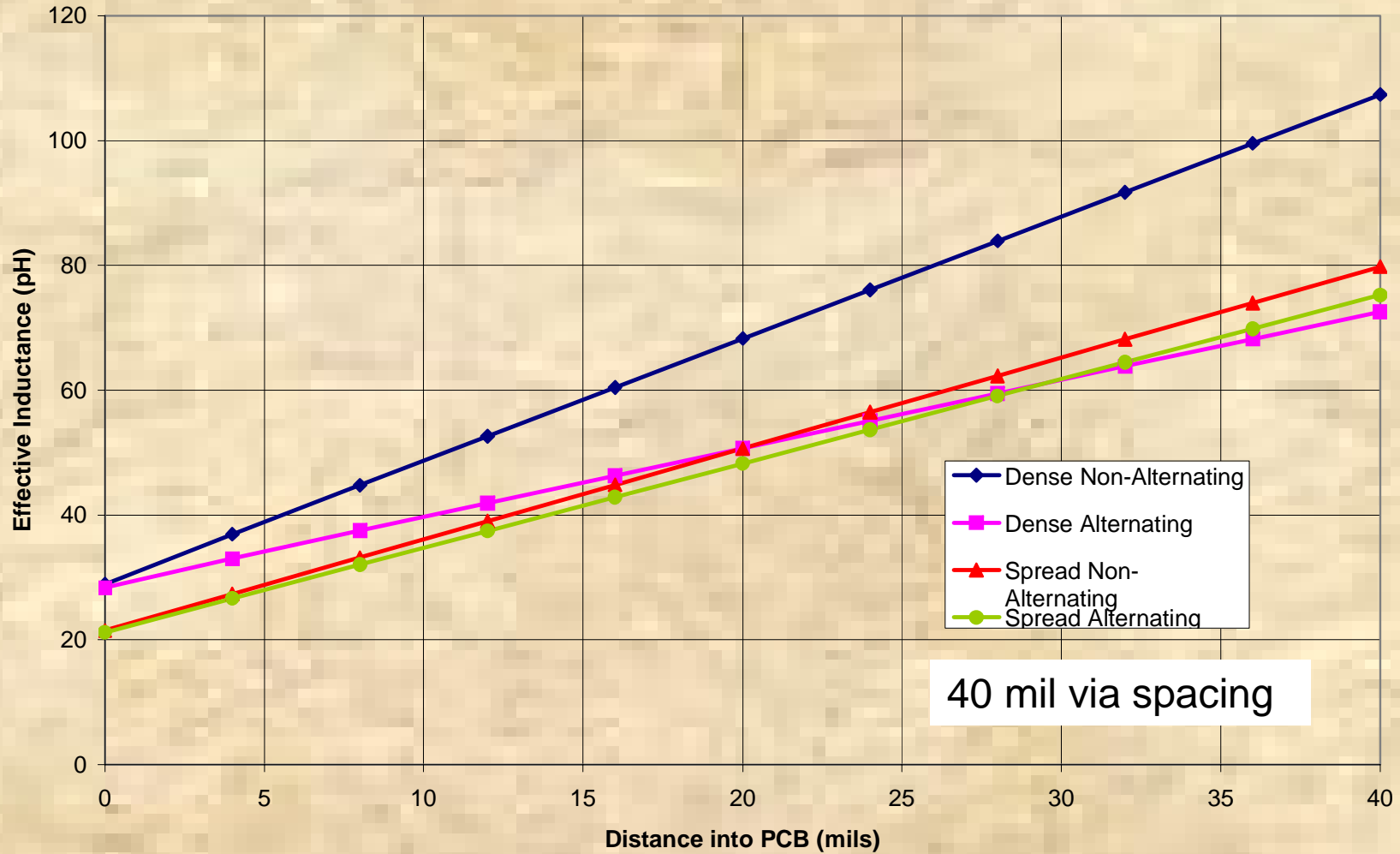
Effective Inductance for 16 Decoupling Capacitors for Dense and Spread Configurations and Plane Pair Depth



Number of Capacitors

     


 Effective Inductance vs. Number of Capacitors and Plane Pair Depth




40 mil via spacing

Effect of Plane width on Inductance

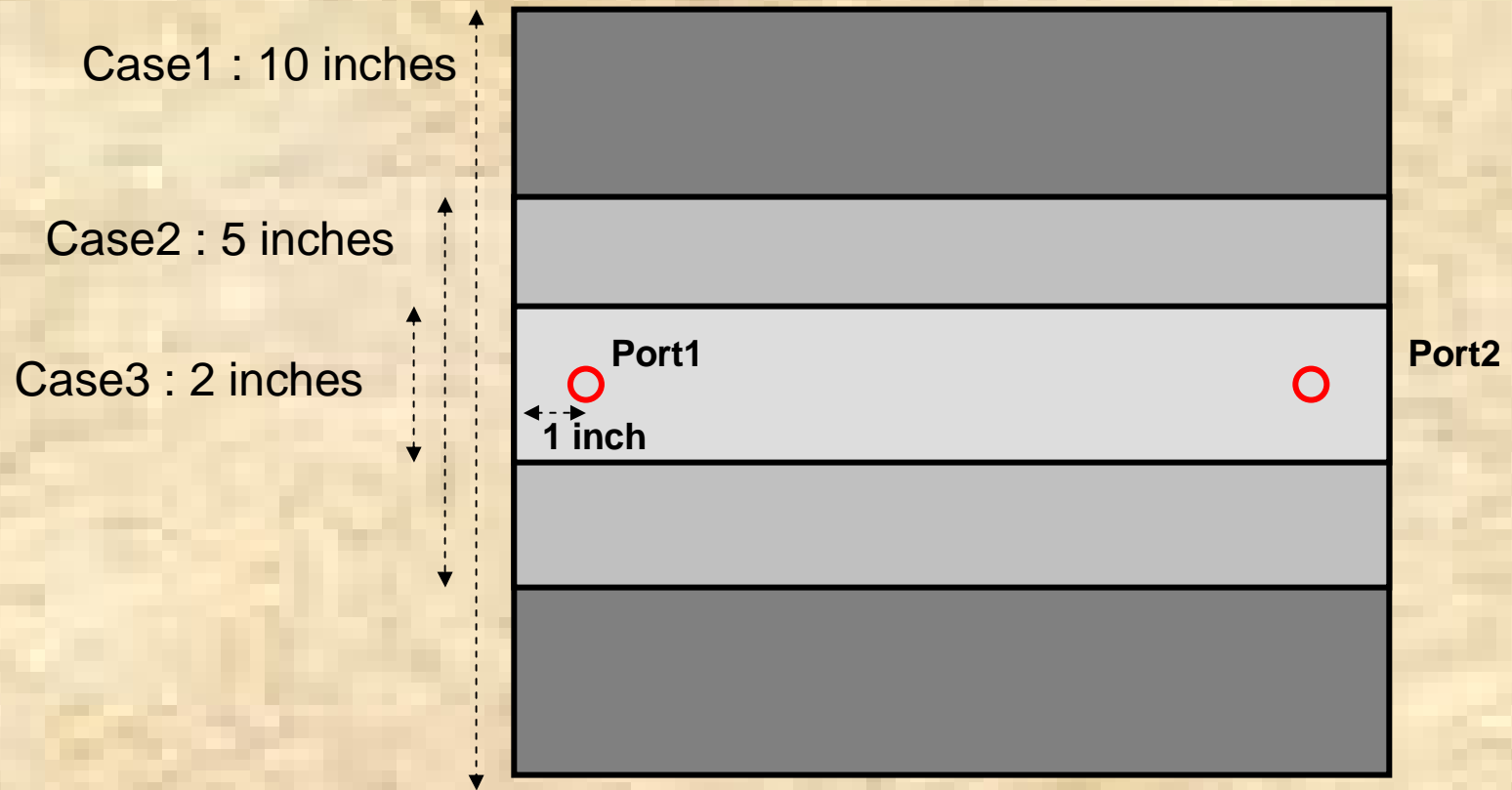


Inductance as Board Width Changes (Current Density Also Changes)

Case1 : 10 inches

 


~ 250pH

Case2 : 5 inches

 

~ 330pH

Case2 : 2 inches

 


~ 560pH

Summary

- Capacitance values should be as large as possible within the package size
- In most cases, IC takes charge from between the plates, capacitors replenish that charge
- Capacitors are better able to provide charge when spread out
- If placed near each other, capacitors should alternate power/ground pins
 - Worst configuration is when capacitors are close together and all pins in the same direction
- When plane pair is deep in PCB stackup, effective inductance is higher

Conventional Wisdom

 - ~~Need a variety of capacitance values to maintain low impedance over frequency range~~
- ~~Many capacitors of one value is better than many values~~
- Place capacitors close to ICs as possible
- ~~Location does not matter~~
- ~~Spread capacitors over entire board~~





Backup

Modeling Technique

- Difficult to model many layer PCB with full wave models
- Multi-Via Transition Tool (MVTT)
 - Breaks multiple layers into individual via transitions
 - Cavity resonance technique to find impedance between planes
 - Capacitance calculation for via-to-plane effects
 - Concatenate S-parameters from all individual elements

Breaking the Problem

 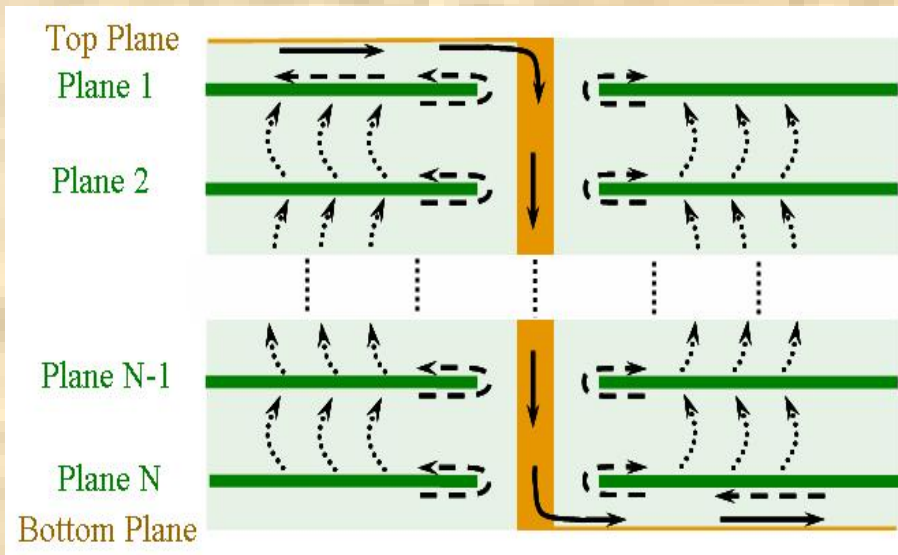

Via Configurations

