



Schéma équivalent:

① → Distances d'entrée:  $R_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{be}}{I_{be}} = \frac{V_{be}}{h_{21(1)} \cdot i_{b1} + h_{21(2)} \cdot i_{b2}}$

$$R_{in} = \frac{h_{21(1)} \cdot i_{b1} + h_{21(2)} \cdot (i_{b1} + h_{21(1)} \cdot i_{b1})}{h_{21(1)} \cdot i_{b1} + h_{21(2)} \cdot i_{b2}}$$

$$R_{in} = h_{21(1)} + h_{21(2)} + h_{21(2)} h_{21(1)} = [h_{21(1)} + h_{21(2)}] [1 + h_{21(1)}]$$

Si on prend  $h_{21(1)} = h_{21(2)}$  on obtient:  $R_{in} = h_{21(1)} (1 + h_{21(1)})$  soit  $R_{in} \approx h_{21(1)} \cdot h_{21(1)}$

② → Gain en courant:

Le gain en courant s'exprime par  $\beta_c = \frac{I_{out}}{I_{in}} = \frac{I_b}{I_c}$

$$\frac{I_c}{I_b} = \frac{h_{21(1)} \cdot i_{b1} + h_{21(2)} \cdot i_{b2}}{h_{21(1)} \cdot i_{b1} + h_{21(2)} \cdot (i_{b1} + h_{21(1)} \cdot i_{b1})}$$

$$\frac{I_c}{I_b} = h_{21(1)} + h_{21(2)} + h_{21(1)} h_{21(2)}$$

$$\text{Si } h_{21(1)} = h_{21(2)} \Rightarrow \frac{I_c}{I_b} = h_{21(1)} = h_{21(1)}^2 + 2h_{21(1)}$$

Soit  $I_c \approx h_{21(1)}^2$