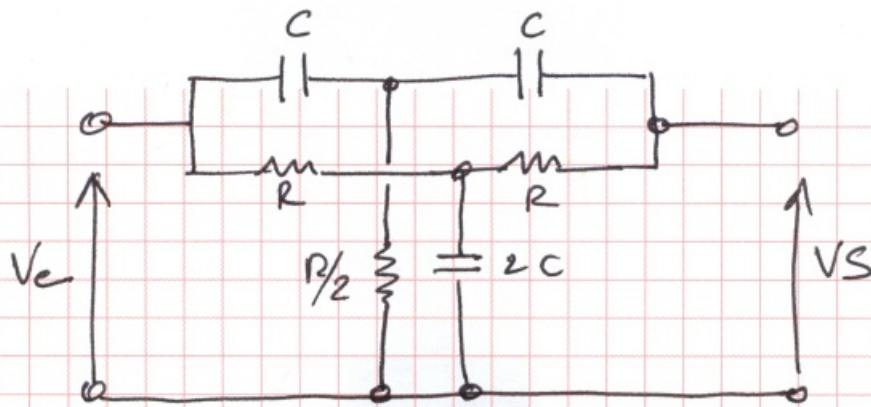


Filtre réjecteur double T ponté



On transforme chaque T en π :

$$\left\{ \begin{array}{l} \Sigma \underline{Y}_i = \frac{2}{R} + 2j\omega C \\ \underline{Y}_{13} = j\omega C \frac{x}{2(1+jx)} \\ \underline{Y}_{23} = \underline{Y}_{21} = j\omega C / (1+jx) \end{array} \right. \quad \left\{ \begin{array}{l} \Sigma \underline{Y}'_i = \frac{2}{R} + 2j\omega C \\ \underline{Y}'_{13} = \frac{1}{2R(1+jx)} \\ \underline{Y}'_{23} = \underline{Y}'_{21} = j\omega C / (1+jx) \end{array} \right.$$

On réunit les 2 quadripôles qui sont reliés en // :

les admittances s'additionnent 2 à 2 :

$$\underline{Y}''_{13} = \underline{Y}_{13} + \underline{Y}'_{13} = \frac{(1-x^2)}{2R(1+jx)}$$

$$\underline{Y}''_{23} = \underline{Y}''_{21} = \underline{Y}_{21} + \underline{Y}'_{21} = \frac{j4x}{2R(1+jx)}$$

$$\text{On obtient } \underline{T} = \frac{V_s}{V_c} = \frac{\underline{Y}''_{13}}{\underline{Y}''_{13} + \underline{Y}''_{23}} = \frac{(1-x^2)}{1+4jx-x^2}$$

$$\underline{T} = \frac{1 + (j \frac{\omega}{\omega_0})^2}{(1 + j \frac{\omega}{\omega_1})(1 + j \frac{\omega}{\omega_2})}$$

$$\text{avec } \omega_0 = \frac{1}{RC}$$

$$\omega_1 = \frac{1}{(\sqrt{3}+2)RC}$$

$$\omega_2 = \frac{1}{(2-\sqrt{3})RC}$$

CQFD