



This circuit amplifies the signal from three microphones then compairs the amplitude triggering an output if the signal is louder on the left or right. These signals through the Arduino control a servo to turn a head.

The LM324 chip has four OpAmps that can also be used as amps or comparitors. The LM324 chips are powered by the 5-12V power supply (pins not shown).

Description	Sound localization sensor with microcontroller and servo control		
Drawn By	Fileark	Date	2011 05 09
Company	<a href="http://Fileark.com">http://Fileark.com</a>		
Rev	01.00		