
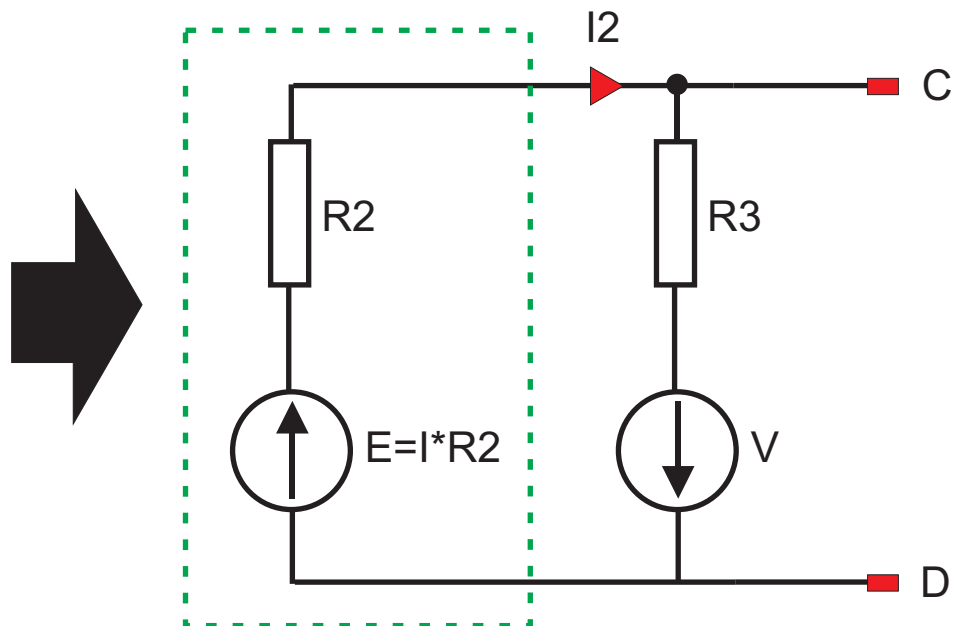
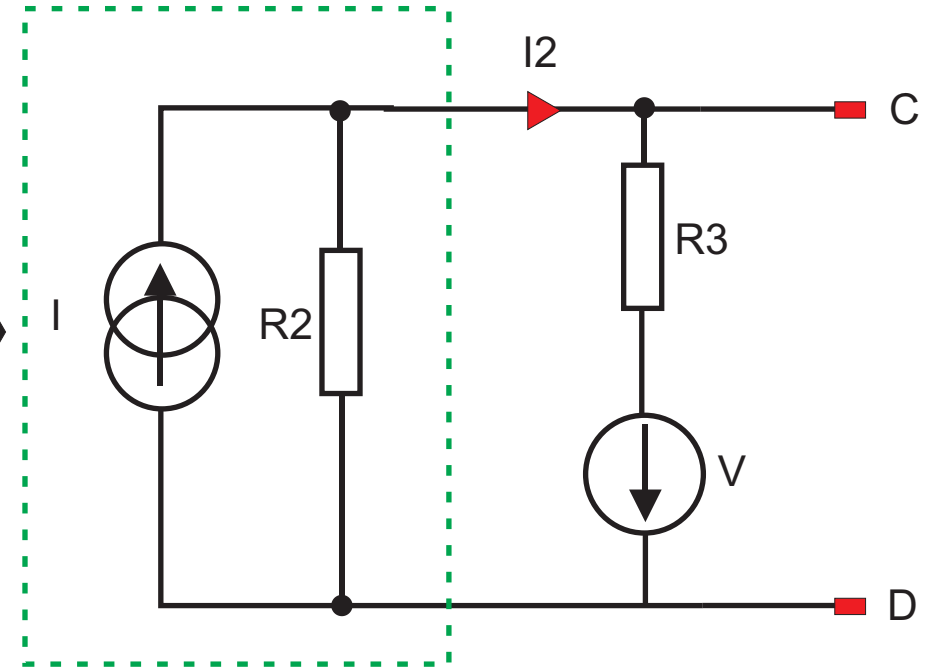


CALCUL DE E_{th}

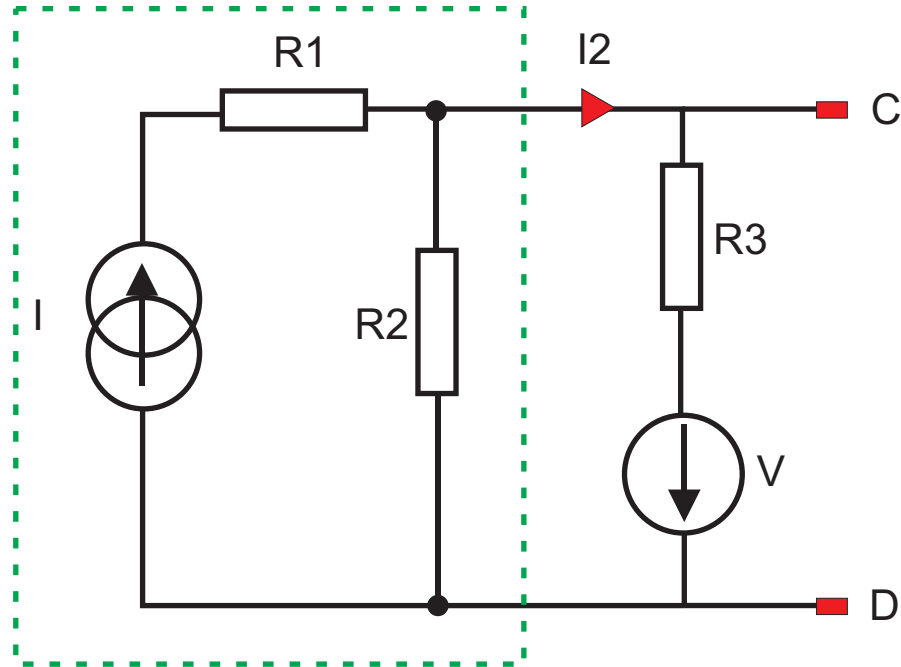Pour trouver E_{th} on cherche ce que vaut $V(CD)$ à vide.



$$E_{th} = V(CD)_0 = -V + R3 * I2 = E - R2 * I2$$

$$I2 = (R2 * I + V) / (R2 + R3)$$

$$\Rightarrow E_{th} = (-V * R2 + R3 * I) / (R3 + R2)$$