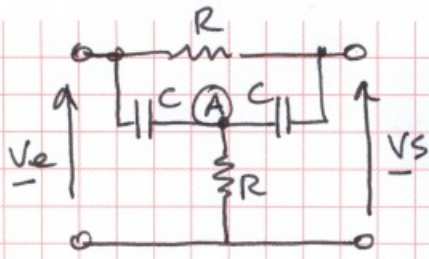


HULK28
pour NECCO

Filtre en "T ponté"
Coupe-bande⁺



$$\underline{V_s} = \underline{V_A} + \underline{Z_C} \underline{I}$$

$$\underline{I} = \frac{\underline{V_e} - \underline{V_s}}{R}$$

$$\underline{V_s} = \underline{V_A} + \frac{\underline{Z_C}}{R} (\underline{V_e} - \underline{V_s}) \quad (1)$$

Millmann en A:

$$\underline{V_A} = \frac{R(\underline{V_e} + \underline{V_s})}{2R + \underline{Z_C}} \quad (2)$$

On injecte (2) dans (1)

$$\underline{V_s} = \frac{R(\underline{V_e} + \underline{V_s})}{2R + \underline{Z_C}} + \underline{Z_C} \left(\frac{\underline{V_e} - \underline{V_s}}{R} \right) = \frac{R^2(\underline{V_e} + \underline{V_s}) + \underline{Z_C}(2R + \underline{Z_C})(\underline{V_e} - \underline{V_s})}{R(2R + \underline{Z_C})}$$

$$\Rightarrow \underline{V_s} [2R^2 + R\underline{Z_C}] - R^2 + 2R\underline{Z_C} + \underline{Z_C}^2 = \underline{V_e} (R^2 + 2R\underline{Z_C} + \underline{Z_C}^2)$$

$$\Rightarrow \underline{T} = \frac{\underline{V_s}}{\underline{V_e}} = \frac{R^2 + \underline{Z_C}(\underline{Z_C} + 2R)}{R^2 + (3R + \underline{Z_C})\underline{Z_C}} = \frac{R^2 + \frac{1}{j\omega} \left(\frac{1}{j\omega} + 2R \right)}{R^2 + \frac{1}{j\omega} \left(\frac{1}{j\omega} + 3R \right)}$$

$$\Rightarrow \underline{T} = \frac{R^2 + \left(\frac{1}{j\omega} \right)^2 + \frac{2R}{j\omega}}{R^2 + \left(\frac{1}{j\omega} \right)^2 + \frac{3R}{j\omega}} = \frac{1 + \left(\frac{1}{jRC\omega} \right)^2 + \frac{2}{jRC\omega}}{1 + \left(\frac{1}{jRC\omega} \right)^2 + \frac{3}{jRC\omega}}$$

$$\Rightarrow \underline{T} = \frac{1 + \left(j \frac{\omega_0}{\omega} \right)^2 - j 2 \left(\frac{\omega_0}{\omega} \right)}{1 + \left(j \frac{\omega_0}{\omega} \right)^2 - j 3 \left(\frac{\omega_0}{\omega} \right)} = \frac{(1 - j \frac{\omega_0}{\omega})^2}{(1 - j \frac{\omega_0}{\omega})^2 - j \frac{\omega_0}{\omega}} \quad \left(\text{avec } \omega_0 = \frac{1}{RC} \right)$$

$$\text{Soit } \underline{T} = \frac{1}{1 - \frac{1}{j \frac{\omega_0}{\omega} - j \frac{\omega}{\omega_0}}} = \frac{1}{1 - \frac{1}{-j \left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0} \right)}}$$

d'où

$$\underline{T} = \frac{1}{1 + \frac{1}{j \left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0} \right)}} \quad \text{CQFD.}$$