

$$\begin{cases} V_1 = R_1 I_1 + R_3 (I_1 + I_2) \\ V_2 = R_2 I_2 + R_3 (I_1 + I_2) \end{cases}$$

